Advantages: Additional number of features

- i) High input impedance
- High gain accuracy than use of sing op-amp ii)
- High CMRR iii)

Suppose the voltage

i)
$$u_1 = -1$$

 $u_2 = +1$ $\bigg\}$ $u_d = 2V$

- $u_1 = 1$ ii) $u_d = 2V$ $u_2 = 3$
- High gain stability with low temperature coefficient iii)
- iv) Low dc off set
- Low output impedance v)

One application



Balanced

$$\left(\frac{R_2}{R_3} = \frac{R_1}{R_4}\right)$$

Change in small resistance will be measured/translated into v_0

Saying $B_1 + B_2 = 1 + \alpha_1 + \alpha_4$ making this assumption

$$u_{03} = \frac{1}{SGR_1} \frac{-2(1-\alpha)S^2C_1C_2R_1R_2}{[S^2C_1C_2R_1R_2+2\alpha_2C_2R_2+1]} \qquad \qquad s = jw \qquad u_{03} = 0$$
$$= -2(1\alpha)SC_sR_2 \qquad \qquad w = 0 \qquad u_{03} = 0$$

= BPF- transfers fxn

$w = \infty$

At $w_0^2 = \frac{1}{GC_2} R_1 R_2$ =Reasonant frequency

Once again integrate $u_{02} = \frac{-2(1-\alpha)S^2R_2R_2}{S^2R^2C^2(S^2C_1C_2R_1R_2 + 2\alpha_2C_2R_2 + 1)}$

s = jw

w = 0 $u_{02} = infinity$

$$w = \infty$$
 $u_{02} = 0$

Hpf- transfer fxn

- These three outputs are simultaneously available in this port be active filter. Hence add able in this cet hence its called universal _
- e can get using additional summing amplifier. Hencron
- Poles of the system are lie on the negative side hence the systems is stable filter fxn
- One can cascade such filter block one can get higher order filter block. -

ACTIVE FILTERS

Double integrator loop (2 integrator are used)



- High Q reduces horizontal distance W/2Q
- *jw* is going to be close to w_0 resonant frequency $j\left(\sqrt{1-\frac{1}{40^2}}\right)$
- Poles on imaginary axis forms resonant frequency
- If the pole Q is high the actual frequency is close to resonant frequency
- The LP, HP and BP equations above give us information about the system i.e. 2nd order system, the pole being second order. And the high pole Q- means high quality factor (Qquality factor)
- If Q is infinity (when $\propto = 0$ since $Q = \frac{1}{2\alpha}$, meaning there is no real part the poles fall on imaginary axis.
- It means there is no feedback i.e. there is no \propto connection of



i.e. there is no u_i and hence u_{02} is not feedback as shown therefore the cct has two integrators and inversion from the different equation above.

$$\frac{d^2u_0}{dt^2} + \delta u_0$$

- This is second order system of harmonic oscillator
- When $\frac{du}{dt}$ term is not present this is **<u>Harmonic Oscillator</u>**
- It can by itself without input the output will be close to resonant frequency
- $(1-\alpha)R$ still can exist as R and u_i can still exist, but as an oscillator u_1 can as well be connected to ground

Potential across R _

$$u_{i} \longrightarrow \mathbb{R} \qquad u_{i} - \frac{u_{i}}{SCR}$$
$$\left(u_{i} - u_{i} - \frac{u_{i}}{SCR}\right) = \frac{u_{i}}{SCR}$$

Current across outermost

$$R = \frac{u_i}{SCR^2}$$

Input impendence Z;

$$Z = \frac{u_o}{I_i} = \frac{u_i}{SCR^2/u_i}$$

 $= SCR^2$; impendence Z is SCR^2 which is that of an inductor.



source) to output. Total admittance

$$\frac{u_o}{u_i} = \frac{1/R_s}{1/R_s + SC + 1/SL}$$

$$=\frac{SL/R_s}{S^2LC+SL/R_s+1}$$

(summance of all admittance) Re-write using state variable felt to KHN network

Conductance linking the output (with

$$\omega_{o} = \frac{1}{\sqrt{LC}}$$
$$\omega_{o} \theta = \frac{R_{s}}{L}$$
$$\theta = \frac{R_{s}}{\omega_{o}L}$$

$$=\frac{S/_{\omega_o\theta}}{S^2/_{\omega_o^2}+S/_{\omega_o\theta}+1}$$



$$2u_i = \frac{\frac{2.5}{\omega_o \theta}}{\frac{S^2}{\omega_o^2} + \frac{S}{\omega_o \theta} + 1}$$
$$\omega_o = \frac{1}{\sqrt{CR^2}C} = \frac{1}{RC} = \frac{1}{\sqrt{LC}}$$



Take portion of $\frac{-1}{RC} \frac{\delta \varphi_o}{\partial t} \left(\frac{1}{SRC} \right)$ and take it to the output $\gamma \varphi_o$

$$\alpha \frac{\delta \varphi_o}{\partial t} = \frac{-\frac{R_b}{R_a}}{R_1 C_1} \frac{\delta \varphi_o}{\partial t}$$

RC will facilitate oscillation ($\alpha - ve$).

RC will be large and grow to infinity. At RC = ∞ all the poles of the system falls along the imaginary axis hence an oscillation.

RC goes to infinity as amplitude builds up.

NB:

Remember we had seen α being fed to summer on +ve terminal forms/enables a filter to be designed.

Now substitute $s = j\omega$

$$\frac{1 + \frac{R_b}{R_a}}{1 + \frac{R_1}{R_2} + \frac{C_2}{C_1} + j\left(\frac{1}{\omega C_2 R_1} + \omega C_1 R_2\right)}$$

In phase $\omega = \frac{1}{\sqrt{C_1 C_2 R_1 R_2}}$

At that frequency of oscillation

$$\frac{1 + \frac{R_b}{R_a}}{1 + \frac{R_2}{R_1} + \frac{C_1}{C_2}} = 1$$

Conditions for oscillation

$$\frac{1}{1 + \frac{R_2}{R_1} + \frac{C_1}{C_2}} = 1$$
Connect input to output.
Conditions for oscillation

$$\frac{R_b}{R_a} = \frac{R_2}{R_a} + \frac{C_1}{2} + \frac{C_1}{2} + \frac{C_1}{R_a} + \frac{C_1}$$

Attained by setting

$$R_b/R_a = 2$$

If ${R_b}/{R_a} > 2$ it will build up oscillation

 $at^{R_b}/R_a = 2$ poles line on the imaginary – oscillator

 $R_b/R_a < \alpha$ Decay

Then connect the loop from input to output and remove the input signal.

Connect input to output.

Preview from Notesale.co.uk page 49 of 93

- The condition in equation (iv) and (v) are known as Barkhausen criteria in rectangular form for $A_r(jw) = A_{ro}$
- In polar form Barkhausen criteria is given by

 $B(jw) A_r(jw) = |B(jw)A(jw)| B(jw)A_r(jw) = 1$ |B(jw)A(jw)| = 1 $B(jw) A(jw) = +n360^0$

- This condition of unit loop-gain and zero loop phase shift is known as criterion for sustained oscillations.
- Since ac power required by the input of an amplifier is lees than output power, it is possible to make the amplifier supply its own input and hence generate self-sustained oscillations.
- The active device in the amplifier circuit thus changes the dc power supplied to it into ac energy at the output.
- The initiating ac triggering signal is provided by the abrupt flow of forward bias device current from its zero value.
- This abrupt signal pulse contains all possible sinusoidal frequencies out which a particular frequency is selected by the frequency sensitive cct comparents to provide a positive self-sustaining feedback.

Note the overall fain $A_f = \begin{pmatrix} -1 \\ 1-B \end{pmatrix}$, ander the condition above, it tends to be infinite and hence the amplitude multiple self-limited. This funiting action is generally provided by the non-linear cutoff and saturation regions of the active device characteristics where available amplification ceases to satisfy the condition for oscillations. However, with the help of linear analysis, one can obtain the frequency of oscillations and the conditions for starting of the oscillations.

The choice of feedback network or frequency determining cct is decided by the frequency range in which the oscillator is intended to work.

Frequency determining network can be RC-type and LC type for frequency upto few look HZ.

The choice of an optimal cct is detected by its requirements regarding;

- i) Frequency stability
- ii) Amp stability
- iii) Freedom from non-linear distortion



 Y_a - is the active device(s) making the circuit go to saturation. It is not a feedback but a biasing circuit. Also called input impedance. (Takes the active device to oscillation)

Objective

- To know whether such circuit can be made into an oscillator?
- Analysis of such a phenomenon.
- Transistor could be BJT, FET, or Op-Amp

$$\begin{pmatrix} Y_a + \frac{1}{\gamma_e^{(\beta+1)}} + Y_c & -Y_c \\ g_m - Y_c & Y_b + \frac{1}{\gamma_{ce}} + Y_c \end{pmatrix} \begin{pmatrix} Y_p = Y_a \\ Admittance \ at \ output \end{pmatrix}$$

$$\Delta Y = \left(Y_a + \frac{1}{\gamma_e^{(\beta+1)}} + Y_c\right) \left(Y_b + Y_c + \frac{1}{\gamma_{ce}}\right) + Y_c (g_m - Y_c) = 0$$

This equation gives the condition as well as the frequency of oscillation. At certain frequency it should be = 0.

Simplify:

$$Y_{a}Y_{b} + Y_{a}Y_{c} + \frac{Y_{b}}{\gamma_{e}^{(\beta+1)}} + \frac{Y_{c}}{\gamma_{e}^{(\beta+1)}} + \frac{1}{\gamma_{e}^{(\beta+1)}\gamma_{e}} + Y_{b}Y_{c} + Y_{c}^{2} + \frac{Y_{c}}{\gamma_{ce}} + Y_{c}g_{m} - Y_{c}^{2} = 0$$

$$\sum Y_{a}Y_{b}Y_{c} + \frac{1}{\gamma_{e}^{(\beta+1)}}(Y_{b} + Y_{c}) - \frac{1}{\gamma_{e}^{(\beta+1)}\gamma_{e}} + \frac{1}{\gamma_{ea}}(Y_{a} + Y_{c}) \oplus Q_{m} = 0$$
These are the factors
$$065093$$
For such condition to be possible ve 1a to 5 show that =0.

The equation must have the real and imaginary part and they should be made to go to zero. Select up the possible combinations.

Real part =0

Im=0

Choose the possible combination for this to work.

 $Y_c = \frac{1}{g\omega L}$ feed back dement takes one part/ one type and other two opposite.

 $Y_a = j\omega C_1$

 $Y_b = j\omega C_2$



$$-\frac{1}{w^{2}L_{1}L_{2}} + jwC\left(\frac{1}{jwL_{1}} + \frac{1}{jwL_{2}}\right)$$
$$-\frac{1}{w^{2}L_{1}L_{2}} + jwC\frac{(L_{1}L_{2})}{jwL_{1}L_{2}} + \frac{1}{r_{e}(B+1)r_{ce}} = 0$$
$$w^{2} = C(L_{1}L_{2})$$
$$w \approx \sqrt{CL_{1}L_{2}}$$

Imaginary part

$$\frac{1}{r_e(B+1)}(Y_b + Y_c) + \frac{Y_a + Y_c}{r_{ce}} + gmY_c = 0$$

$$\frac{jwC - \frac{j}{wL_2}}{r_e(B+1)} + \frac{jwC - \frac{j}{wL_1}}{r_{ce}} + jwcgm = 0$$

Collect the coefficient of $1/_W$

$$\frac{jwC - \frac{J}{wL_2}}{r_e(B+1)} + \frac{jwC - \frac{J}{wL_1}}{r_{ce}} + jwcgm = 0$$

Collect the coefficient of $\frac{1}{w}$
 $jw\left(cgm + \frac{C}{r_e(A+1)} + \frac{1}{r_{ce}}\right) = \frac{J}{w}\left[\frac{1}{r_1} + \frac{1}{e_2}\right] 68$ of 93
 $w^2C\left[gm + \frac{1}{r_e(B+1)} + \frac{1}{r_{ce}}\right] = \left(\frac{1}{r_e(B+1)} + \frac{1}{r_{ce}L_2}\right)$

 $w^2C(gm)$

 $w_0 = C(L_1 + L_2)$

$$C^{2}(L_{1}+L_{2})gm = \left(\frac{1}{r_{e}(B+1)L_{2}} + \frac{1}{r_{ce}L_{2}}\right)$$

Summary

These are two of the most popular LC – oscillators' transistor or FET oscillator existing today.

The analysis is valid only that in FET we replace open cct for $r_e(B+1)$ and for r_{ce})the rest remain the same). The same analysis remains.

Hartley	2-	inductors	1- capacitor

Culprit 2inductor 2- capacitors NB: the phase shift oscillator in figure above have been implemented by inter-changing R and C in the phase shift sections. It follow that for such an oscillator the frequency of oscillation is given by $w_0 = \frac{\sqrt{6}}{RC}$ and given condition is $|A_{uo}| > 29$.

FEEDBACK THEORY

- Important for circuit design.
- Negative and positive.
- Advantages and disadvantages.

Consider



Discussing negative feedback:

- To remove distortion used to improve the performance of circuit (Used in eplepsy).

$$\frac{X_0}{X_i} = \frac{G}{1 + GH}$$

If G and H are positive quantities then

$$\frac{G}{1+GH} < G$$

- Hence a feedback (negative) amplifier has less gain than open-loop gain amplifier (reduction in transfer parameter).
- Reduction in active parameter sensitivity.

- The active components depends on operating point.
- BJT = $g_m \infty I$ and dependent on temperature

Feedback situation makes an amplifier with gain more than 1, using positive, attenuators, resistors, capacitors, inductors.

In this case H is made more stable hence

$$G_f = \frac{X_0}{X_i} = \frac{G}{1 + GH}$$

$$\cong \frac{1}{H} if GH \gg 1$$

G is the active parameter now made insetive

H made from passive device e.g.R, C and linear The resultant gain is G_f $\frac{\partial G_f / G_f}{\partial G / G} = \int_G^{G_f}$ (Sensitivity factor of f relation to f **84** 0 **93** (Sensitivity factor of f relation to f **84** 0 **93** = % variation in G_f compare if year % variation in G is called sensitivity) $= \frac{\partial G_f}{\partial G} \times \frac{G}{G_f}$ $= \frac{1}{1 + GH}$

 $\frac{1}{1+GH}$; is important equation for sensitivity in designing amplifiers G – H forms a loop hence GH – loop gain. If GH >> very high $\frac{1}{1+GH} \ll 1$ hence sensitivity factor gets to zero.

Loop Gain

- GH (negative feedback)

+ GH (positive feedback)



NB: RC network produces/introduces definite phase shift.

Phase Lead



Hence phase shift due to an RC circuit is always $\leq 90^{\circ}$ and it is a fraction of frequency.

$$\emptyset = \tan^{-}\left(\frac{X_{c}}{R}\right) = -\tan^{-}\left(\frac{X_{c}}{R}\right).$$

Hence if we want positive with 180⁰ phase shift we need attest three RC networks. Remember, since X₁, is frequency sensitive $A_1 = \frac{1}{2\pi f_c}$, the 180[°] phase lift also can be achieved only at a particular frequency.

Thus a simple RC oscillator can be built with an amplifier and a feedback network with three RC combination.

Such as oscillator is called phase shift oscillator.