

Multiple Choice Online Test

Indicate the correct answer by clicking on the button next to the numbers 1, 2, 3 or 4. There is only one correct answer per question. After you have answered **all** multiple choice questions compare your choices with the correct answers.

Electricity I

1.) If a current of 3 A is divided by the following circuit, the current flowing through the 4 Ohm resistor is ...

- 1 ☐ 3 A
- 2 ☐ 2 A
- 3 ☐ 1,5 A
- 4 ☐ 1 A


Explanation



2.) The diagram at the right shows part of a circuit into which a current I is flowing. Which ammeter shows the highest reading?

- 1 ☐ A_1
- 2 ☐ A_2
- 3 ☐ A_3
- 4 ☐ All three ammeters give the same reading


Explanation

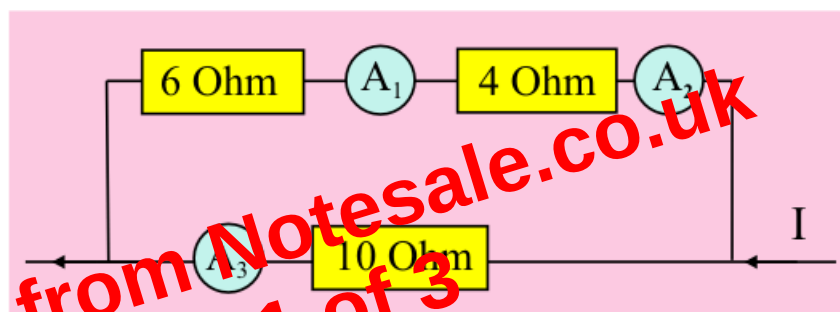


3.) The diagram to the right represents a part of a circuit containing an ohmic resistor, a voltmeter and an ammeter. If the reading on the ammeter A increases the reading on voltmeter V ...

- 1 ☐ increases in the same ratio.
- 2 ☐ increases, but not in the same ratio.
- 3 ☐ remains unchanged.
- 4 ☐ decreases in the same ratio.

Explanation

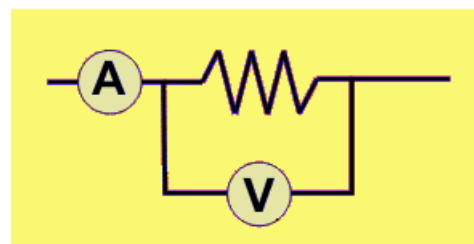

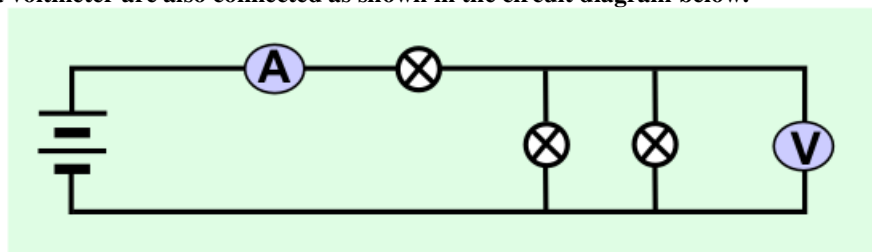4.) A battery is connected to two identical light bulbs in parallel as well as another identical bulb in series. An ammeter and a voltmeter are also connected as shown in the circuit diagram below.



One of the light bulbs connected in parallel is unscrewed. How will the ammeter and the voltmeter readings change?