

# Discharge of a Capacitance Through a Resistance

$$RCsKe^{st} + Ke^{st} = 0$$


$$(RCs + 1)Ke^{st} = 0$$

$$RCs + 1 = 0$$

$$s = \frac{-1}{RC}$$

$$v_C(t) = Ke^{-t/RC}$$

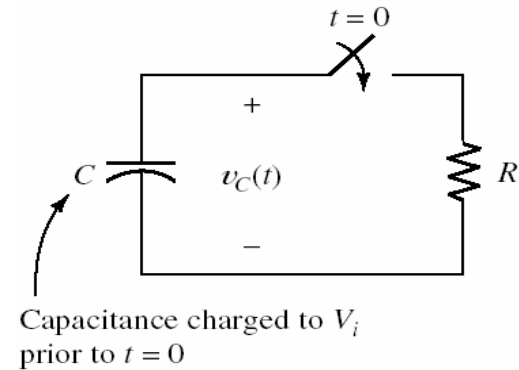Since voltage across the capacitor cannot change instantaneously (current would be infinite)



Voltage immediately after the switch closes

$$v_C(0^+) = V_i$$

$$v_C(0^+) = V_i = Ke^0 = K$$

Thus,

$$v_C(t) = V_i e^{-t/RC}$$

# Second-Order Circuits


Circuits with two energy-storage elements

Write KVL:

$$L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int_{t_0}^t i(t) dt + v_C(0) = v_s(t)$$

$$L \frac{d^2 i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{1}{C} i(t) = \frac{dv_s(t)}{dt}$$
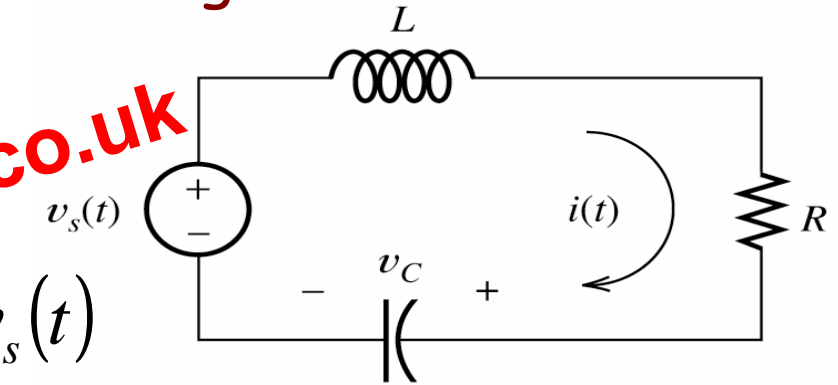
$$\frac{d^2 i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = \frac{1}{L} \frac{dv_s(t)}{dt}$$



(a) Electrical circuit

Define:

$$\alpha = \frac{R}{2L} \quad (\text{Damping coefficient})$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (\text{Undamped resonant frequency})$$

$$f(t) = \frac{1}{L} \frac{dv_s(t)}{dt} \quad (\text{forcing function})$$

$$\frac{d^2 i(t)}{dt^2} + 2\alpha \frac{di(t)}{dt} + \omega_0^2 i(t) = f(t)$$



# Solution to the DE:

$$(s^2 + 2\alpha s + \omega_0^2) = 0$$

The roots of the characteristic equation are:

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

Define the damping ratio as:  $\zeta = \frac{\alpha}{\omega_0}$

The form of the complementary solution depends on the value of the damping ratio

		Roots (s1, s2)
$\zeta > 1$ ( $\alpha > \omega_0$ )	Overdamped	Real and distinct
$\zeta = 1$ ( $\alpha = \omega_0$ )	Critically damped	Real and equal
$\zeta < 1$ ( $\alpha < \omega_0$ )	Underdamped	Complex



# Example (cont.)

$$i(t) = C \frac{dv_c(t)}{dt}$$

We need to find the  $v_c(t)$  for  $R = 300, 200, 100 \Omega$

$$L \frac{di(t)}{dt} + Ri(t) + v_c(t) = V_s$$


$$LC \frac{d^2 v_c(t)}{dt^2} + RC \frac{dv_c(t)}{dt} + v_c(t) = V_s$$

$$\frac{d^2 v_c(t)}{dt^2} + \frac{R}{L} \frac{dv_c(t)}{dt} + \frac{1}{LC} v_c(t) = \frac{V_s}{LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 10000$$

$$\alpha = \frac{R}{2L} = \begin{cases} 15000 & \text{if } R = 300 \\ 10000 & \text{if } R = 200 \\ 5000 & \text{if } R = 100 \end{cases}$$

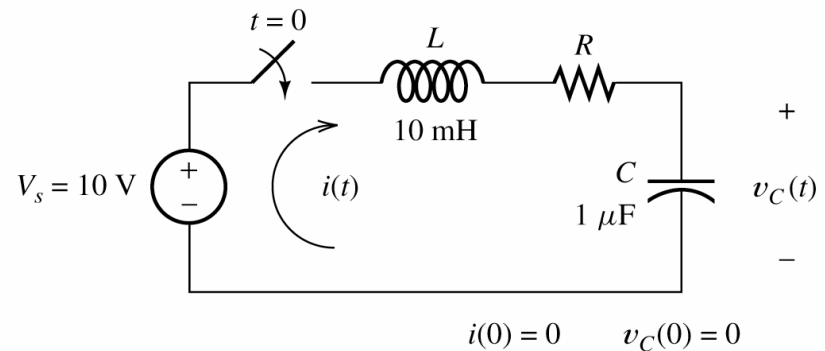Preview from Notesale.co.uk  
Page 25 of 32



$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (\text{Undamped resonant frequency})$$

$$\alpha = \frac{R}{2L} \quad (\text{Damping coefficient})$$

$$f(t) = \frac{1}{L} \frac{dv_s(t)}{dt} \quad (\text{forcing function})$$



# Comparing the three cases

