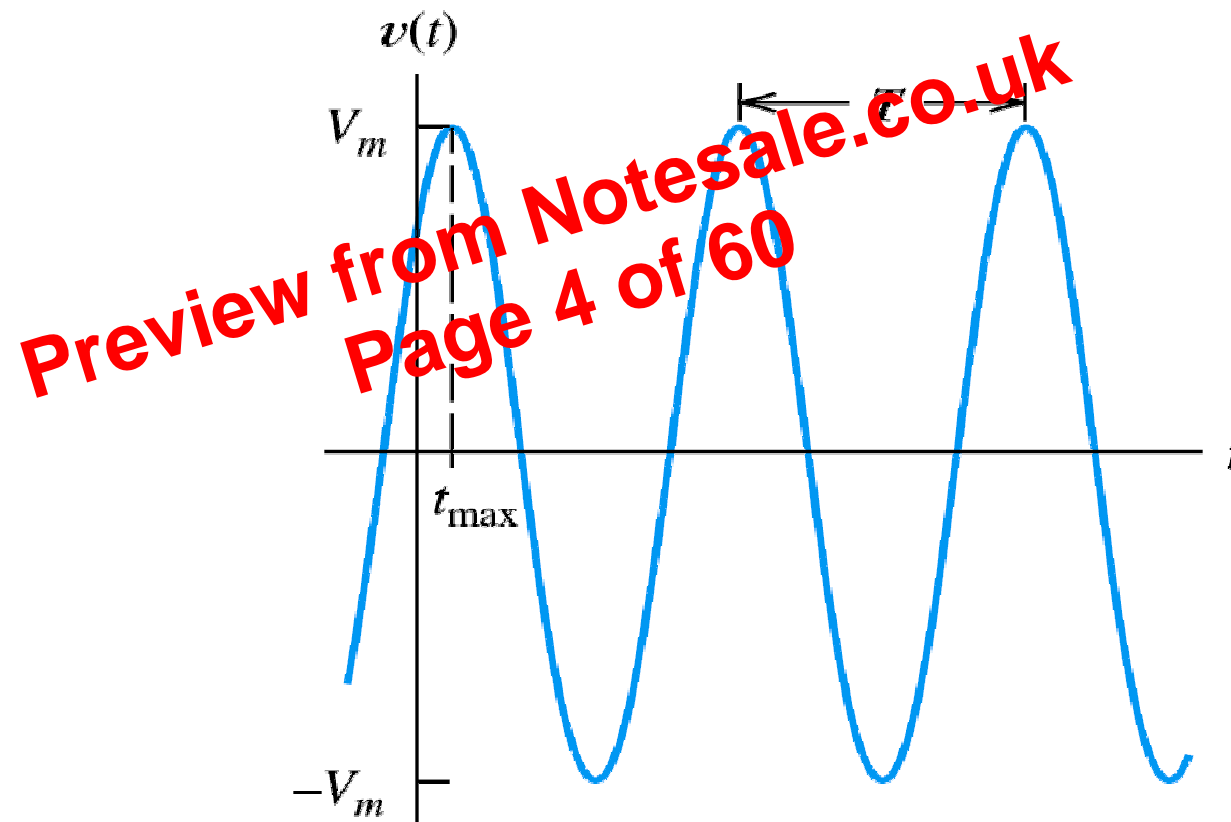


Sinusoidal Currents or Voltages



A sinusoidal voltage waveform given by $v(t) = V_m \cos(\omega t + \theta)$.
Note: Assuming that θ is in degrees, we have $t_{\max} = \frac{-\theta}{360} \times T$.
For the waveform shown, θ is -45° .

Real and Complex Signals

A complex number is given by:

$$Z = x + jy$$

Real part

Imaginary part

Preview from Notesale.co.uk
Page 8 of 60
Rectangular form


It can also be represented by a **POINT** in the complex Plane

Note that Z can be written as: $|Z| \angle \theta$

Polar form

Complex conjugate of z is:

$$z^* = x - jy$$

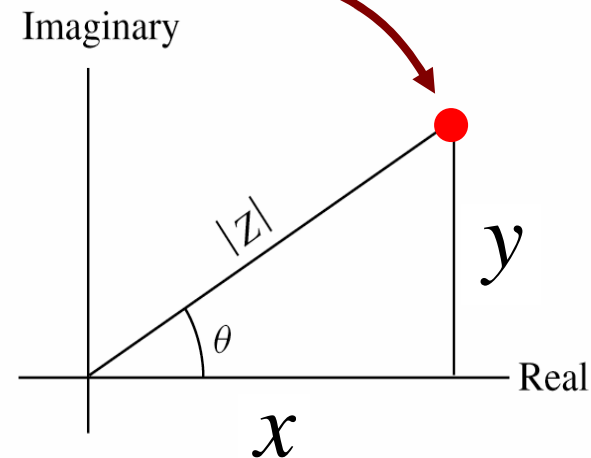

Complex Numbers

$$z = x + jy \leftarrow \text{Rectangular form}$$


Real part $\sqrt{-1}$ Imaginary part

Preview from Notesale.co.uk Page 10 of 60

A complex number can be represented as a **point** in the complex Plane

Complex conjugate of z is:

$$z^* = x - jy$$

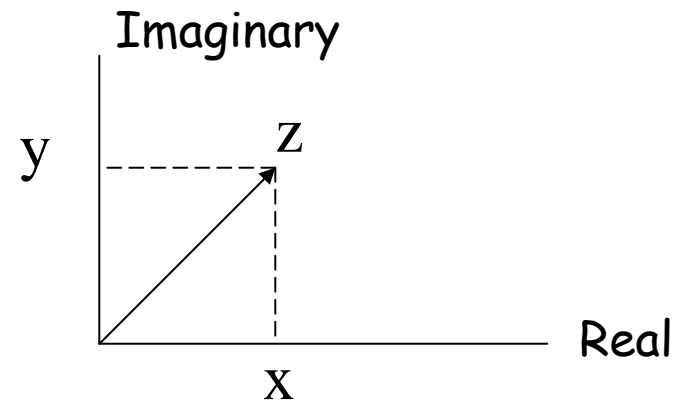

Complex Numbers in Polar Form

- Represent the complex number by the length of the arrow and the angle between the arrow and the positive real axis
- We write complex numbers in polar form as:

$$z = |z| \angle \theta$$

$$|z|^2 = x^2 + y^2 \implies |z| = \sqrt{x^2 + y^2}$$


$$\tan \theta = \frac{y}{x} \text{ or } \theta = \tan^{-1} \frac{y}{x}$$

Polar to Rectangular:

$$x = |z| \cos \theta$$

$$y = |z| \sin \theta$$

In exponential form: $= |Z| e^{j\theta}$

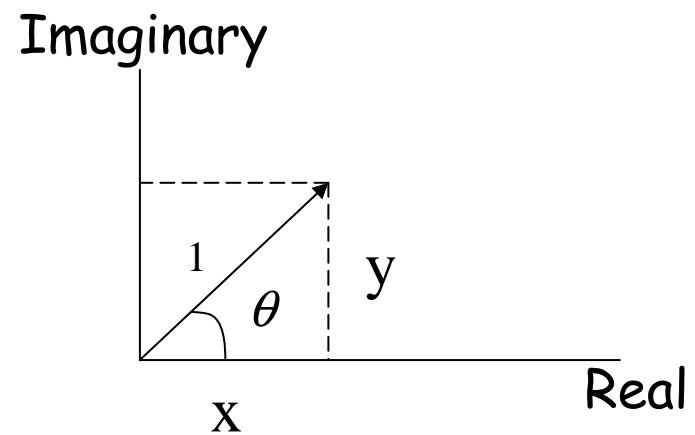

Forms of a Complex Number

$$z_2 = 10 + j5 \longleftarrow \text{Rectangular form}$$

$$z_2 = \sqrt{(10)^2 + (5)^2} \angle \tan^{-1}\left(\frac{5}{10}\right)$$

$$= 11.18 \angle 26.57^\circ \longleftarrow \text{Polar form}$$

$$= 11.18 e^{j26.57^\circ} \longleftarrow \text{Exponential form}$$

Important Note:

$$1 \angle 90^\circ = \cos 90 + j \sin 90 = j$$



Complex Impedances: Inductances

$$i_L = I_m \sin(\omega t + \theta)$$

$$\mathbf{I}_L = I_m \angle \theta - 90^\circ$$

$$v_L = L \frac{di_L}{dt}$$

$$= \omega L I_m \cos(\omega t + \theta)$$

$$\longrightarrow \mathbf{V}_L = \omega L I_m \angle \theta = V_m \angle \theta$$

Current through the inductor lags the voltage by 90°

$$V_L = \omega L I_m \angle \theta \angle (90^\circ - 90^\circ)$$

$$= \omega L \angle 90^\circ I_m \angle (\theta - 90^\circ)$$

$$= \omega L I_L \angle 90^\circ$$

$$= j\omega L I_L$$

$$\mathbf{V}_L = \mathbf{Z}_L \mathbf{I}_L$$


$Z_L = j\omega L$ is called the impedance of the inductor (measured in ohms)

Ohm's law in phasor form






Complex Impedances: Resistance
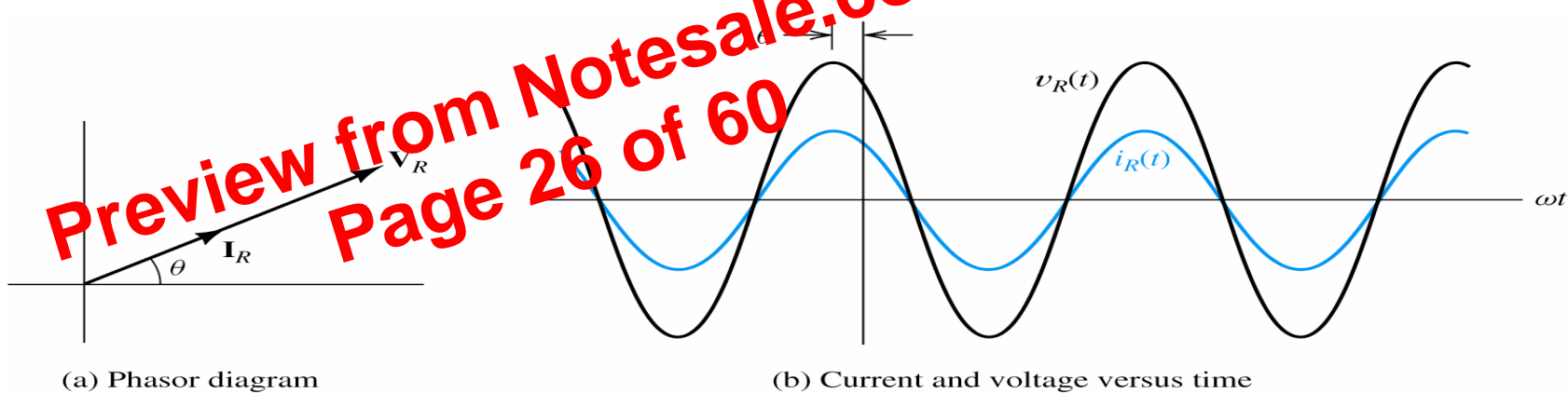
$$\mathbf{V}_R = R\mathbf{I}_R \Rightarrow \mathbf{Z}_R = R$$



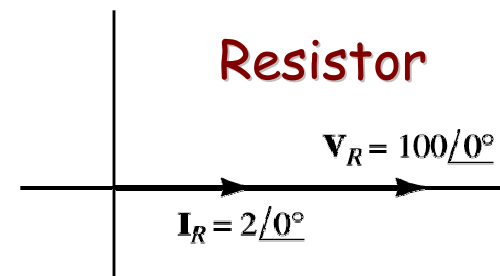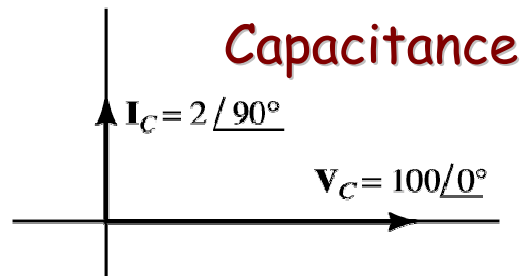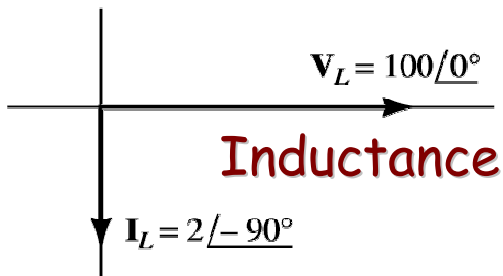In a pure resistor, current & voltage are in phase



The impedances that are pure imaginary are called **reactance**



Example (cont.)

Inductor:

$$Q_L = I_{rms}^2 X_L = (0.1)^2 100 = 1 \text{ VAR}$$

Capacitor:

$$Q_C = I_{C rms}^2 X_C = \left(\frac{0.1}{\sqrt{2}}\right)^2 (-100) = -0.5 \text{ VAR}$$

Resistor:

$$P_R = I_{R rms}^2 R = \left(\frac{0.1}{\sqrt{2}}\right)^2 100 = 0.5 \text{ W}$$

It is important to note that: $\begin{cases} P_L = 0 \\ P_C = 0 \end{cases}$


Check:

$$Q = Q_L + Q_C$$


$$P = P_R$$

In real life, the values are much bigger (kW, MW, kVA)

Thévenin and Norton Equivalent Circuits

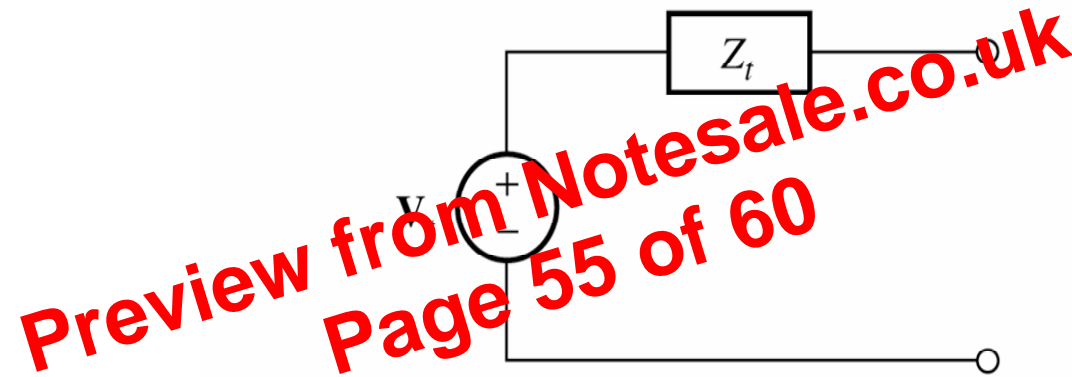

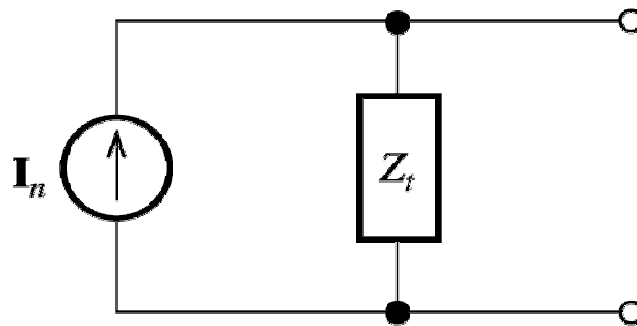
The Thévenin equivalent for an ac circuit consists of a phasor voltage source V_t in series with a complex impedance Z_t .




The Norton equivalent circuit consists of a phasor current source I_n in parallel with the complex impedance Z_t .

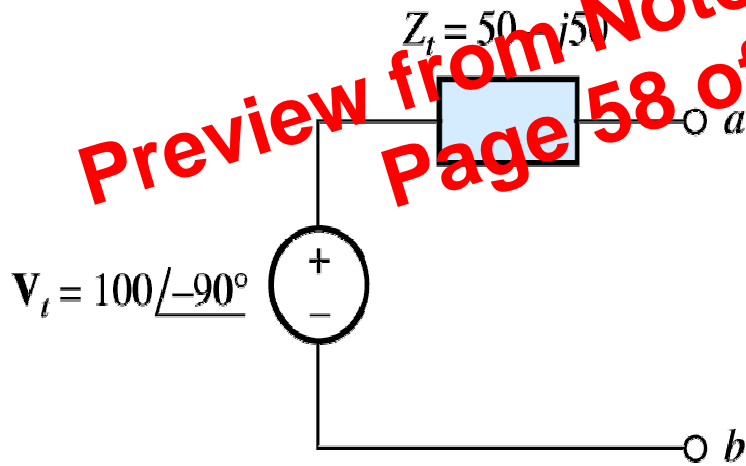Example (cont.)

Preview from Notesale.co.uk
Page 58 of 60



(a) Thévenin equivalent

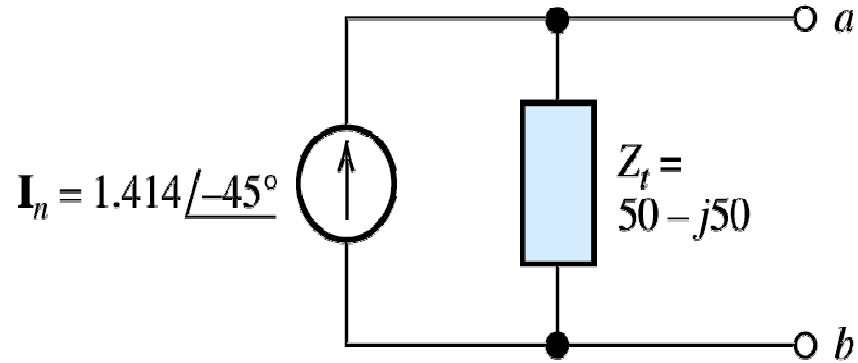

(b) Norton equivalent

