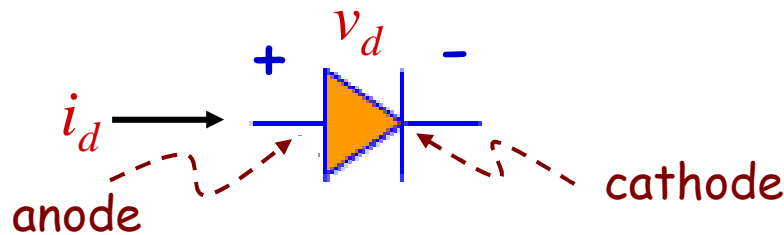


Basic Diode Concepts

- Like resistors and capacitors, diodes are two terminal devices
 - The 2 terminals are called **Anode** and **Cathode**
- It conducts current in one direction only (from anode to cathode)
- Unlike capacitors & inductors, current in diodes is directly related to voltage
 - But this **current** is **not linearly** related to voltage
- Diodes only consume power → They are said to be passive devices



Diodes are nonlinear, two terminal, passive electrical devices

Load-Line Analysis of Diode Circuits

Example: Find the diode voltage & current at the operating point for the following cases:

- $V_{SS} = 2 \text{ V}$ and $R = 1 \text{ k}\Omega$

- $V_{SS} = 10 \text{ V}$ and $R = 10 \text{ k}\Omega$

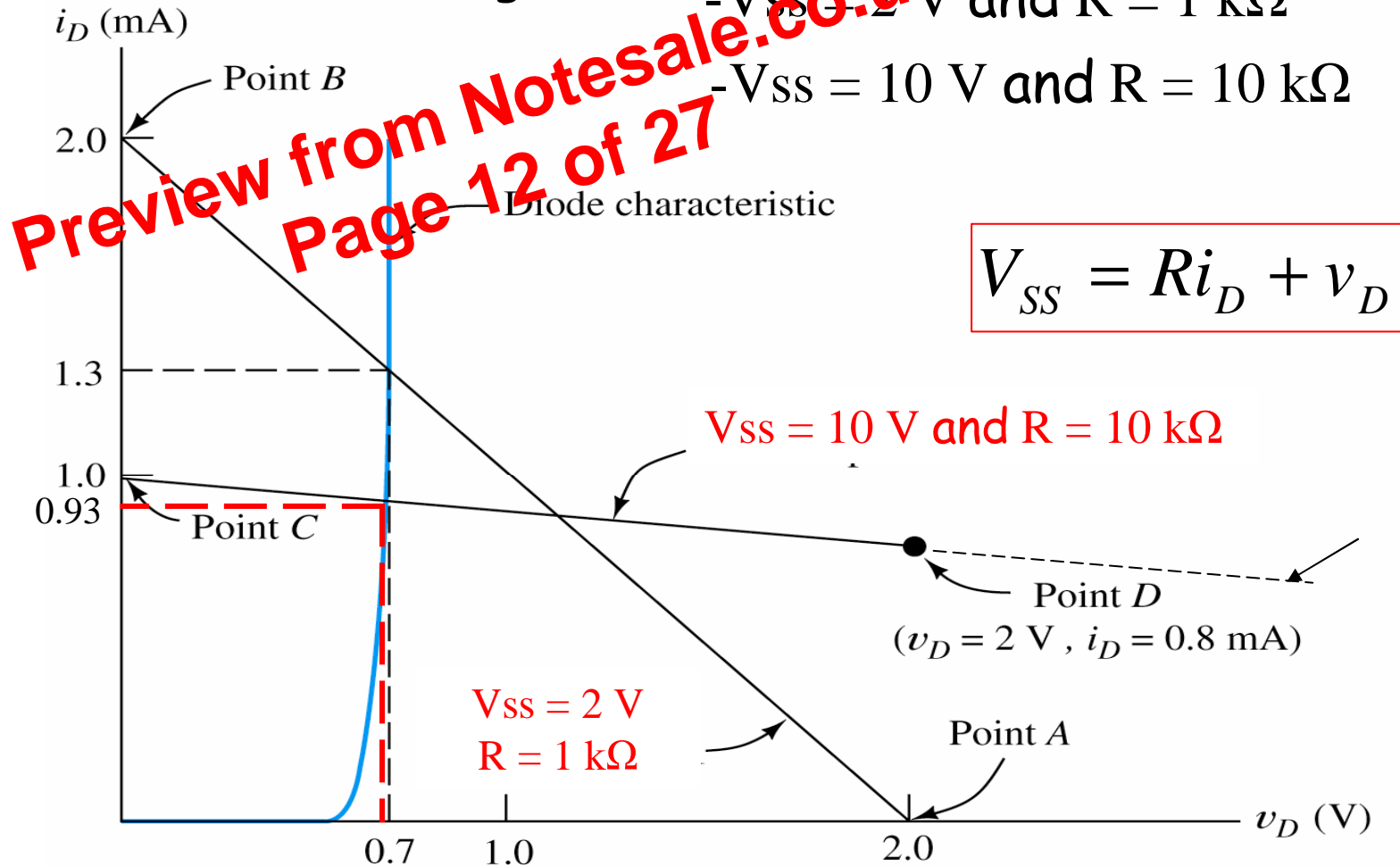


Figure 10.7 Load-line analysis for Examples 10.1 and 10.2.



Peak Inverse Voltage (PIV)

- The maximum voltage that will appear across the diode when it is off.
- The specification of the diode should be greater in magnitude than PIV so it is not damaged.

- For half-Wave rectifier:




$$PIV = V_m$$

- For half-Wave rectifier with capacitor:

$$PIV = 2V_m$$



Clipper Circuits

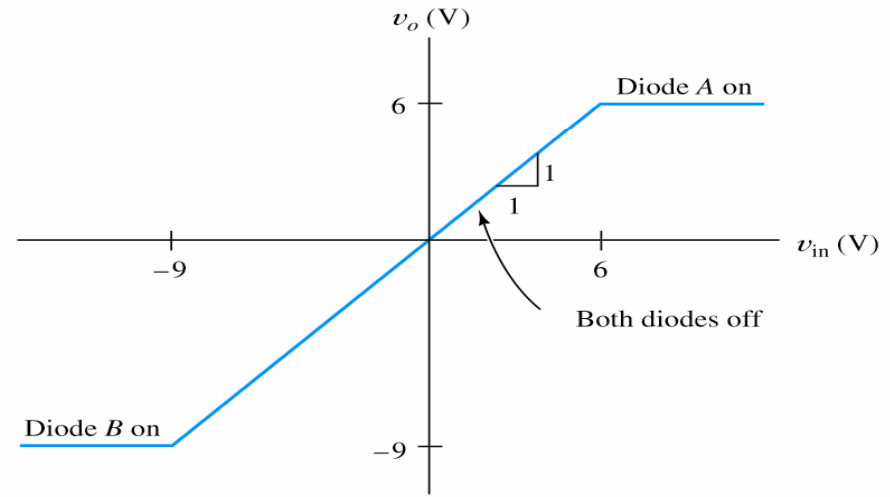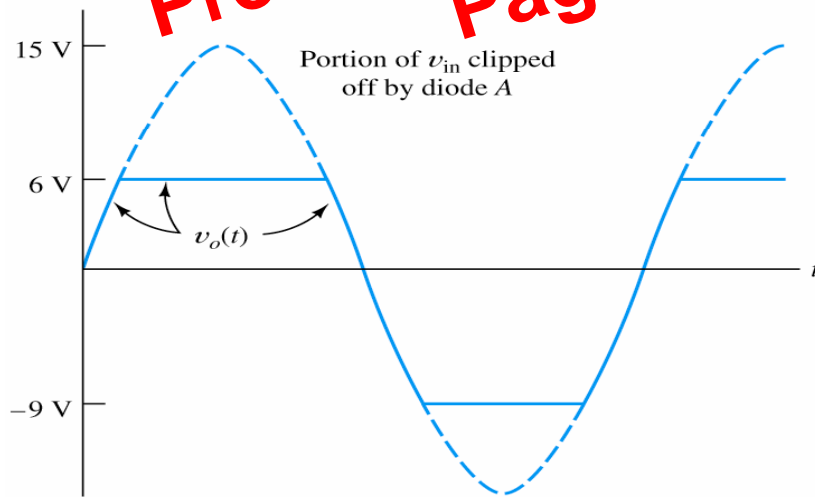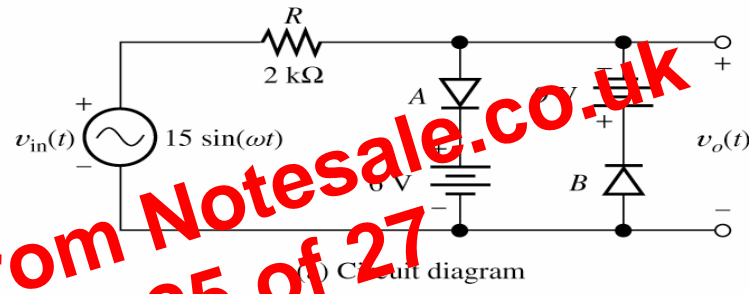

Clipper circuit.

R is large to limit the current but small to prevent the reverse current from causing a large voltage drop

