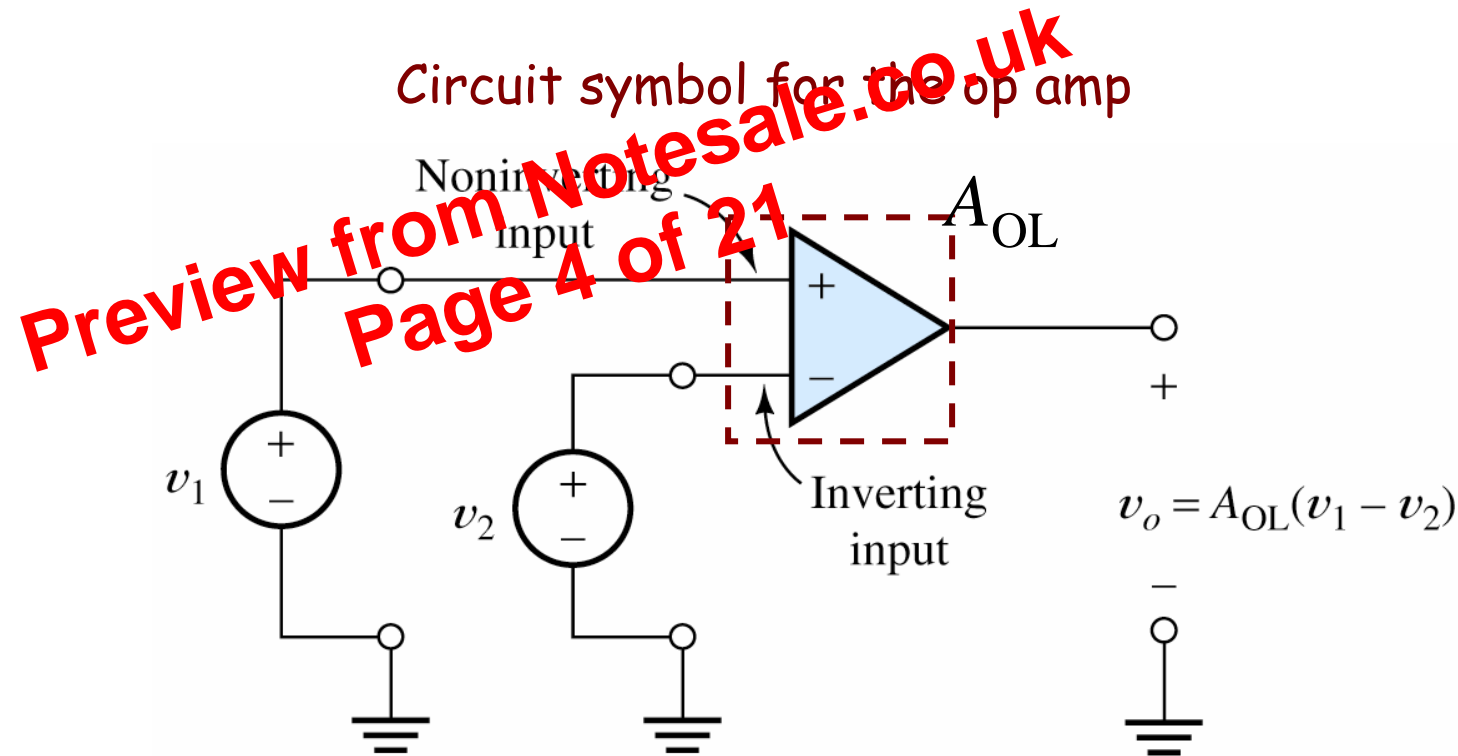



Ideal Operational Amplifiers



A_{OL} is the gain of the op amp without a feedback network
(OL \rightarrow open-loop gain)

Power-Supply Connections

Preview from Notesale.co.uk
Page 7 of 21

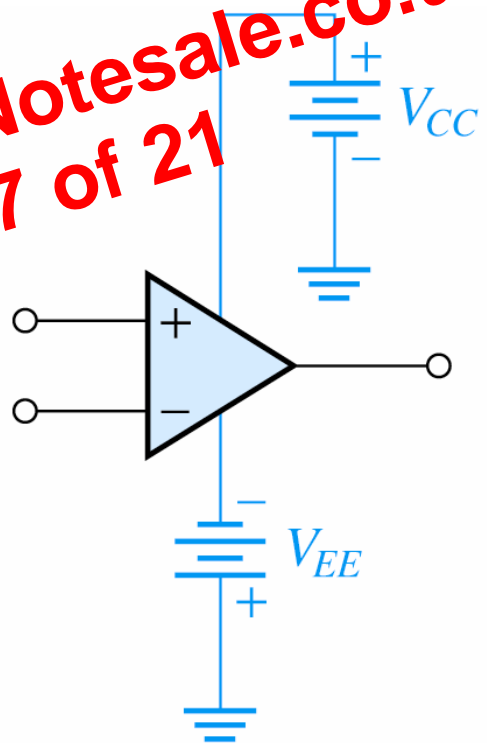


Op-amp symbol showing the dc power supplies, V_{CC} and V_{EE} .



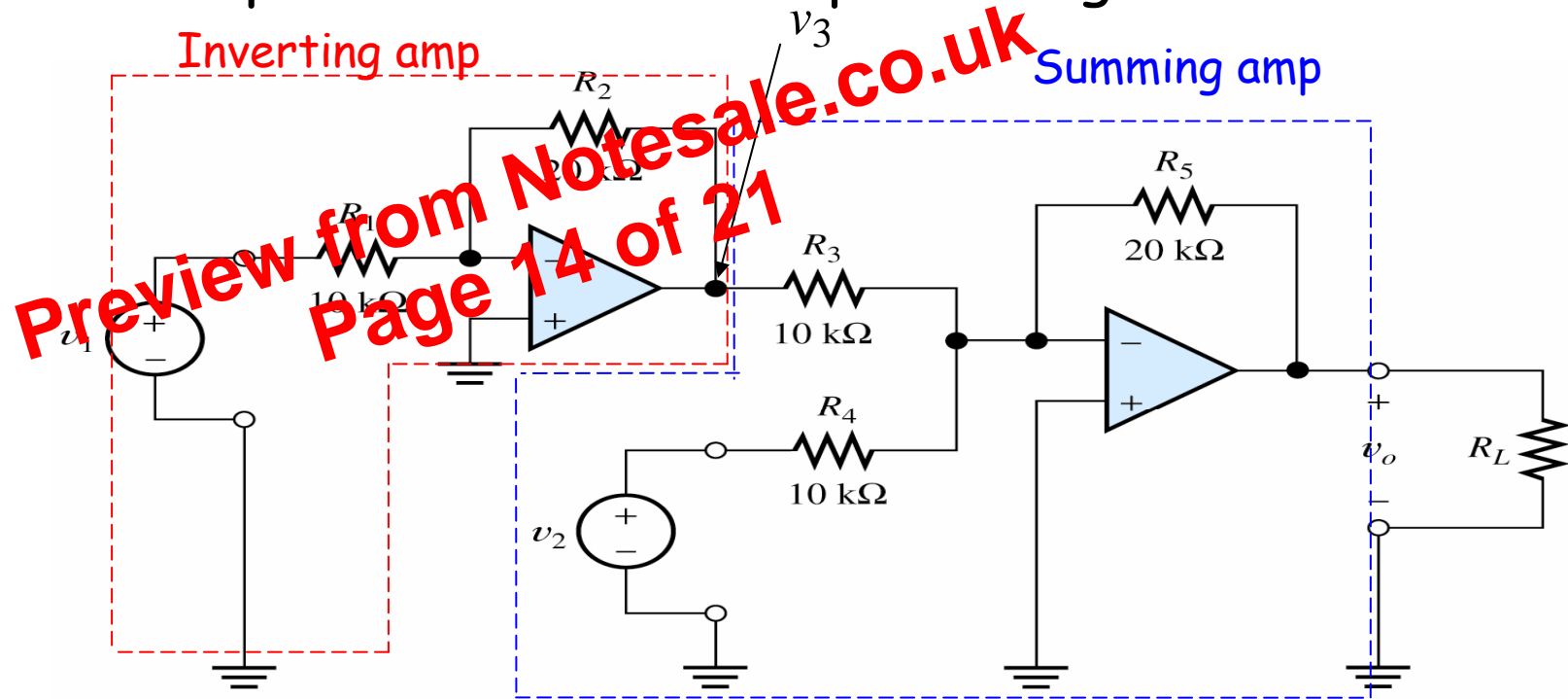Example

Find the expression for the output voltage



$$v_3 = -\frac{R_2}{R_1} v_1 = -\frac{20\text{k}}{10\text{k}} v_1 = -2v_1$$

$$\begin{aligned} v_o &= -\frac{R_5}{R_3} v_3 - \frac{R_5}{R_4} v_2 \\ &= -2v_3 - 2v_2 = 4v_1 - 2v_2 \end{aligned}$$