

Introduction

- A Bipolar Junction Transistor (BJT) is a three-terminal device
- It is constructed as layers of semiconductor materials (usually silicon)
- It is used in amplifiers and logic circuits
- BJTs are capable of producing large output currents


Preview from Notesale.co.uk
Page 3 of 24




NPN Bipolar Junction Transistors (BJT)

- A layer of p-type material between two layers on n-type material
- Each PN junction forms a diode, but current in one junction affects the other
- Three layers are called:
 - Emitter
 - Base
 - Collector
- With the voltages applied, a small current from the base causes much larger currents to flow from the collector to the emitter

preview from Notesale.co.uk
Page 4 of 24

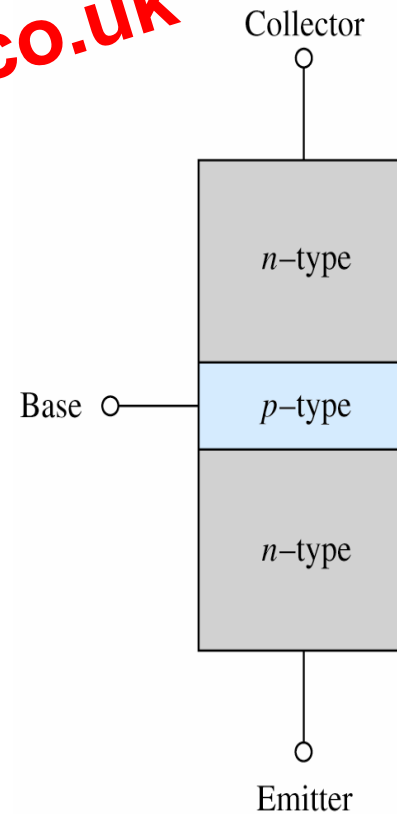

(a) Physical structure

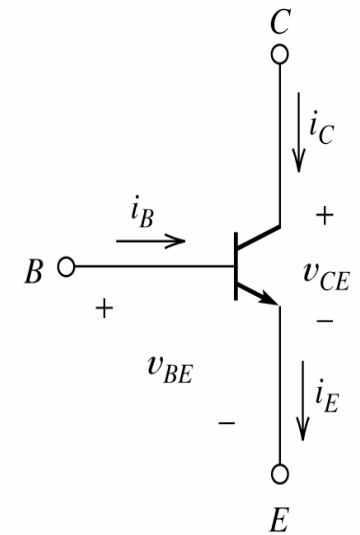



(b) Circuit symbol

The *npn* BJT.





Analysis of the Four-Resistor Bias Circuit

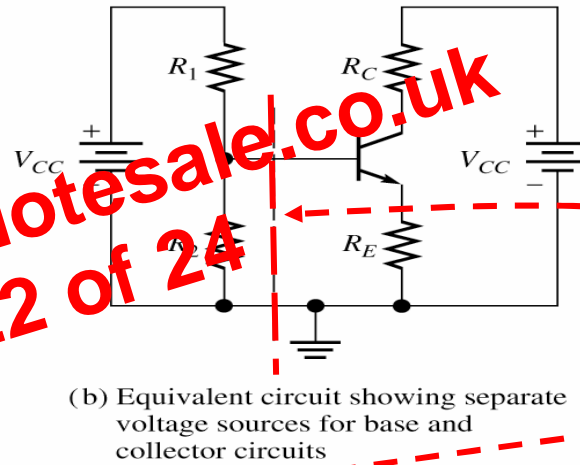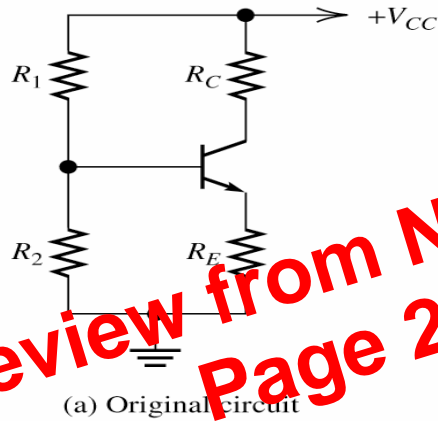Preview from Notesale.co.uk
Page 22 of 24



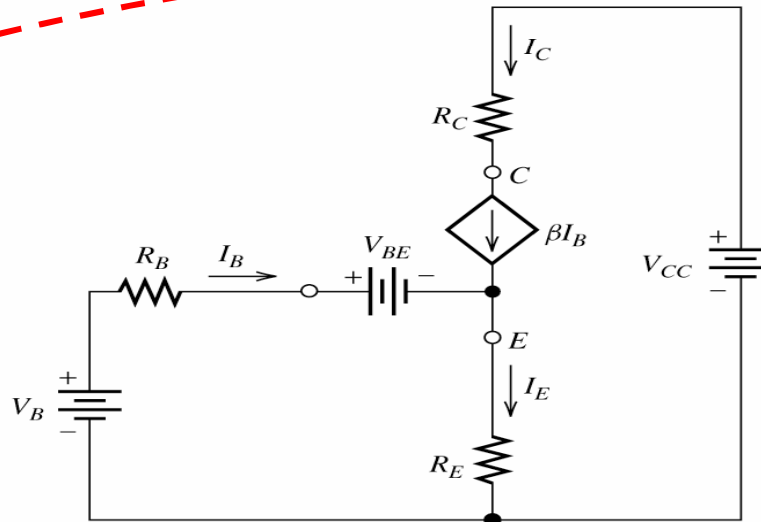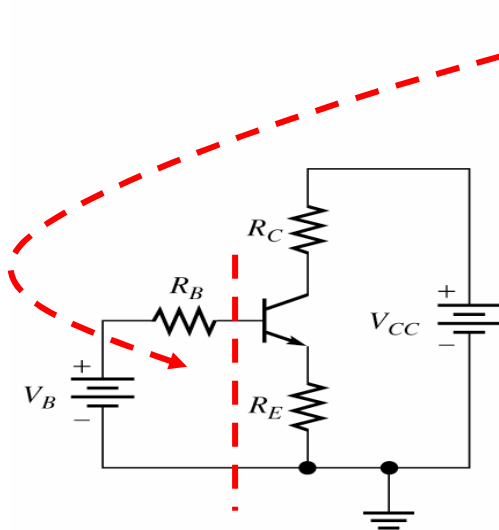R_B – Thevenin resistance
 V_B – Thevenin voltage



Example

Find I_C and V_{CE} for $\beta = 100$ and $\beta = 300$. Assume $V_{BE} = 0.7 \text{ V}$.

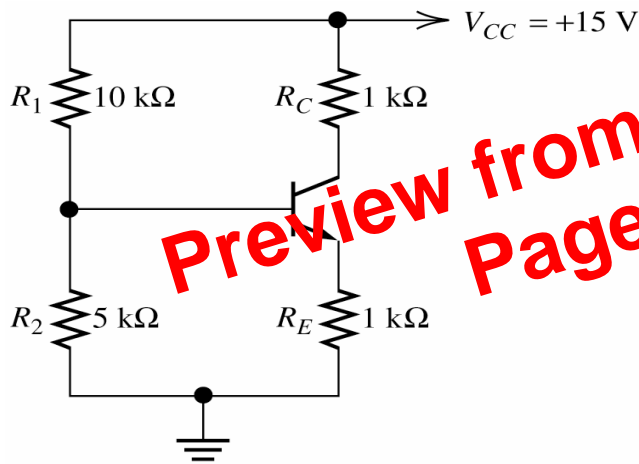


Figure 13.23 Circuit for Example 13.7.

Preview from Notesale.co.uk
Page 24 of 24

$$V_B = V_{CC} \frac{R_2}{R_1 + R_2} = 5\text{V}$$

$$R_B = \frac{1}{1/R_1 + 1/R_2} = R_1 \parallel R_2 = 3.33\text{k}\Omega$$

$$I_B = \frac{V_B - V_{BE}}{R_B + (\beta + 1)R_E} = 41.2\mu\text{A}$$

$$\text{For } \beta = 100, I_C = \beta I_B = 4.12\text{mA}$$

$$V_{CE} = V_{CC} - R_C I_C - R_E I_E = 6.72\text{V}$$

For $\beta = 300$, $I_B = 14.1 \mu\text{A}$, $I_C = 4.24 \text{ mA}$, and $V_{CE} = 6.51 \text{ V}$

This configuration has a Q-point almost independent of β