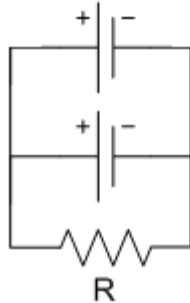


Example 2

Two cells with e.m.f 1.5 V for each cell and internal resistance 0.2Ω are joined in parallel and connected to an external resistor of 4Ω . What is current will flow.

Solution:



$$\text{Total e.m.f, } E = 1.5\text{V}$$

$$\text{Total internal resistance} = r/m = 0.2/2 = 0.1\Omega$$

$$\begin{aligned} \text{Total resistance, } R_T &= r/m + R \\ &= 0.1 + 4 \\ &= 4.1\Omega \end{aligned}$$


$$\begin{aligned} \text{Current, } I &= \frac{\text{total emf}}{\text{total resistance}} \\ &= \frac{E}{r/m + R} \\ &= \frac{1.5}{4.1} \\ &= 0.366\text{A} \end{aligned}$$

Example 3

Eight cells are divided in two groups. Four cells for each group and the group are joined in parallel. Emf for each cell is 1.5V and internal resistance is 0.6Ω . One external resistor 5Ω connected in parallel to the group. Calculate:

- Current flow
- Voltage drop for internal resistor
- The potential difference at the battery terminals

Solution:

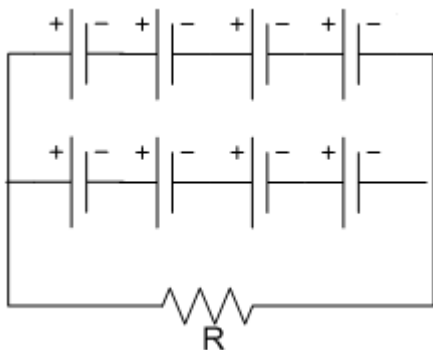

$$\text{a) } I = \frac{nE(V)}{\frac{nr}{m} + R(\Omega)} \text{ (A)} = \frac{4(1.5)}{\frac{4(0.6)}{2} + 5} = 0.968\text{A}$$

$$\text{b) } V_r = I \times \frac{nr}{m} = 0.968 \times \frac{4(0.6)}{2} = 1.16\text{V}$$

$$\begin{aligned} \text{c) Voltage source, } V_s &= nE - V_r \\ &= 4(1.5) - 1.16\text{V} \\ &= 4.84\text{V} \end{aligned}$$

@

$$V_s = IR_L = 0.968 \times 5 = 4.84\text{V}$$