

Combinational Logic Functions

- Data Selectors

- Multiplexers (Data Selectors)
- Demultiplexers

- Others

- Comparators
- Parity Generators / Checkers

Preview from Notesale.co.uk
Page 4 of 47

WEEK

8


Preview from Notesale.co.uk
Page 5 of 47

EMT 125/3

DIGITAL ELECTRONIC PRINCIPLES

COMBINATIONAL LOGIC FUNCTIONS

CONVERTERS (Encoder)

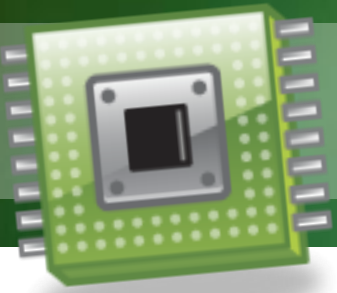

Exercise



Preview from Notesale.co.uk
Page 20 of 47

- Construct a 16-to-4-line Encoder


Decoders

Preview from Notesale.co.uk
Page 22 of 47

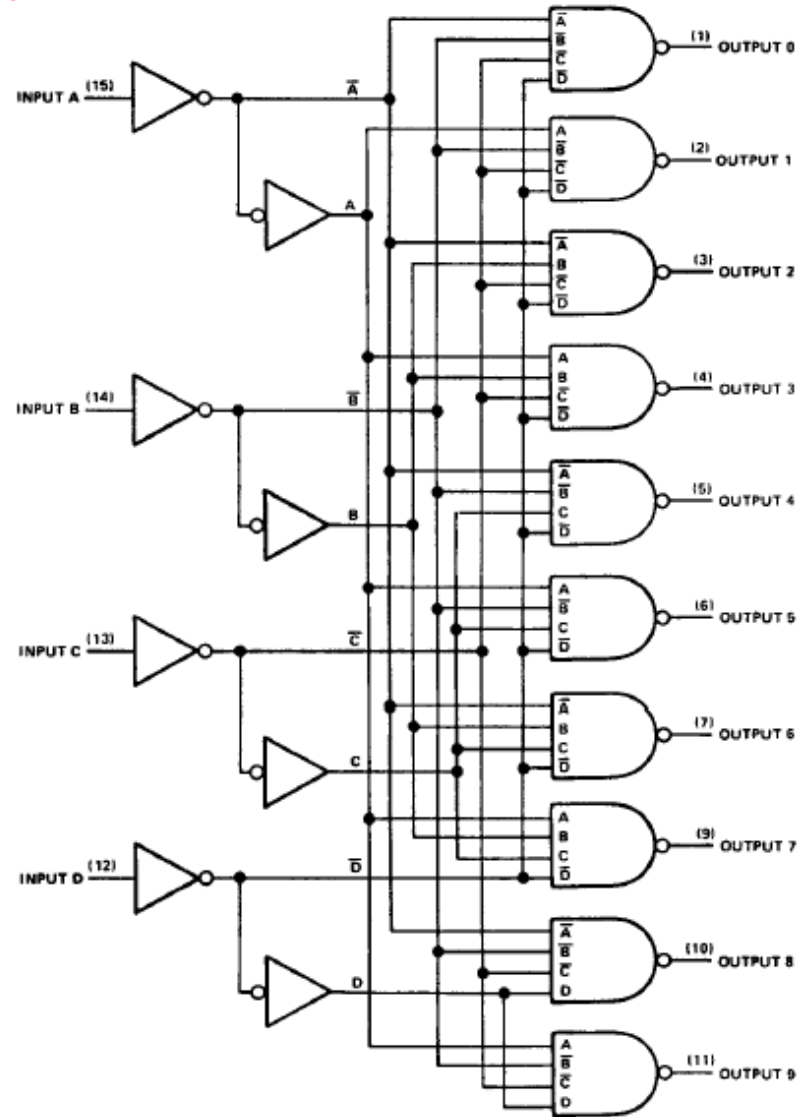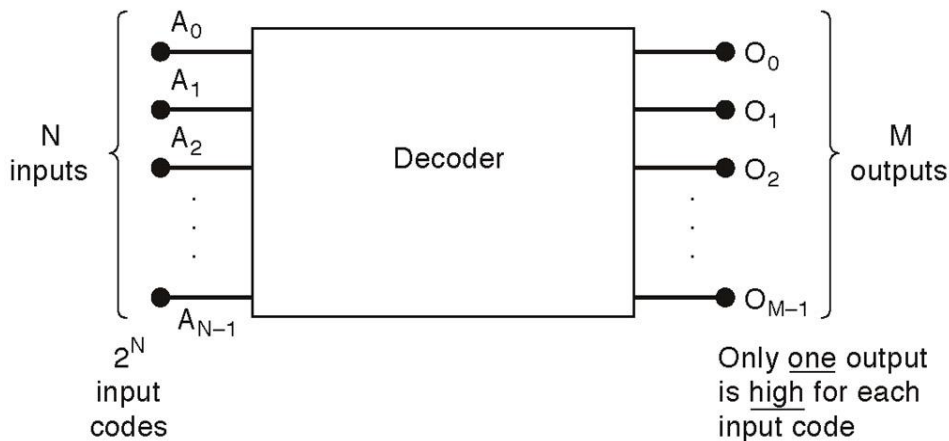- A decoder is a circuit that creates an output based on the binary states of a given input
- Selects one of several output lines, based on a coded input signal.
- Do the opposite of encoder




Decoders

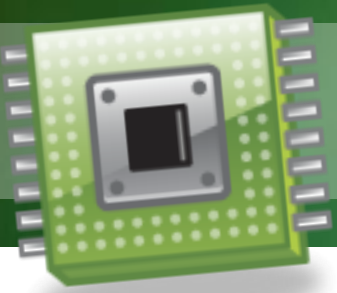

- Decoders come in two varieties:
 - active high
 - active low

- We focus our lectures on **active high decoders**:
 - the selected output goes to logic 1
 - the outputs not selected stay at logic 0.

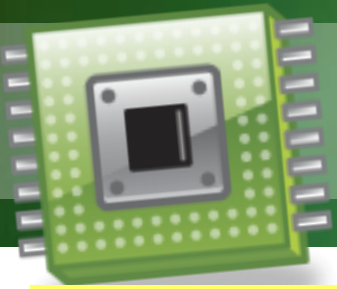Preview from Notesale.co.uk
Page 24 of 47





Decoder

Basic Binary Decoder

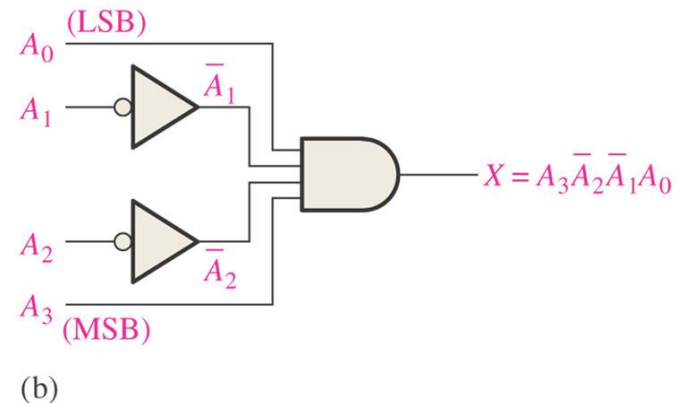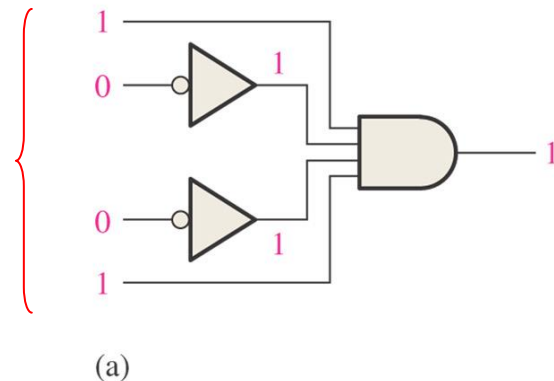
Example:

- To determine when a binary 1001 occurs on the input of a digital circuit, **AND gate** can be used as the **basic decoding element**.
- AND gate -> produce HIGH output when all inputs are HIGH
- How to ensure that inputs to the AND gate are HIGH when binary 1001 occurs?

Other than this input combinations, the output is 0




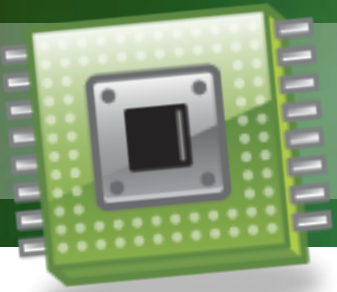Decoding logic for the binary code 1001 with an **active-HIGH output**.



Design Example

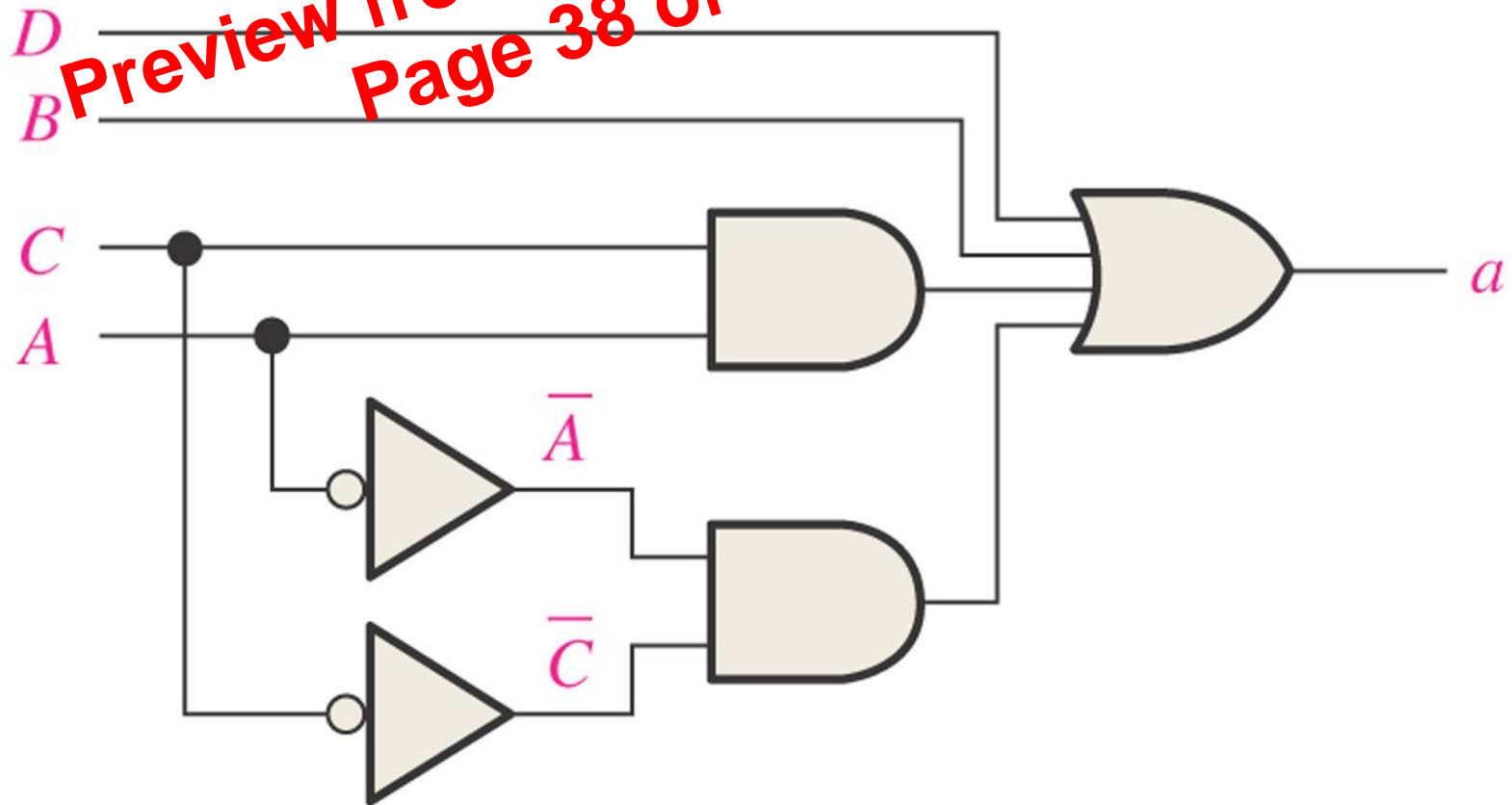Preview from Notesale.co.uk
Page 38 of 47



The minimum logic implementation for segment a of the 7-segment display