

Edge-Triggered S-R Flip-flop


- The **S and R input** of the S-R latch are called **synchronous inputs** as data on these inputs are transferred to the flip-flop's output only on the triggering edge of the clock pulse.

| INPUTS | | | OUTPUTS | | COMMENTS |
|--------|---|-----|----------------|-----------------|-----------|
| S | R | CLK | Q | Q' | |
| 0 | 0 | X | Q ₀ | Q' ₀ | No Change |
| 0 | 1 | ↑ | 0 | 1 | RESET |
| 1 | 0 | ↑ | 1 | 0 | SET |
| 1 | 1 | ↑ | ? | ? | Invalid |


Function table

Edge-Triggered S-R Flip-flop

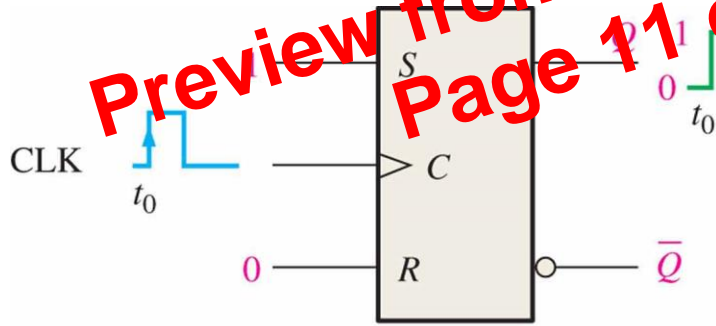
Basic Operation of Positive Edge-Triggered S-R Flip-flop



 
(a) $S = 1, R = 0$ flip-flop SETS on positive clock edge. (If already SET, it remains SET.)



 (b) $S = 0, R = 1$ flip-flop RESETS on positive clock edge. (If already RESET, it remains RESET.)



 (c) $S = 0, R = 0$ flip-flop does not change. (If SET, it remains SET; if RESET, it remains RESET.)




Edge-Triggered S-R Flip-flop

REMEMBER

Preview from Notesale.co.uk
Page 12 of 34

 
- Flip-flop cannot change state except on the triggering edge of a clock.
- The S-R inputs can be changed at any time when the clock input is LOW or HIGH (*except for a very short interval around the triggering transition of the clock*) without affecting the output.



Edge-Triggered D Flip-flop

 Example 2:

Given the waveform for D input and the clock, determine the Q output waveform if the FF starts in RESET.



Exercises

Preview from Notesale.co.uk
Page 34 of 34

- For a positive edge triggered J-K flip-flop with inputs shown, determine the output. Assume that Q starts low.

