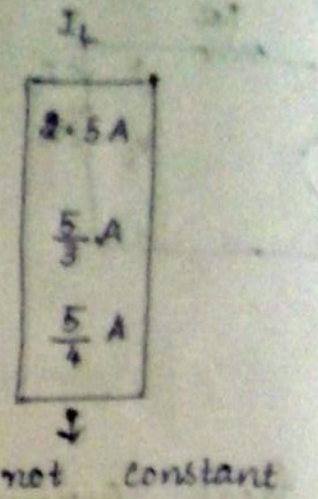


R	V_L
1Ω	$2.5V$
2Ω	$\frac{10}{3}V$
3Ω	$\frac{15}{4}V$



③ Dependent Sources

A source whose v_{tg} / current depends on other circuit parameters

Dependent V_{tg} Sources





Dependent Current Sources

a) VCVS

b) CCVS

c) VCCS

d) CCCS

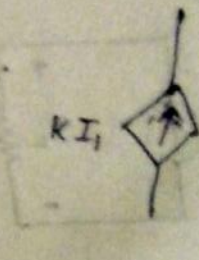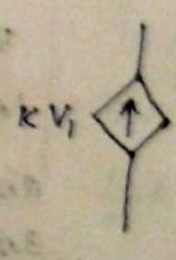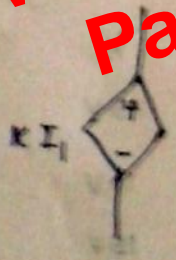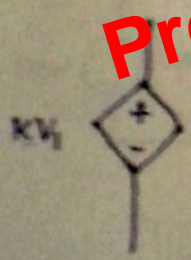

Dependent source is linear w.r.t the control variable.

#3 KIRCHHOFF'S LAWS

1) Kirchhoff's Current Law (KCL):

Algebraic sum of currents at a

node = 0

a) For a resistor:

$$I_{R1} = I \left[\frac{R_2}{R_1 + R_2} \right]$$

$$I_{R2} = I \left[\frac{R_1}{R_1 + R_2} \right]$$

b) For an inductor:

$$I_{L1} = I \left[\frac{L_2}{L_1 + L_2} \right]$$

$$I_{L2} = I \left[\frac{L_1}{L_1 + L_2} \right]$$

c) For a capacitor:

$$I_{C1} = I \left[\frac{C_2}{C_1 + C_2} \right]$$

$$I_{C2} = I \left[\frac{C_1}{C_1 + C_2} \right]$$



#5 SOURCE TRANSFORMATIONS

Source transformation can be performed only on practical v_s/i_s sources.


Do not perform source transformation on ideal current/voltage source.




source transformation

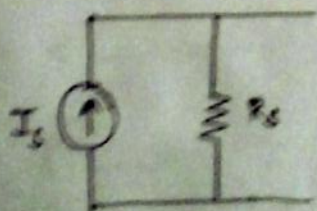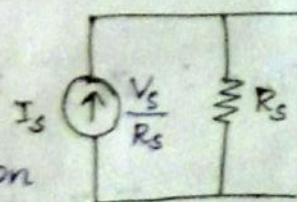


source transformation

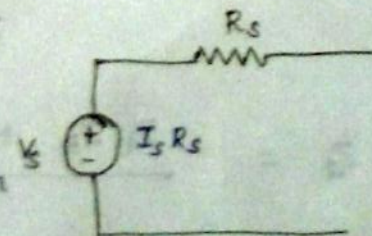

Example: Reduce the ckt b/w A and B

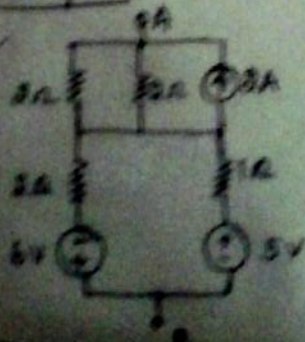

≡

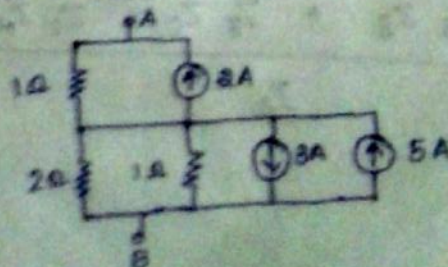

b) delta to star:

given : Z_1, Z_2, Z_3


To find : Z_A, Z_B, Z_C

$$Z_A = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3}$$

$$Z_B = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3}$$

$$Z_C = \frac{Z_2 Z_3}{Z_1 + Z_2 + Z_3}$$

Example : Find R_{AB}


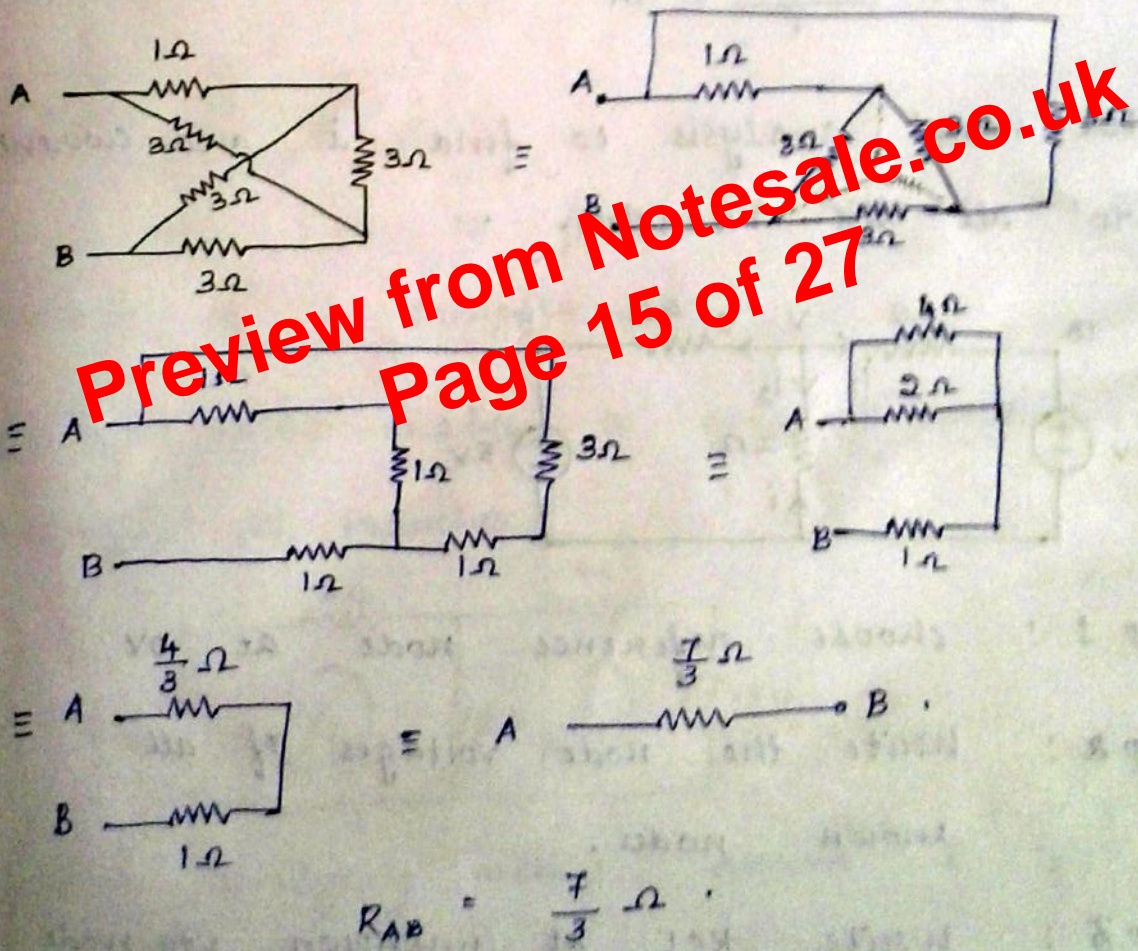


Preview from Notesale.co.uk
Page 15 of 27

#7 NODAL AND MESH ANALYSIS

a) Nodal analysis


uses KCL to find the response in any

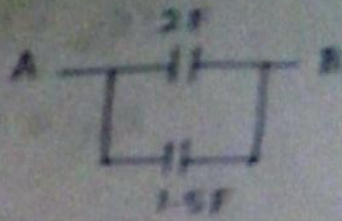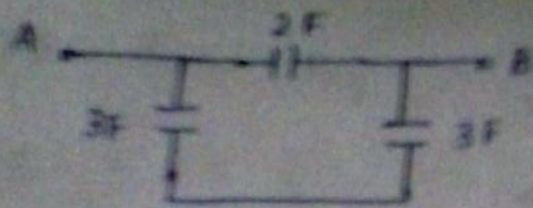

$$C_{AB} = 3.5 F$$

#7: Find i_L . Given $i_L = 3e^{-4t} + 4e^{-2t}$

$$i_L(0) = 1 A$$

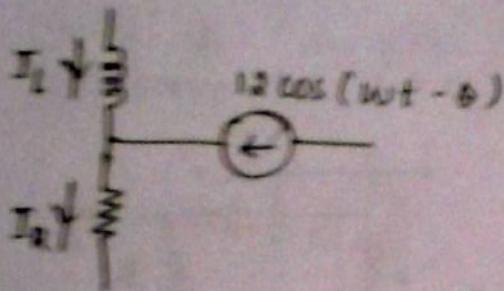

$$KCL: i_L + 12 \cos(\omega t - \theta) = 0$$


@ $t = 0$

$$12 \cos \theta = 1$$

$$12 \cos \theta = 6$$

$$\theta = \cos^{-1}\left(\frac{1}{2}\right) = 60^\circ$$

#8 Find i_x

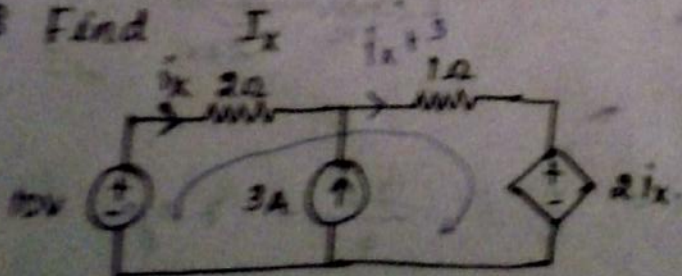

$$-10 + 2i_x + i_x + 3 + 2i_x = 0$$

$$5i_x = 7$$

$$i_x = \frac{7}{5} A$$

Preview from Notesale.co.uk
Page 24 of 27