

Q. $x = 1000111\underline{000}$ ←

2's complement of $x = 011100\underline{1000}$

Q. $x = 1011$

2's of $x = 0101$

Q. $11010_2 - 01110_2 = +(-01110)$

(i). $11010 + (1's \text{ of } 01110) = 11010 + 10001$

(ii). $11010 + (2's \text{ of } 01110)$

EOC ① $01011 \rightarrow +1$
 01100

$11010 = 10010$

EOC ignore 100

Q. $01110_2 - 11010_2 = + (2's \text{ of } 11010)$

$01110 = 00110$

NO EOC → $10100 \downarrow 2's$
 01100

$2^4 = 16$
 $16 - 2 = 14$

1's comp

2's comp

$16 - 1 = 15$

$+0 = 0000$

$+0 = 0000$

$-0 = 1's \text{ comp of } +0$

$-0 = 2's \text{ comp. of } +0$

$= 1's \text{ of } 0000$

$= 0000$

$= 1111$

(Disadv. of 1's complement)

* Range of numbers represented using 'n' bits

1's comp. form $\Rightarrow + (2^{n-1} - 1)$ to $- (2^{n-1} - 1)$

let $n=4 \Rightarrow +7$ to $-7 \rightarrow (14)$

2's comp. form $\Rightarrow + (2^{n-1} - 1)$ to -2^{n-1}

let $n=4 \Rightarrow +7$ to $-8 \rightarrow (15)$

Q. How many bits are required to represent -64_{10} in a). 1's comp. form b). 2's form

1's form $\Rightarrow + (2^{n-1} - 1)$ to $- (2^{n-1} - 1)$

let $n=7 \Rightarrow +63$ to -63

$\checkmark n=8 \Rightarrow +127$ to -127

2's form $\Rightarrow + (2^{n-1} - 1)$ to -2^{n-1}

$\checkmark$ let $n=7 \Rightarrow +63$ to -64

Q. 10's comp for $(731)_{10}$

$$\begin{array}{r} A A A \\ 7 3 1 \\ (-) \hline 3 7 9 \end{array}$$

Q. 9's comp of $(731)_{10}$


$$\begin{array}{r} 999 \\ (-) 731 \\ \hline 268 \end{array}$$

Binary Numbers:

(a). Unsigned Numbers $\rightarrow$

(b). Signed Numbers $\downarrow$ represented by

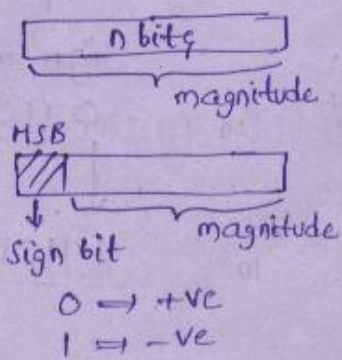- (i). sign magnitude
- (ii). 1's comp form
- (iii). 2's comp form



These three representations are same for unsigned (+ve numbers).

minterms & maxterms :

Let $f(A, B, C)$.

containing all variables

minterms

$$\begin{array}{l} \bar{A} \cdot \bar{B} \cdot \bar{C} \\ \bar{A} \cdot \bar{B} \cdot C \\ \bar{A} \cdot B \cdot \bar{C} \\ \vdots \\ A \cdot B \cdot \bar{C} \\ A \cdot B \cdot C \end{array}$$

maxterms

$$\begin{array}{l} \bar{A} + \bar{B} + \bar{C} \\ \bar{A} + \bar{B} + C \\ \bar{A} + B + \bar{C} \\ \vdots \\ A + B + \bar{C} \\ A + B + C \end{array}$$

* for 'n' var. function $\rightarrow 2^n$ minterms
 2^n maxterms

* Sum of all minterms = 1. $\sum_{i=0}^{2^n-1} m_i = 1$

* product of all maxterms = 0. $\prod_{i=0}^{2^n-1} M_i = 0$

* product of any two minterms = 0

Preview from Notesale.co.uk
 Page 17 of 98

$$\begin{aligned} m_i \cdot m_j &= 0, \text{ if } i \neq j \\ &= m_i, \text{ if } i = j \end{aligned}$$

* Sum of any two maxterms = 1.

$$\begin{aligned} M_i + M_j &= 1, \text{ if } i \neq j \\ &= M_i, \text{ if } i = j. \end{aligned}$$

Let $f(x, y)$

$1 = \text{var}$
 $0 = \overline{\text{var}}$

$1 = \overline{\text{var}}$
 $0 = \text{var}$

x y

minterm

max term

0 0

$\bar{x} \cdot \bar{y}$ m_0

$x + y$ M_0

0 1

$\bar{x} \cdot y$ m_1

$x + \bar{y}$ M_1

1 0

$x \cdot \bar{y}$ m_2

$\bar{x} + y$ M_2

1 1

$x \cdot y$ m_3

$\bar{x} + \bar{y}$ M_3

$$f = \sum m(2, 4)$$


$$\text{Similarly } f_3 = f_1 - f_2 \Rightarrow f_3 = ?$$

$$f_3 = \sum m(0, 7).$$

$$f_4 = f_2 - f_1 \Rightarrow f_4 = ?$$

$$f_4 = \sum m(1, 6).$$

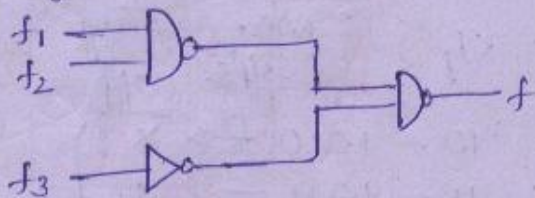Q. Determine the function f_3 in the following logic ckt.



$$\text{where } f = \sum m(0, 1, 3, 5)$$

$$f_1 = \sum m(2, 3, 6, 7)$$

$$f_2 = \sum m(0, 1, 5).$$

$$f = \overline{f_1 f_2 f_3}$$

$$= f_1 f_2 + f_3$$

$$\Rightarrow f_3 = f$$

$$f_1 f_2 = f$$

$$\Rightarrow f_3 = f = \sum m(0, 1, 3, 5).$$

Q. $f = f_1 \cdot f_2$ where $f_1 = \sum m(0, 1, 5) + d(2, 3, 7)$

$$f_2 = \sum m(1, 2, 4, 5) + d(0, 7).$$

$$f = f_1 \cdot f_2 = \sum m(1, 5)$$

$$+ d(0, 2, 7).$$

minterm in one fun. $\downarrow$ don't care in another fun. $\downarrow$

$$1 \cdot d = d$$


$$0 \cdot d = 0$$

$$1 + d = 1$$

$$0 + d = d$$

Two level logic :-
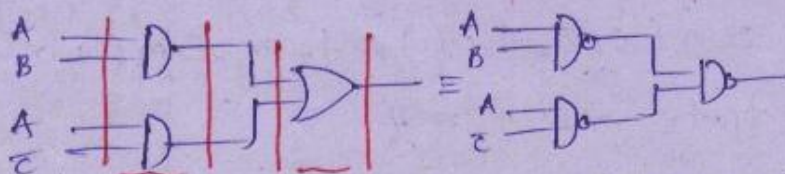
$$\text{SOP form} \rightarrow Y = AB + A\bar{C}$$




AND - OR logic $\equiv$ NAND - NAND

PRIORITY ENCODER: (74 LS 148)


D_7 - highest priority

D_0 - lowest priority

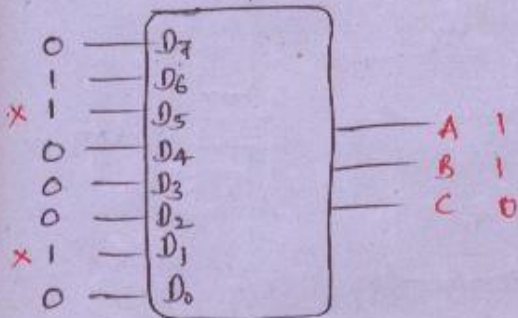

x - ignored

MULTIPLEXER:

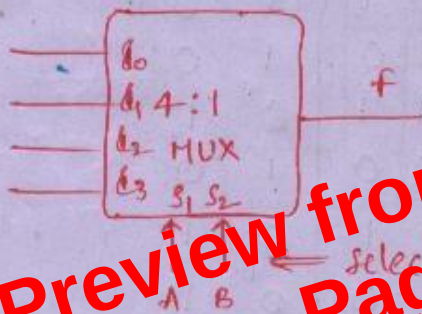


A	B	F
0	0	d_0
0	1	d_1
1	0	d_2
1	1	d_3

for 4:1 MUX,

$$f = \bar{A}\bar{B}d_0 + \bar{A}Bd_1 + A\bar{B}d_2 + ABd_3$$


$$= m_0d_0 + m_1d_1 + m_2d_2 + m_3d_3$$

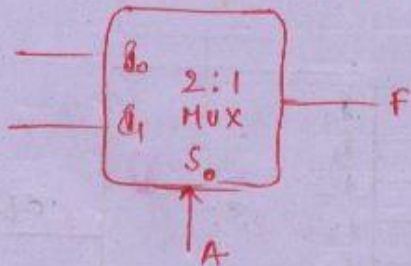

for 2:1 MUX,


$$f = \bar{A}d_0 + Ad_1$$

Q.

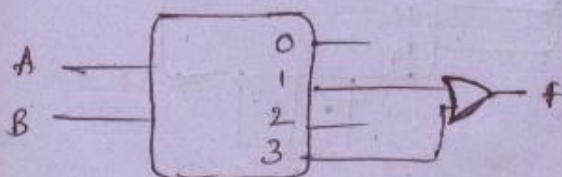

$$f(A, B) = \sum m(1, 3)$$

decoder

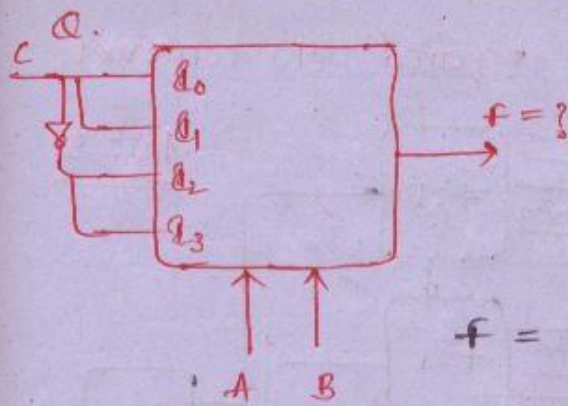

Given that

$$a_0 = a_1 = c$$

$$a_2 = a_3 = \bar{c}$$



$$f = \bar{A}\bar{B}c + \bar{A}Bc + A\bar{B}\bar{c} + AB\bar{c}$$

$$= \bar{A}c(\bar{B}+B) + A\bar{c}(\bar{B}+B)$$

$$= A \oplus c$$

Q. Determine the o/p's of the following Mux's?

1). Switching speed is 50 ns.

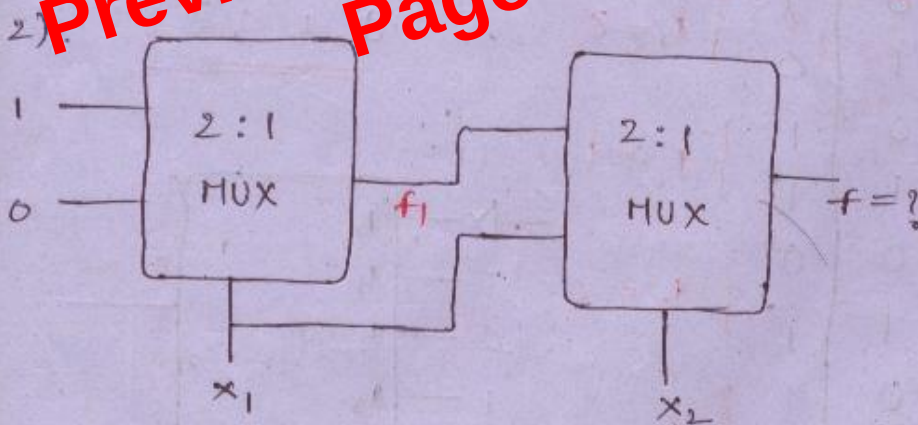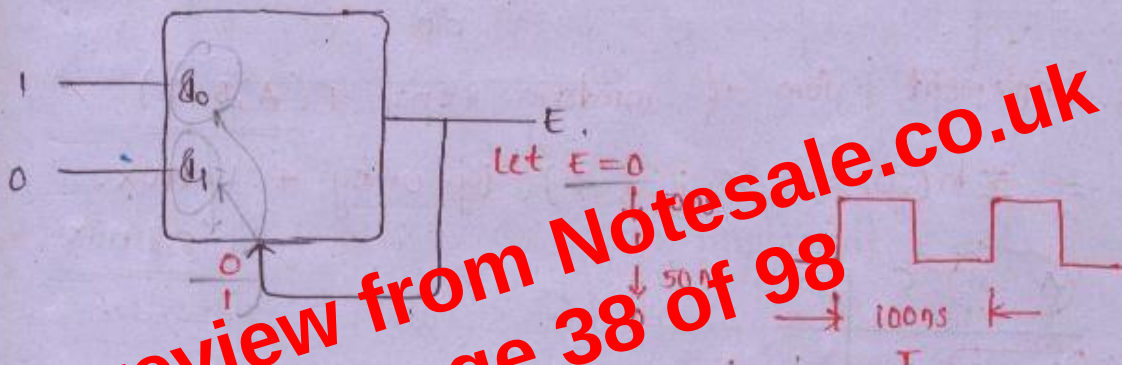

$$f_1 = \bar{A}a_0 + Aa_1$$

$$f_1 = \bar{x}_1 \cdot 1 + x_1 \cdot 0 = \bar{x}_1$$


$$f = \bar{A}a_0 + Aa_1$$

$$= \bar{x}_2 \cdot \bar{x}_1 + x_2 \cdot x_1$$

$$= x_2 \odot x_1$$


CHAR. TABLE:

J	K	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

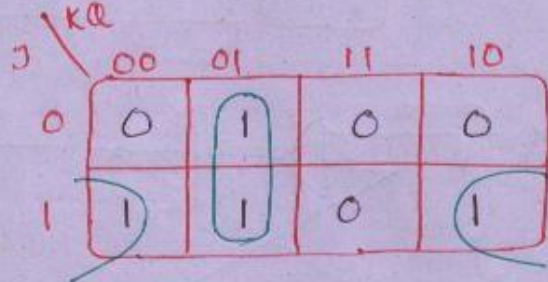

$$Q(t+1) = J\bar{Q} + KQ$$

CLOCKED T- FLIP FLOP:

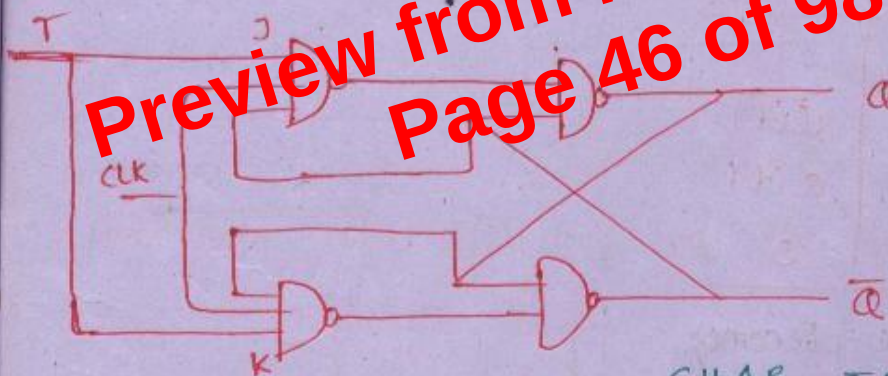

TRUTH TABLE :-

T	Q(t+1)
0	Q(t)
1	$\bar{Q}(t)$

J=K=0

← 0

J=K=1


← 1

CHAR. TABLE :-

T	Q(t)	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

$$Q(t+1) = T \oplus Q$$

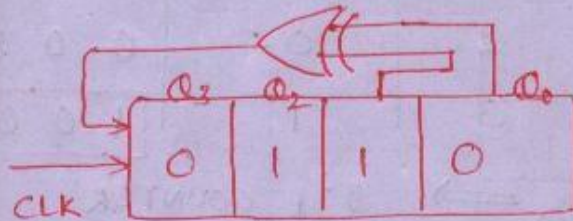Q. In the following shift reg. how many CLK's are required to make shift reg. content to have all one's.




CLK	Serial i/p ($Q_3 \oplus Q_0$)	Q_3	Q_2	Q_1	Q_0
0	—	0	1	1	0
1	1	1	0	1	1
2	0	0	1	0	1
3	1	1	0	1	0
4	1	1	1	0	1
5		1	1	1	0
		1	1	1	1

Preview from Notesale.co.uk
Page 52 of 98


APPLICATIONS OF SHIFT REG'S:

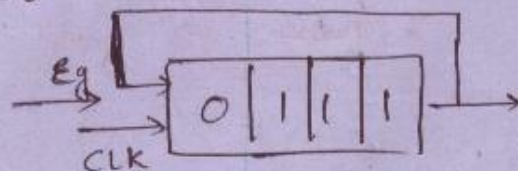- (1). Serial to parallel & parallel to serial conversion
- (2). Time delays - SISO
- (3). Sequence Generator
- (4). Counter
 - RING
 - JOHNSON.



... 011101110111.

RING COUNTER:

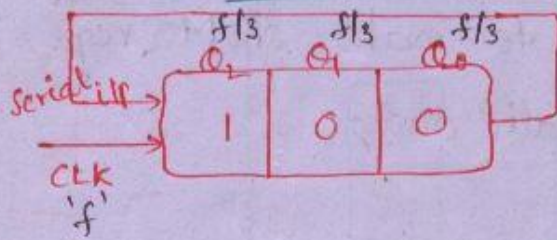


CLK	Serial i/p (Q ₀)	Q ₂	Q ₁	Q ₀
0	—	1	0	0
1	0	0	1	0
2	0	0	0	1
3	1	1	0	0

N-bit Ring Counter: $\Rightarrow$ 3:1 COUNTER

- Counting capacity = $N:1$
- Output frequency = f/N .

JOHNSON COUNTER: [TWISTED RING COUNTER]

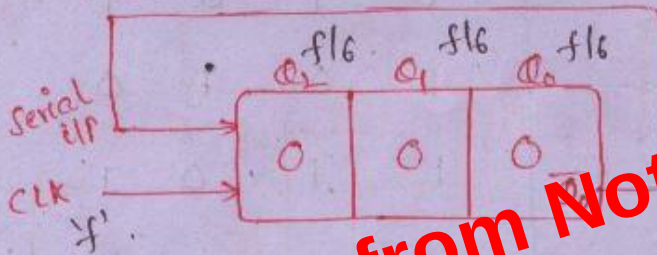

CLK	Serial i/p (Q ₀)	Q ₂	Q ₁	Q ₀
0	—	0	0	0
1	1	1	0	0
2	1	1	1	0
3	1	1	1	1
4	0	0	1	1
5	0	0	0	1
6	0	0	0	0

$\Rightarrow$ 6:1 COUNTER.

N-Bit Johnson Counter:

- Counting capacity = $2N:1$
- Output frequency = $f/2N$.

Preview from Notesale.co.uk
Page 53 of 98

Excitation Tables :


J K $Q(t+1)$

~~0 0~~ $Q(t)$

~~0 1~~ 0

1 0 1

1 1 $\overline{Q(t)}$

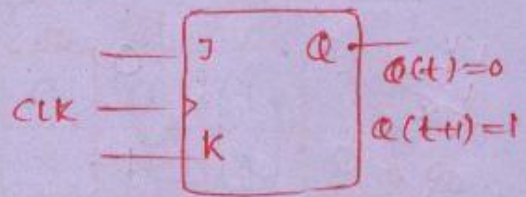


J K

1 0

1 1

1 x

S R f/f :

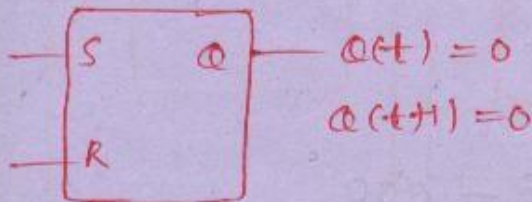

S R

0 1


0 0

$Q(t)$	$Q(t+1)$	J	K	S	R	D
0	0	0	x	0	0	0
0	1	1	x	1	0	1
1	0	x	1	0	1	0
1	1	x	0	x	0	1

Q. Obtain excitation table of x-y f/f:-


x	y	$Q(t+1)$
0	0	1
0	1	$\overline{Q(t)}$
1	0	$Q(t)$
1	1	0

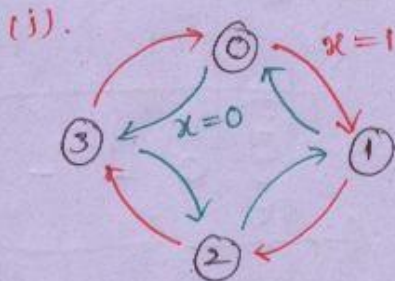Q. Draw the state diagram of following digital circuit (i.e. 2 bit syn. up/down counter).



(ii). JK - f/f

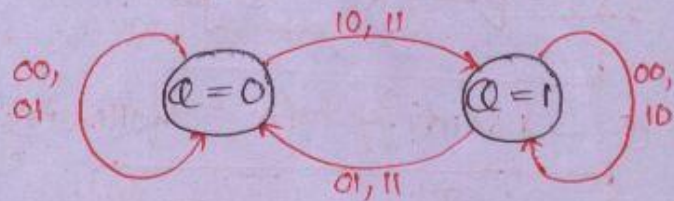present i/p { J → branches of each state.
k
P.S { Q → states




(iii). T - f/f

T → present i/p
Q → P.S.



Preview from Notesale.co.uk
Page 62 of 98

CONVERSION OF f/f's:

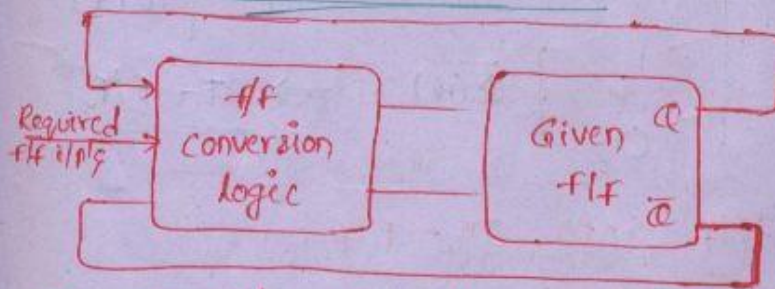

Q. Convert SR - f/f into T - f/f.

SR f/f → T - f/f
exci. table char. table

T	Q(t)	Q(t+1)	S	R
0	0	0	0	x
0	1	1	x	0
1	0	1	1	0
1	1	0	0	1


	0	1
0	0	x
1	1	0

$$S = T\bar{Q}$$


	0	1
0	x	0
1	0	1

$$R = TQ$$

$\Rightarrow T-f/f$

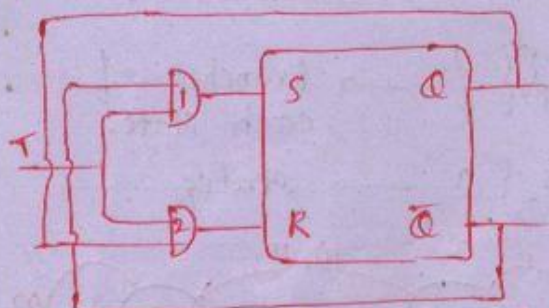

Q. Identify the following f/f.

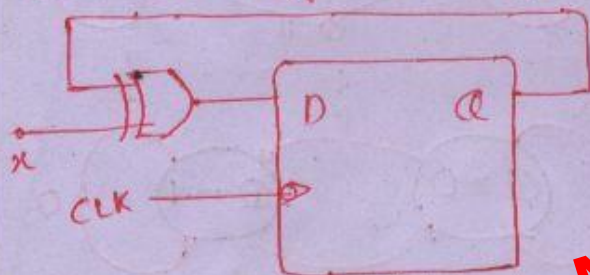


x	Q(t)	x ⊕ Q	Q(t+1)
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0


x	Q(t+1)
0	Q(t)
1	Q̄(t)

$\Rightarrow T-f/f$

Q. Convert D-f/f into JK-f/f.


Q2. Identify the following f/f.

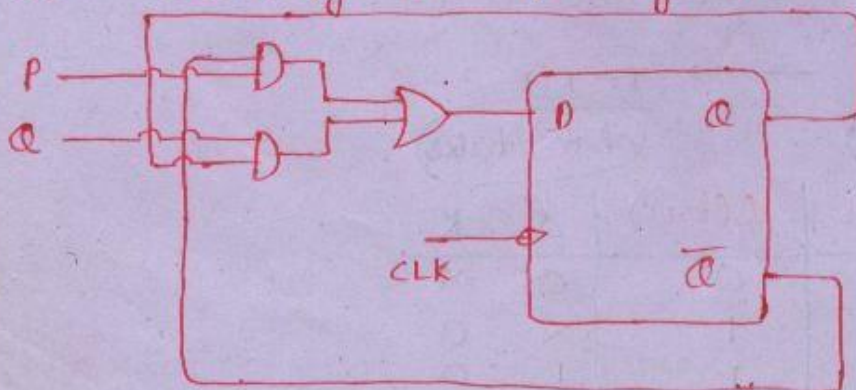

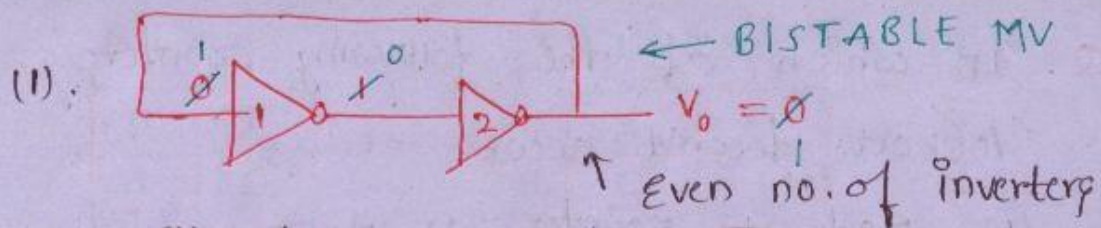


(2). flip flop

MONO STABLE :

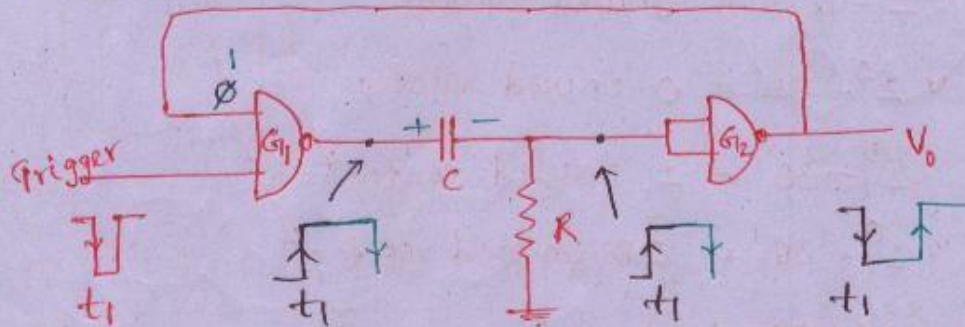

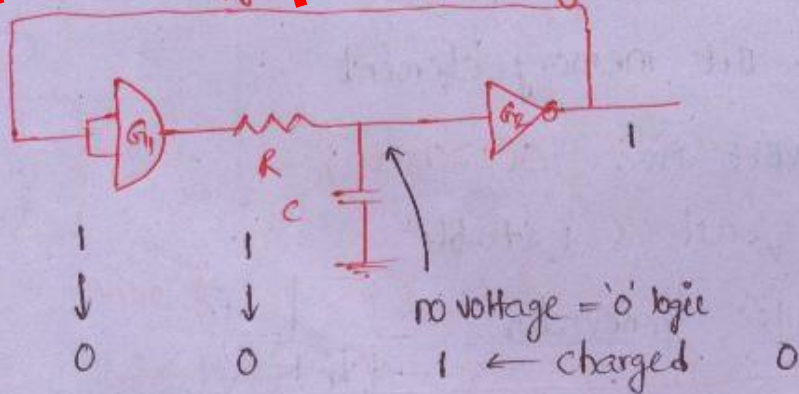
Preview from Notesale.co.uk
 Page 65 of 98




→ NO trigger ; Ans: ASTABLE MV.

$\begin{matrix} \text{EPROM} \\ \uparrow \end{matrix}$
 $\begin{matrix} 2716 \\ 8 \end{matrix} = 2 \text{ KB} \leftarrow \begin{matrix} \text{RAM} \\ \boxed{6116} \end{matrix}$
 $\begin{matrix} 2732 \\ 8 \end{matrix} = 4 \text{ KB} \leftarrow 6132$
 $\begin{matrix} 2764 \\ 8 \end{matrix} = 8 \text{ KB} \leftarrow 6164$
 $\begin{matrix} 27128 \\ 8 \end{matrix} = 16 \text{ KB} \leftarrow 61128$

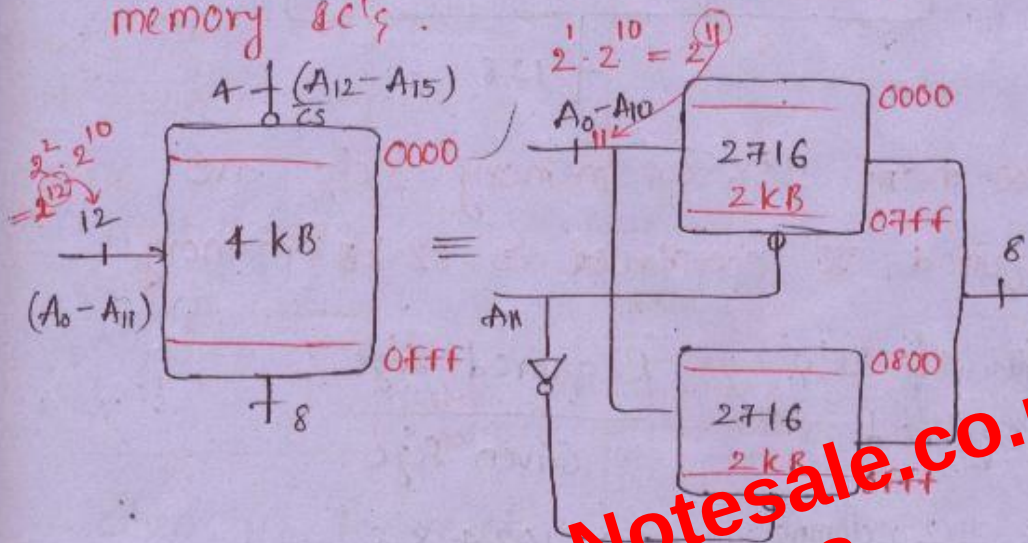Q. Construct a 4 KB memory using 2716 memory IC's.



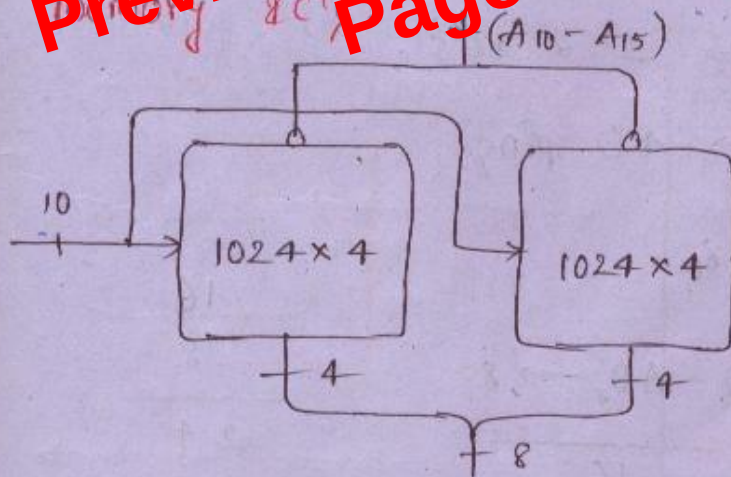Q. Construct a 1 KB memory using 1024 x 4 memory IC's.



$\frac{1 \text{ KB}}{1024 \times 8}$

Q. The add. lines of 64 memory IC having capacity of 256×2 are connected together. What is the size of resulting memory.

Instruction Operation Bytes/H/L/R Types of M/C flags affected

1). ADD ^{B, C, D, E, H, L, A.} R

$A + R \rightarrow A$

1/1/4

f

ALL

ADD M

$A + (HL) \rightarrow A$

1/2/7

f, R

ALL

ADD 8bit data

$A + (8bit\ data) \rightarrow A$

2/2/7

f, R

ALL

2). SUB R

SUB H

SUB 8bit data

3). ADC R

$Cy + A + R \rightarrow A$

1/1/4

ADC M

$Cy + A + (HL) \rightarrow A$

1/2/7

ADC 8bit data

$Cy^A + (8bit\ data) \rightarrow A$

2/2/7

4). SBB R

SBB M

$A - (HL) - Cy \rightarrow A$

1/2/7

SBB 8bit data

Preview from Notesale.co.uk
Page 92 of 98

ALL
except 'cy' flag

f

f

1/1/4

1/1/4

f, R, w

1/2/10

ALL
except 'cy' flag

f, R, w

1/2/10

S = opcode fetch m/c (GT)

B = Bus idle m/c (3T) No FLAGS

1/1/6

1/1/6

f, B, B

1/3/10

only 'cy' flag

ALL

but cy = 0

R+1 → R

R-1 → R

(HL)+1 → (HL)

(HL)-1 → (HL)

SP+1 → SP

SP-1 → SP

HL+SP → HL

5). INR R

DCR R

INR M

DCR M

INX SP

DCX SP

6). DAD SP

1). ORA R

ORA M

ORI 8bit data

A ← R

A ← (HL)

A ← 8bit data

Preview from Notesale.co.uk
Page 93 of 98

LOGICAL INSTRUCTIONS: