

2) Capacitive Reactance :- If capacitance offered the resistance in the path of A.C then it is known as Capacitive Reactance. It is denoted by X_C .


* Impedance :- Total resistance offered by inductance, resistance and capacitance is known as Impedance and it is denoted by Z .

$$Z = \frac{V}{I}$$

* Admittance :- Reciprocal of Impedance is known as Admittance. It is denoted by A .

$$A = \frac{1}{Z} \rightarrow \text{Impedance}$$

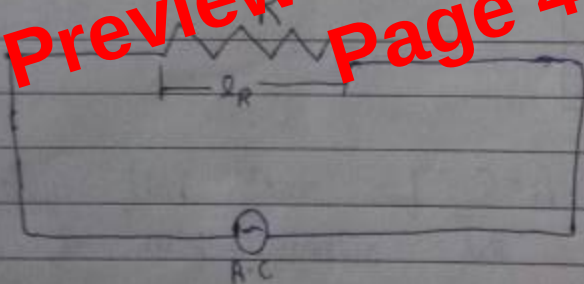* Different types of A.C circuit - Ohm's Circuit containing ohmic resistance :-




if $I = I_0 \sin \omega t$ A.C

Then Potential difference is

$$e = e_0 \sin \omega t \quad \angle = IR$$

Vector representation

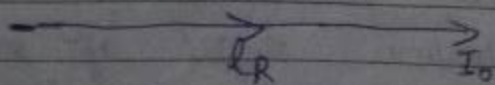

preview from Notesale.co.uk
page 4 of 20

$$F_0 = \frac{1}{2\pi\sqrt{LC}}$$


$$\text{or } \omega_0 = \frac{1}{\sqrt{LC}}$$

* Quality or Q-Factor :- The ratio of resonant frequency to the bandwidth is known as Q-factor.

Sharpness of Resonance is measured by unit less and dimensionless quality factor

$$Q = \frac{\omega_0}{2\Delta\omega}$$

$$\frac{Z}{\text{max (series)}}$$

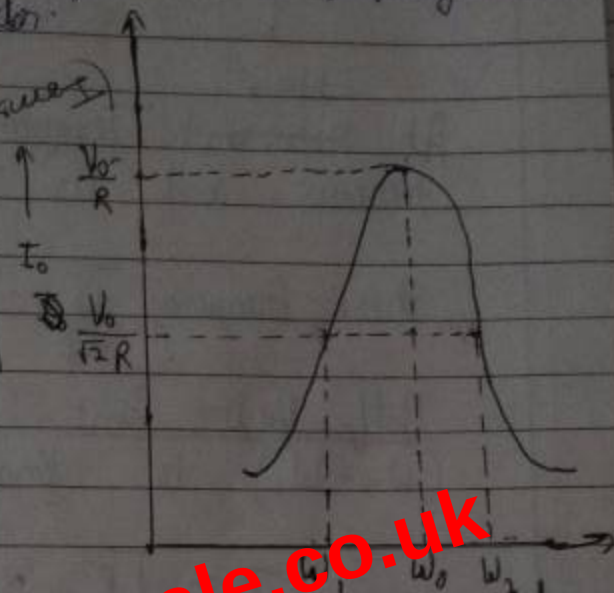

$\omega_0 \rightarrow$ Resonant frequency
 $\Delta\omega \rightarrow$ bandwidth

Experiment :-

Impedance of L-R Circuit

$$Z = \sqrt{R^2 + X^2}$$

$$X^2 = (X_L - X_C)^2$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

At resonant condition

$$X_L = X_C$$

$$\text{So } Z = R$$

and Resonant current $I_0 = \frac{V_0}{R}$

$$X_L = \omega L, \quad X_C = \frac{1}{\omega C}$$

$Q = \frac{\text{Voltage across inductor}}{\text{Voltage in resonance}}$

$$Q = \frac{V_L}{V_{\text{res.}}} = \frac{I \cdot X_L}{I \cdot Z_{\text{min.}}}$$

$$Q = \frac{X_L}{R} \quad [Z_{\text{min.}} = R]$$

$$Q = \frac{\omega_0 L}{R}$$

$Q = \frac{\text{Voltage across capacitor}}{\text{Voltage in resonance}}$

$$Q = \frac{V_C}{V_{\text{res.}}} = \frac{I \cdot X_C}{I \cdot Z_{\text{min.}}}$$

$$Q = \frac{1}{\omega_0 C R} \quad [Z_{\text{min.}} = R]$$

$$Q = \frac{\sqrt{LC}}{CR}$$

$$Q = \frac{\sqrt{L}}{\sqrt{C} R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$(w_2 - w_1) [L + L] = 2R$$

$$(w_2 - w_1) = \frac{R}{L}$$

$$\theta - \text{factor} = \frac{w_0}{2\Delta w}$$

$$Q = \frac{w_0}{2(w_2 - w_1)}$$



$$Q = \frac{w_0 L}{2R}$$

$$w_2 = w_0 + \frac{w_2 - w_1}{2} = w_0 + \frac{R}{2L}$$


$$w_1 = w_0 - \frac{w_2 - w_1}{2} = w_0 - \frac{R}{2L}$$

$$w_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{1}{2\sqrt{LC} R}$$

$$Q = \frac{1}{2R} \cdot \frac{L}{C}$$

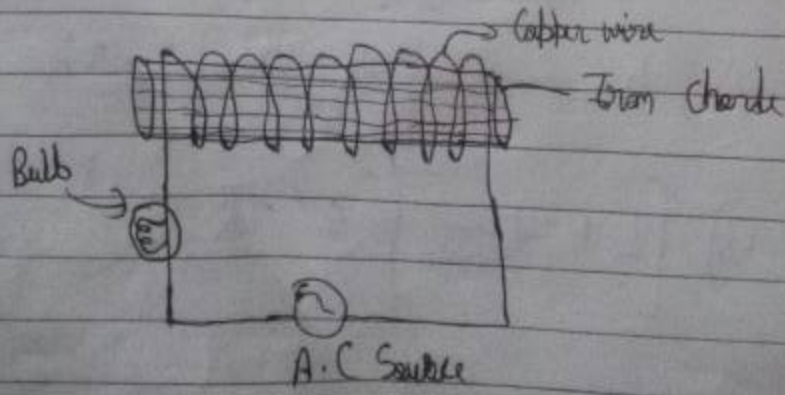* Choke coil :- It is a device which is used to control the current without power consumption.



→ Concept :-

When $\phi = \frac{\pi}{2}$

If ϕ is zero.

* Oscillat
Consider
When
Comm
Curren
So

By