

would be applied to the load on the secondary. This ~~may~~ high voltage may burnout or seriously damage the equipment connected the secondary side.

2. The effective per unit impedance of an autotransformer is smaller as compare to a two winding transformer. The reduced internal ~~resistance~~ ^{impedance} result in a large short ckt (fault) current.
3. In an autotransformer, there is a loss of isolation between input and output circuits.

APPLICATIONS OF AUTOTRANSFORMER

- 1- Autotransformer are used for starting induction motor and synchronous motors.
- 2- It is used for interconnection of power system of different voltage level example 132 kVA, and 230 kVA
- 3- It is used to obtain variable A.C. in laboratory

Volt-Ampere relation :-

- 1- Autotransformer has two types of volt ampere - namely -
 - ① The transformed volt ampere (due to induction)
 - ② Conducted volt - ampere - (due to direct electrical connections -)