

BINARY LOGIC AND GATES

- Binary variables take on one of two values.
- Logical operators operate on binary values and binary variables.
- Basic logical operators are the logic functions AND, OR and NOT.
- Logic gates implement logic functions.



LOGICAL OPERATIONS

- The three basic logical operations are:
 - AND
 - OR
 - NOT
- AND is denoted by a dot ($\cdot$).
- OR is denoted by a plus ($+$).
- NOT is denoted by an overbar ($\bar{}$), a single quote mark ($'$) after, or ($\sim$) before the variable.

NOR

x	y	out = x NOR y
0	0	1
0	1	0
1	0	0
1	1	0

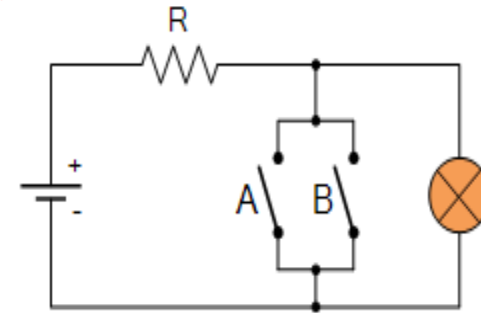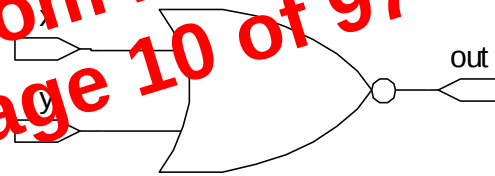Preview from Notesale.co.uk
Page 10 of 97






Lamp - ON = "1"
Lamp - OFF = "0"


Switch A - Open = "0", Closed = "1"

Switch B - Open = "0", Closed = "1"

amplitude

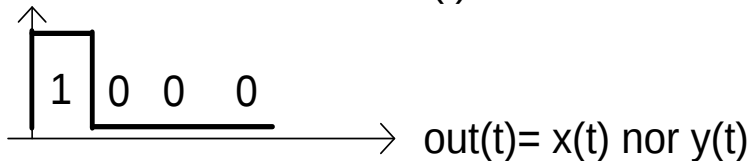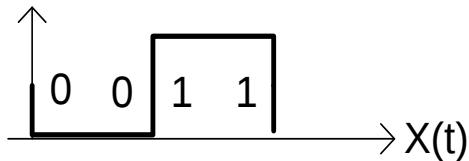
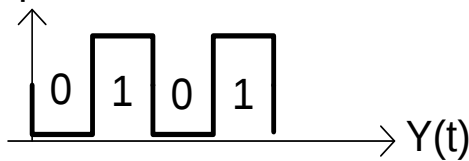


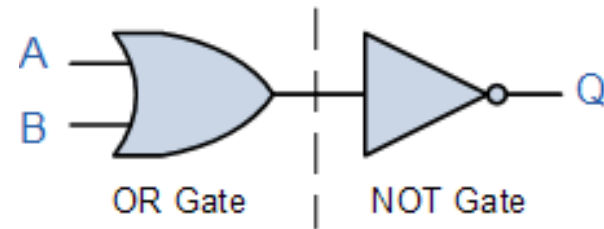- Output value is the complemented output from an "OR" function.



XOR (EXCLUSIVE OR)

x	y	out = $x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

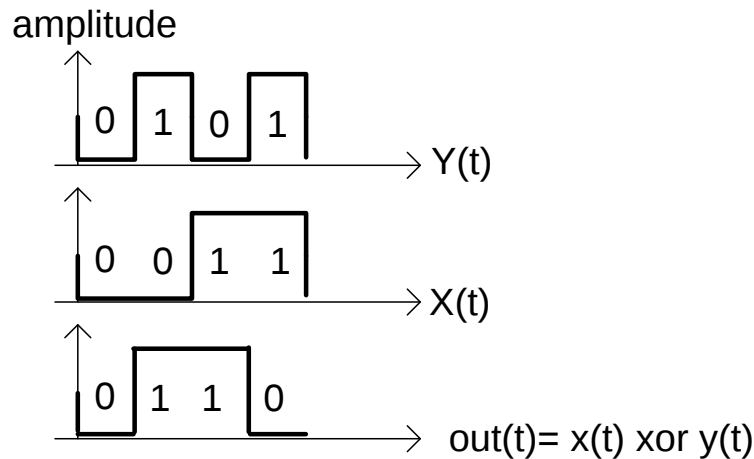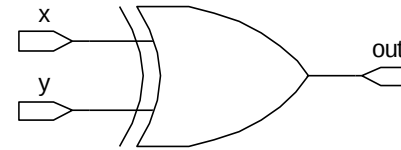

- The number of inputs that are 1 matter.
- More than two values can be “xor-ed” together.
- General rule: the output is equal to 1 if an odd number of input values are 1 and 0 if an even number of input values are 1.

TRUTH TABLES


- Used to evaluate any logic function
- Consider $F(X, Y, Z) = XY + \bar{Y}Z$

X	Y	Z	XY	$\bar{Y}$	$\bar{Y}Z$	$F = XY + \bar{Y}Z$
0	0	0	0	1	0	0
0	0	1	0	1	1	1
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	1	0	0
1	0	1	0	1	1	1
1	1	0	1	0	0	1
1	1	1	1	0	0	1


REALIZATION USING NAND

- NOT GATE

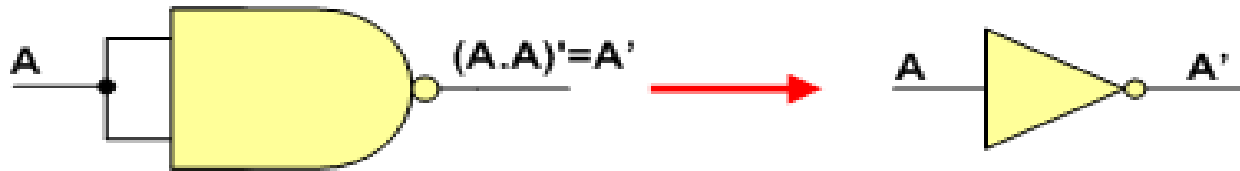All NAND input pins connect to the input signal A gives an output A'.




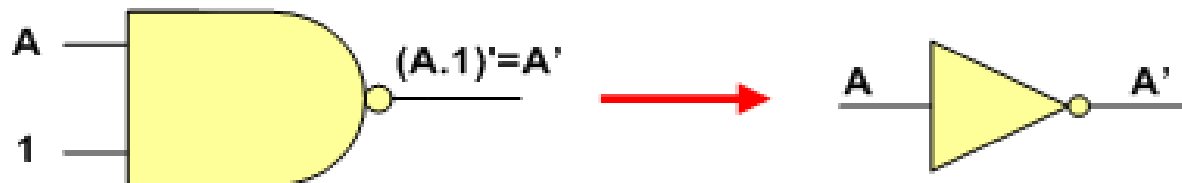One NAND input pin is connected to the input signal A while all other input pins are connected to logic 1. The output will be A'.




DEMORGAN'S THEOREMS

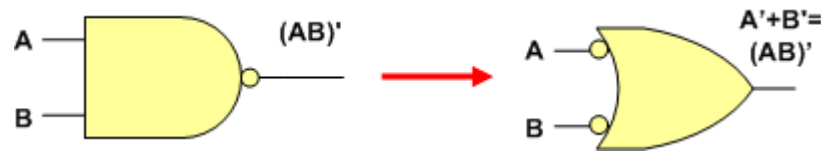- DeMorgan's theorems provide mathematical verification of:
 - the equivalency of the NAND and negative-OR gates



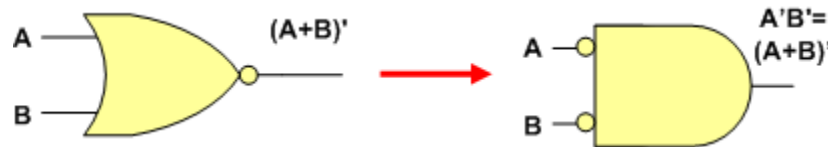- the equivalency of the NOR and negative-AND gates.



DEMORGAN'S THEOREMS

- The complement of two or more ANDed variables is equivalent to the OR of the complements of the individual variables.

NAND

$$\overline{X \bullet Y} = \bar{X} + \bar{Y}$$

Negative-OR

- The complement of two or more ORed variables is equivalent to the AND of the complements of the individual variables.

NOR

$$\overline{X + Y} = \bar{X} \bullet \bar{Y}$$

Negative-AND

BOOLEAN OPERATOR PRECEDENCE

- The order of evaluation is:

1. Parentheses

2. NOT

3. AND

4. OR

- Consequence: Parentheses appear around OR expressions

- Example: $F = A(B + C)(C + \overline{D})$

EXPRESSION SIMPLIFICATION

- An application of Boolean algebra
- Simplify to contain the smallest number of literals (variables that may or may not be complemented)

$$AB + \bar{A}CD + \bar{A}BD + \bar{A}C\bar{D} + ABCD$$

$$= AB + ABCD + \bar{A}CD + \bar{A}C\bar{D} + \bar{A}BD$$

$$= AB + AB(CD) + \bar{A}C(D + \bar{D}) + \bar{A}BD$$

$$= AB + \bar{A}C + \bar{A}BD = B(A + \bar{A}D) + \bar{A}C$$

$$= B(A + D) + \bar{A}C \text{ (has only 5 literals)}$$

- A Simplification Example:

$$F(A, B, C) = \sum (1, 4, 5, 6, 7)$$

- Writing the minterm expression

$$F = \bar{A} \bar{B} C + A \bar{B} C + A \bar{B} \bar{C} + A B \bar{C} + A B C$$

- Simplifying:

$$F = \bar{A} \bar{B} C + A (\bar{B} \bar{C} + \bar{B} C + B \bar{C} + B C)$$

$$F = \bar{A} \bar{B} C + A (\bar{B} (\bar{C} + C) + B (\bar{C} + C))$$

$$F = \bar{A} \bar{B} C + A (\bar{B} + B)$$

$$F = \bar{A} \bar{B} C + A$$

$$F = \bar{B} C + A$$

- Simplified F contains 3 literals

FOUR-VARIABLE K-MAPS

- We can do four-variable expressions too!
 - The minterms in the third and fourth columns, *and* in the third and fourth rows, are switched around.
 - Again, this ensures that adjacent squares have common literals.

		y		
w	$w'x'y'z'$	$w'x'y'z$	$w'x'yz$	$w'x'yz'$
	$w'xy'z'$	$w'xy'z$	$w'xyz$	$w'xyz'$
	$wxy'z'$	$wxy'z$	$wxyz$	$wxyz'$
	$wx'y'z'$	$wx'y'z$	$wx'yz$	$wx'yz'$
		z		x

		y		
w	m_0	m_1	m_3	m_2
	m_4	m_5	m_7	m_6
	m_{12}	m_{13}	m_{15}	m_{14}
	m_8	m_9	m_{11}	m_{10}
		z		x

- Grouping minterms is similar to the three-variable case, but:
 - You can have rectangular groups of 1, 2, 4, 8 or 16 minterms.
 - You can wrap around *all four* sides.

EXAMPLE: SIMPLIFY

$$M_0 + M_2 + M_5 + M_8 + M_{10} + M_{13}$$

- The expression is already a sum of minterms, so here's the K-map:

		y			
		1	0	0	1
		0	1	0	0
W		0	1	0	0
		0	1	0	0
		1	0	0	1
		Z			

		y			
		m ₀	m ₁	m ₃	m ₂
		m ₄	m ₅	m ₇	m ₆
W		m ₁₂	m ₁₃	m ₁₅	m ₁₄
		m ₈	m ₉	m ₁₁	m ₁₀
		Z			


		y			
		1	0	0	1
		0	1	0	0
W		0	1	0	0
		0	1	0	0
		1	0	0	1
		Z			

		y			
		w'x'y'z'	w'x'y'z	w'x'yz	w'xyz'
		w'xy'z'	w'xyz	w'xyz	w'xyz'
W		wxy'z'	wxyz	wxyz	wxyz'
		wxy'z'	wxyz	wxyz	wxyz'
		wxy'z'	wxyz	wxyz	wxyz'
		Z			

- We can make the following groups, resulting in the MSP $x'z' + xy'z$.

K-MAPS CAN BE TRICKY!

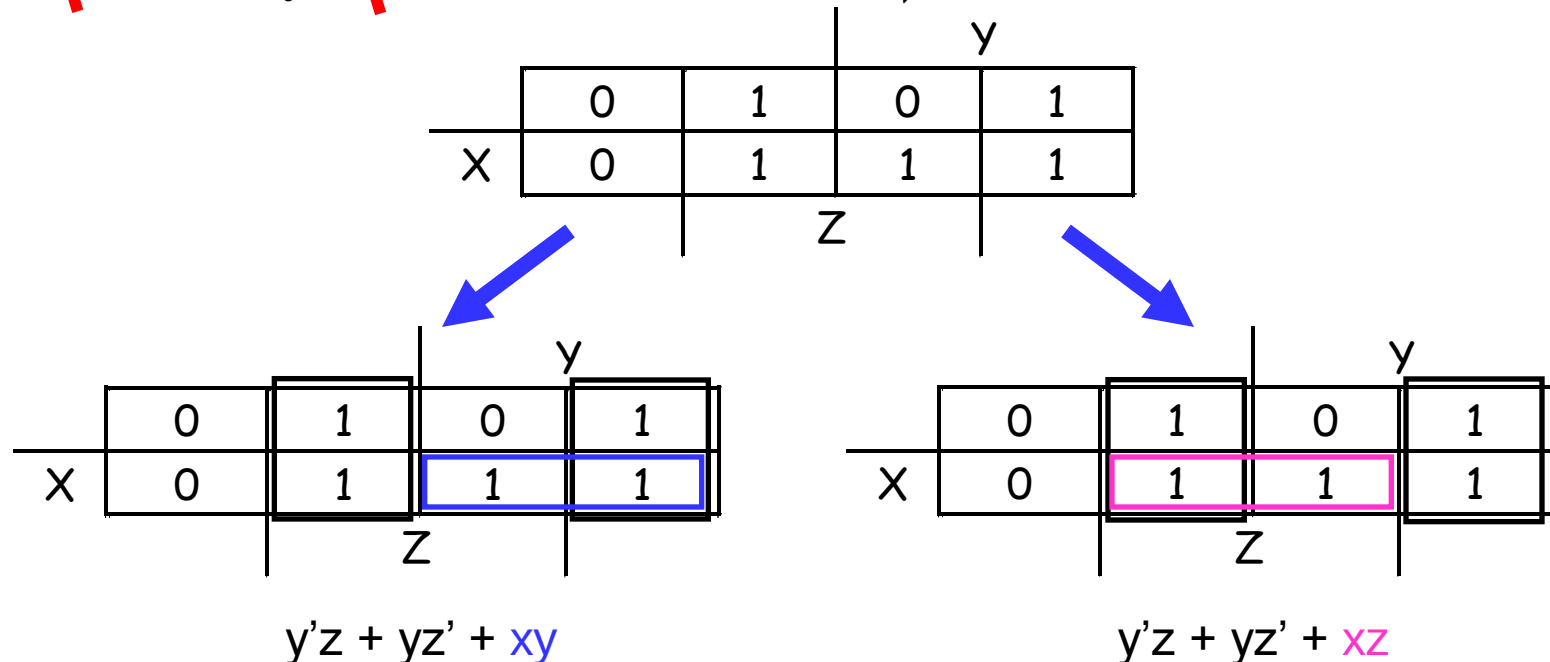- There may not necessarily be a *unique* MSP. The K-map below yields two valid and equivalent MSPs, because there are two possible ways to include minterm m_7 .



- Remember that overlapping groups is possible, as shown above.

MAXTERM EXAMPLE

Preview from Notesale.co.uk
Page 85 of 97

		$(A+B)$	$(A+B')$	$(A'+B')$	$(A'+B)$
		$A'B'$	$A'B$	AB	AB'
C	C'		0	0	0
	C	0		0	

$$f(A,B,C) = \prod M(1,2,4,6,7)$$

$$=(A+B+C')(A+B'+C)(A'+B+C)(A'+B'+C)(A'+B'+C')$$

Note that the complements are (0,3,5) which are the minterms of the previous example

FOUR VARIABLE EXAMPLE

(A) MINTERM FORM. (B) MAXTERM FORM.

$$f(a,b,Q,G) = \sum m(0,3,5,7,10,11,12,13,14,15) = \prod M(1,2,4,6,8,9)$$

Preview from Notesale.co.uk
Page 86 of 97

		a			
		ab			
		00	01	11	10
Q	QG	0	4	12	8
	00	1		1	
	01	1	1	1	9
	11	1	1	1	1
	10			1	1

(a)

		a			
		ab			
		00	01	11	10
Q	QG	0	4	12	8
	00		0		0
	01	0			0
	11				
	10	0	0		

(b)