

INTRODUCTION



Preview from Notesale.co.uk
Page 2 of 36

- ❑ Design problem normally starts with a word description of input output relation and ends with a circuit diagram having sequential and combinatorial logic elements.
- ❑ Sequential logic circuit design refers to synchronous clock-triggered circuit because of its design and implementation advantages.
- ❑ Design a digital circuit whose outputs are to take on specific values after a specific sequence of inputs has taken place.

STATE MACHINE DESIGN



Preview from Notesale.co.uk
Page 10 of 36

MOORE MODEL	MEALY MODEL
The output depends only on present state and not on input	The output is derived from present state as well as input
It requires more number of states and thereby more hardware to solve any problem	It requires less number of states and thereby less hardware to solve any problem
The output is generated one clock cycle after.	The output is generated one clock cycle earlier, so faster
The output remains stable over entire clock period and changes only when there occurs a state change at clock trigger based on input available at that time.	The glitches occurs

SEQUENCE RECOGNIZER




Step: 5 Build the circuit

For Output Z

K-map

X \ Q ₁ Q ₀	00		01	11	10
	0	1	0	1	0
0	0	0	0	0	0
1	0	0	1	0	0

$$Z = XQ_1Q_0$$

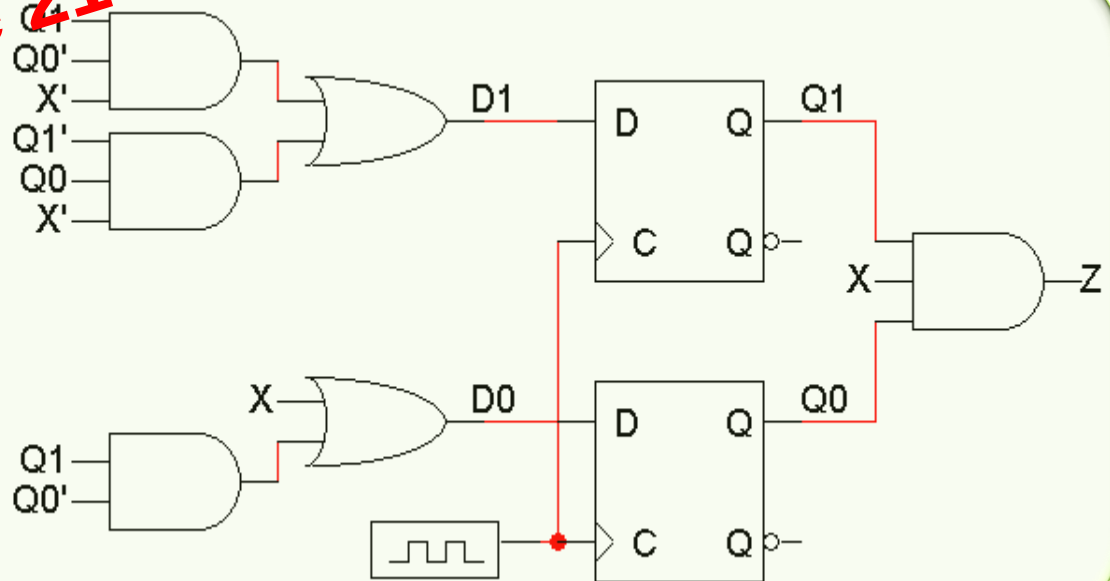

$$D_1 = Q_1 Q_0' X' + Q_1' Q_0 X'$$

$$D_0 = X + Q_1 Q_0'$$

SEQUENCE RECOGNIZER



Step: 2 Assigning binary codes to States

Preview from Notesale.co.uk
Page 23 of 36

Present	Next		Output	
	X=0	X=1	X=0	X=1
A	B	A	0	0
B	B	C	0	0
C	B	A	1	0

Next State Table

Put A=00

B=01

C=10

Present		Next			
		X=0		X=1	
Q ₁	Q ₀	Q ₁	Q ₀	Q ₁	Q ₀
0	0	0	1	0	0
0	1	0	1	1	0
1	0	0	1	0	0

SEQUENCE RECOGNIZER



Step: 4 Find equation for the FF inputs and output

Preview from Notesale.co.uk
Page 25 of 36

X=0			X=1		
QP ₀	QN ₀	T ₀	QP ₀	QN ₀	T ₀
0	1	1	0	0	0
1	1	0	1	0	1
0	1	1	0	0	0

K-map for T₀

Q ₁ Q ₀		00	01	11	10
X	0	<u>1</u>	0	x	<u>1</u>
	1	0	<u>1</u>	<u>x</u>	0

$$T_0 = X'Q_0' + XQ_0$$

SEQUENCE RECOGNIZER



Step: 4 Find equation for the FF inputs and output

Preview from Notesale.co.uk
Page 31 of 36

X=0			X=1		
QP ₀	QN ₀	T ₀	QP ₀	QN ₀	T ₀
0	0	0	0	1	1
1	0	1	1	1	0
0	0	0	0	1	1

K-map for T₀

Q ₁ Q ₀		00	01	11	10
X	0	0	1	X	0
	1	1	0	X	1

$$T_0 = X'Q_0 + XQ_0'$$