

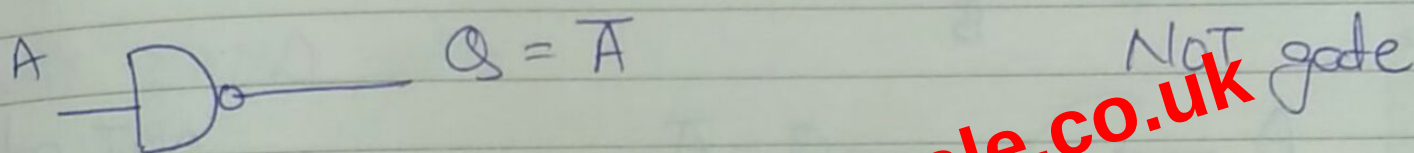
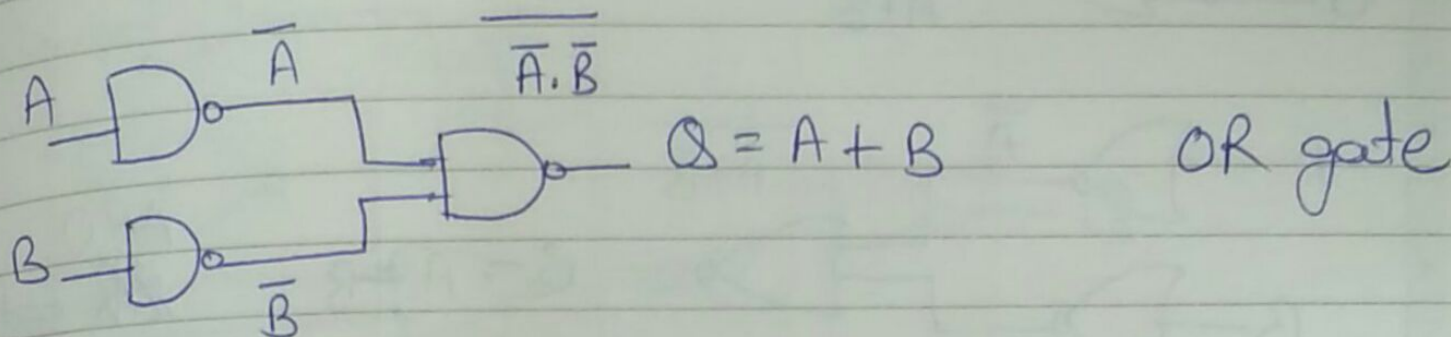


→ Basic Logic gates using NAND gates

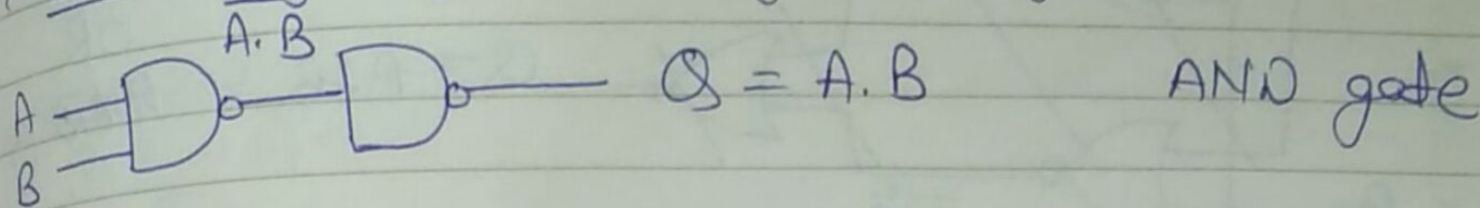

Used in :- Burglar alarm, freezer buzzer, etc
 light activated theft alarm
 automatic watering systems

→ NOR Gate

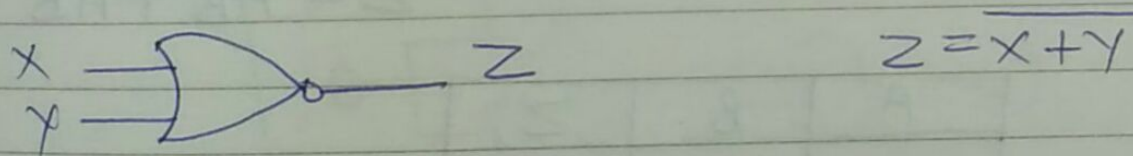

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0