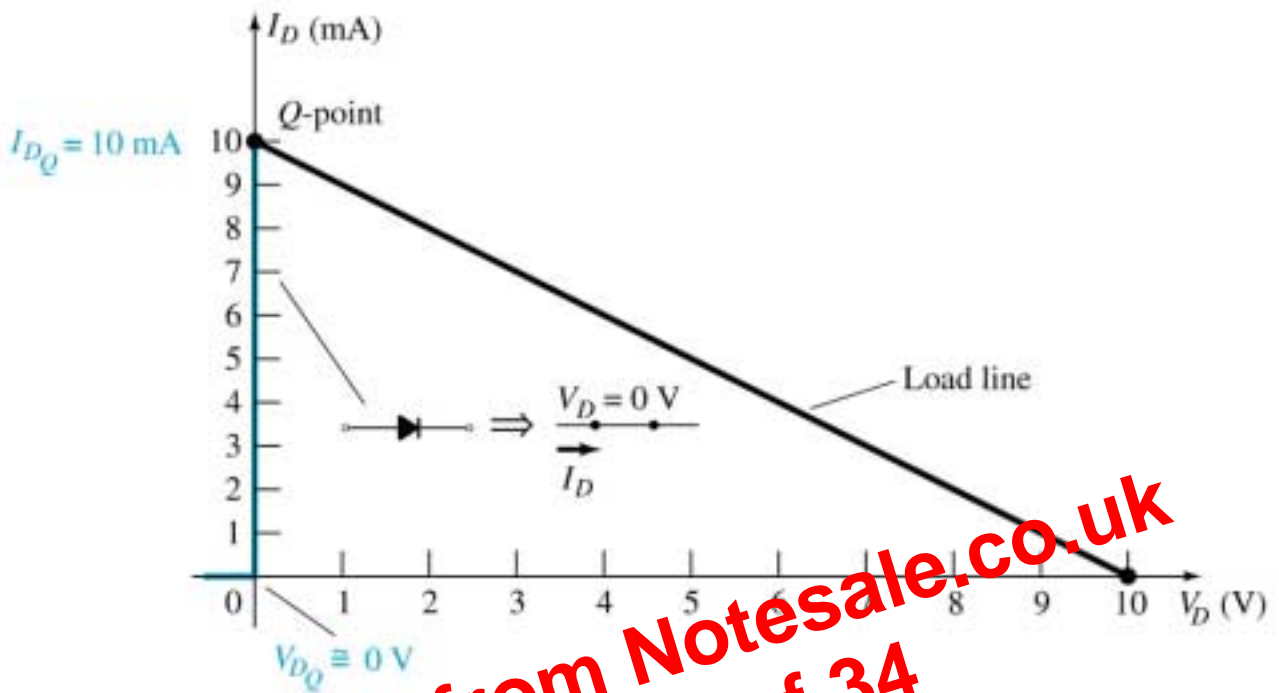


# Load Line Analysis

- The intersection point is called Q point
- Same solution can be found by using nonlinear diode equation
- We can avoid heavy math using load line analysis.
- Exp from notes 1
- Exp from notes 2
- Exp from notes 3


Preview from Notesale.co.uk  
Page 5 of 34



Preview from Notesale.co.uk  
Page 11 of 34

Solution to example 3 using ideal model


# Example 10

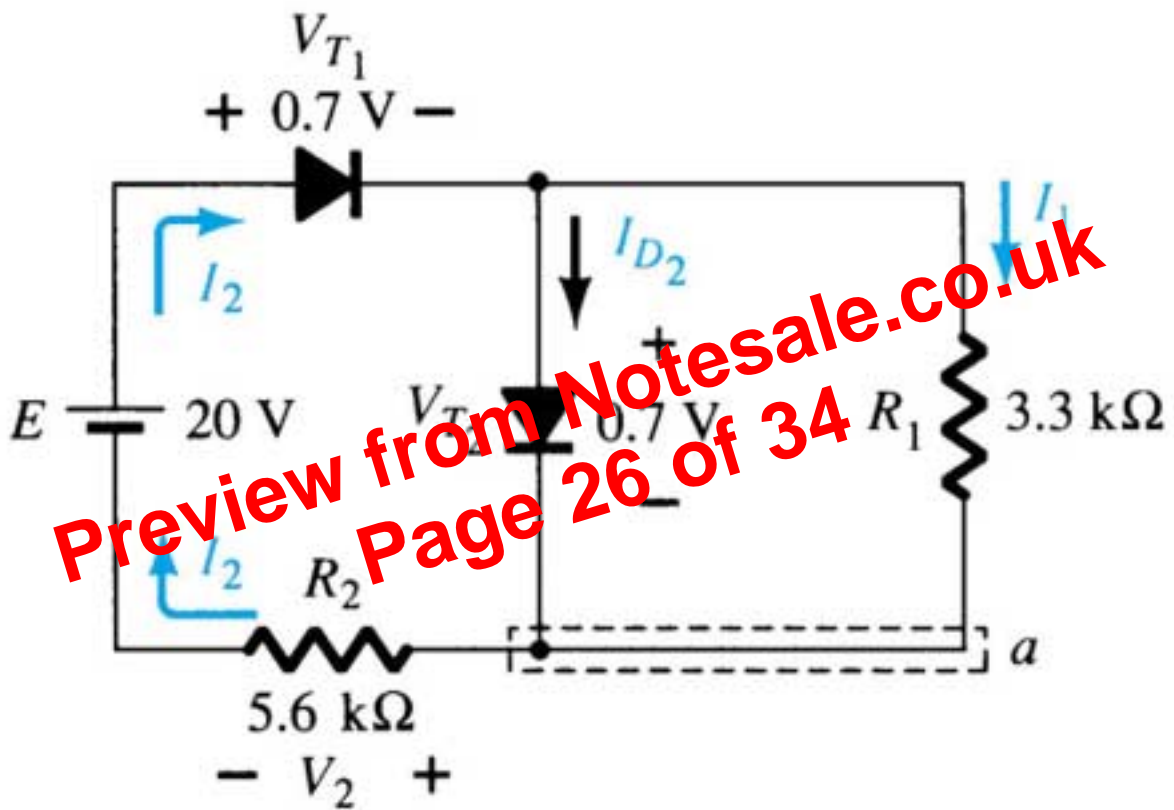

Determining the unknown quantities for the above example
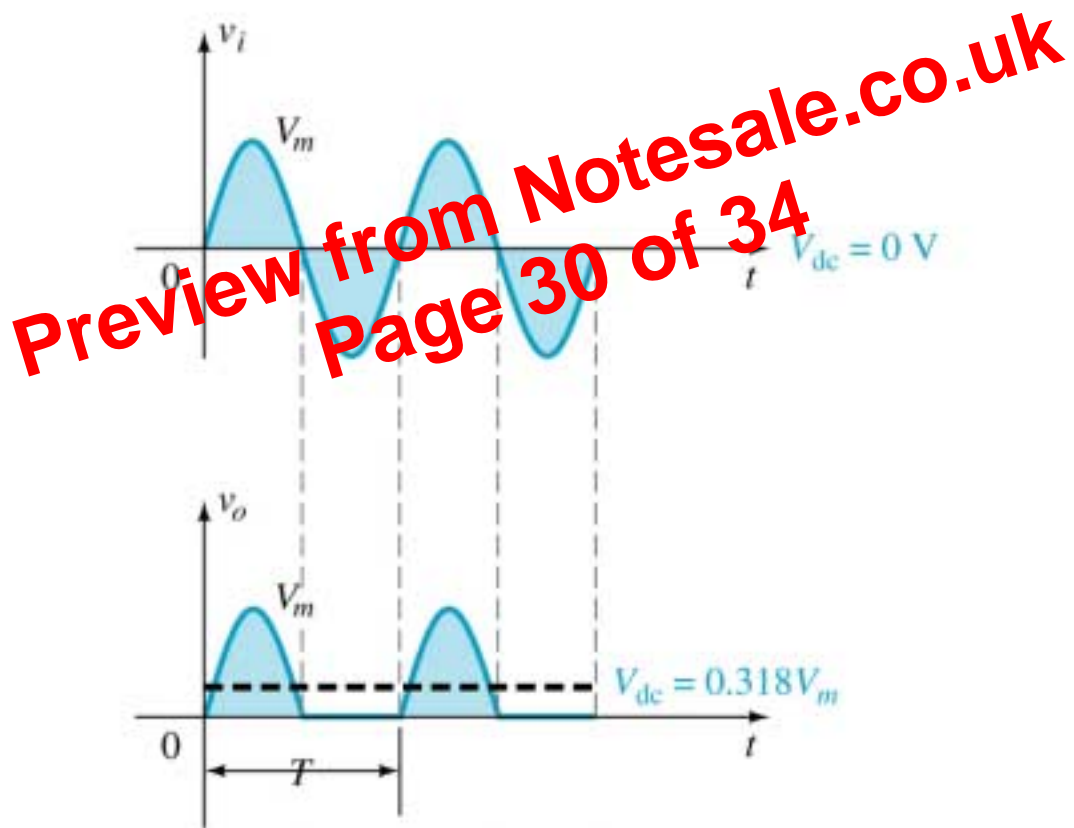
# Half-wave Rectifier

- The total effect of diode on the output signal is given in below



# Half-wave Rectifier

- For the half-wave rectified signal:

$$V_{dc} = 0.318 V_m$$

- If the effect of  $V_T$  is also considered, the output of the system will as below
- $V_{dc} = 0.318 (V_m - V_T)$
- See next Figure

Preview from Notesale.co.uk  
Page 31 of 34