

Similarly during $(1-D)T_s$ period

$$\frac{dI_L}{dt} = \frac{\Delta I_L}{\Delta t} = \frac{\Delta I_L}{(1-D)T_s} = \frac{V_2 - V_0}{L} \rightarrow (2)$$

$$(1) \Rightarrow L = \frac{V_2 D}{\Delta I_L f_s}$$

$$\Delta I_L = \frac{V_2 D}{L f_s} \rightarrow \text{ripple current}$$

Similar to buck converter

$$\Delta Q = C \Delta V_0 = I_0 D T_s$$

$$C = \frac{I_0 D}{\Delta V_0 f_s}$$

$$\Delta V_0 = \frac{I_0 D}{C f_s} \rightarrow \text{ripple voltage}$$

Preview from Notesale.co.uk
Page 6 of 9

