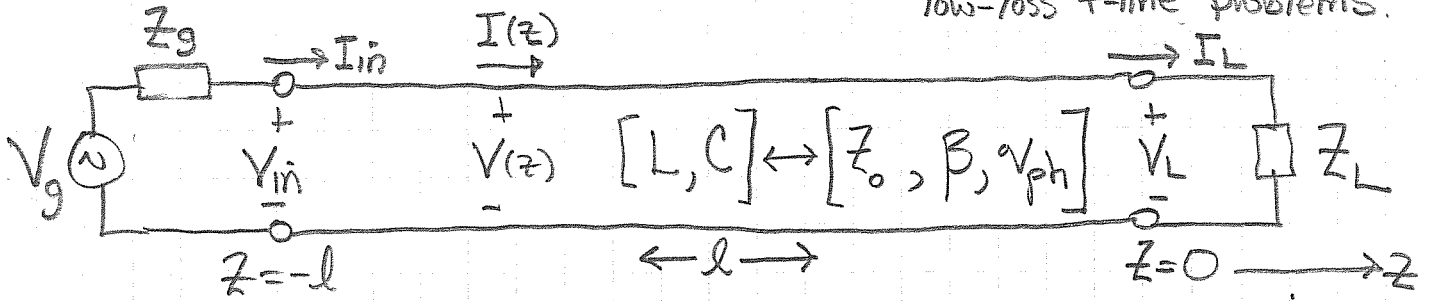


Lossless T-line  $[e^{+j\omega t}]$ ;  $\{R \approx 0, G \approx 0 \rightarrow \alpha \approx 0$   
 good for solving short  
 low-loss +line problems.



$$\begin{cases} Z_{in} \\ \Gamma_{in} = \Gamma_L e^{-j2\beta l} \end{cases} \xrightarrow{\text{lossless}} \begin{cases} \gamma \rightarrow j\beta = j\omega \sqrt{LC} \\ \beta = \frac{\omega}{v_{ph}} = \frac{2\pi}{\lambda} \\ Z_0 = \sqrt{\frac{L}{C}} ; v_{ph} = \frac{1}{\sqrt{\epsilon_{eff}}} \end{cases}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{V^r}{V^i}$$

$$\Gamma_{in}(z=0) = \frac{V_L}{I(z=0)} = \frac{V_L}{I_L}$$

$$\begin{cases} V(z) = [V^i e^{-j\beta z} + V^r e^{+j\beta z}] \\ I(z) = [\frac{V^i}{Z_0} e^{-j\beta z} - \frac{V^r}{Z_0} e^{+j\beta z}] \end{cases}$$

$$|V(z)| = |V^i| |1 + \Gamma_L e^{+j\frac{4\pi}{\lambda} z}|$$

$$\text{Voltage Standing Wave Ratio } VSWR = \frac{V_{max}}{V_{min}} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

Voltage standing wave on line  
 Voltage Standing Wave Ratio

$$* Z_{in} = \frac{V_{in}}{I_{in}} = Z_0 \left[ \frac{e^{+j\beta l} + \Gamma_L e^{-j\beta l}}{e^{+j\beta l} - \Gamma_L e^{-j\beta l}} \right] = Z_0 \left[ \frac{1 + \Gamma_L e^{-j2\beta l}}{1 - \Gamma_L e^{-j2\beta l}} \right] = Z_0 \left( \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} \right)$$

$$\tan h j\beta l = j \tan \beta l \quad Z_{in} = Z_0 \left[ \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right]$$

$$\Gamma_{in} = \Gamma_L e^{-j2\beta l}$$

also sin/cos expressions used

$$V_{in} = \frac{Z_{in}}{Z_{in} + Z_g} V_g ; V^i = \frac{V_{in}}{e^{j\beta l} + \Gamma_L e^{-j\beta l}} = \frac{V_{in}}{1 + \Gamma_{in}(l)} e^{-j\beta l}$$

$$\rightarrow \text{can now solve for } V(z), V_L$$

$$* \lambda_{air} = c/f ; \lambda = \lambda_{air} / \sqrt{\epsilon_{eff}} ; v_{ph} = c / \sqrt{\epsilon_{eff}} ; Z_0 = Z_{air} / \sqrt{\epsilon_{eff}}$$