


Preview from Notesale.co.uk  
Page 1 of 60

# FREQUENCY RESPONSE, BODE PLOT, RESONANCE

Gavax Joshi

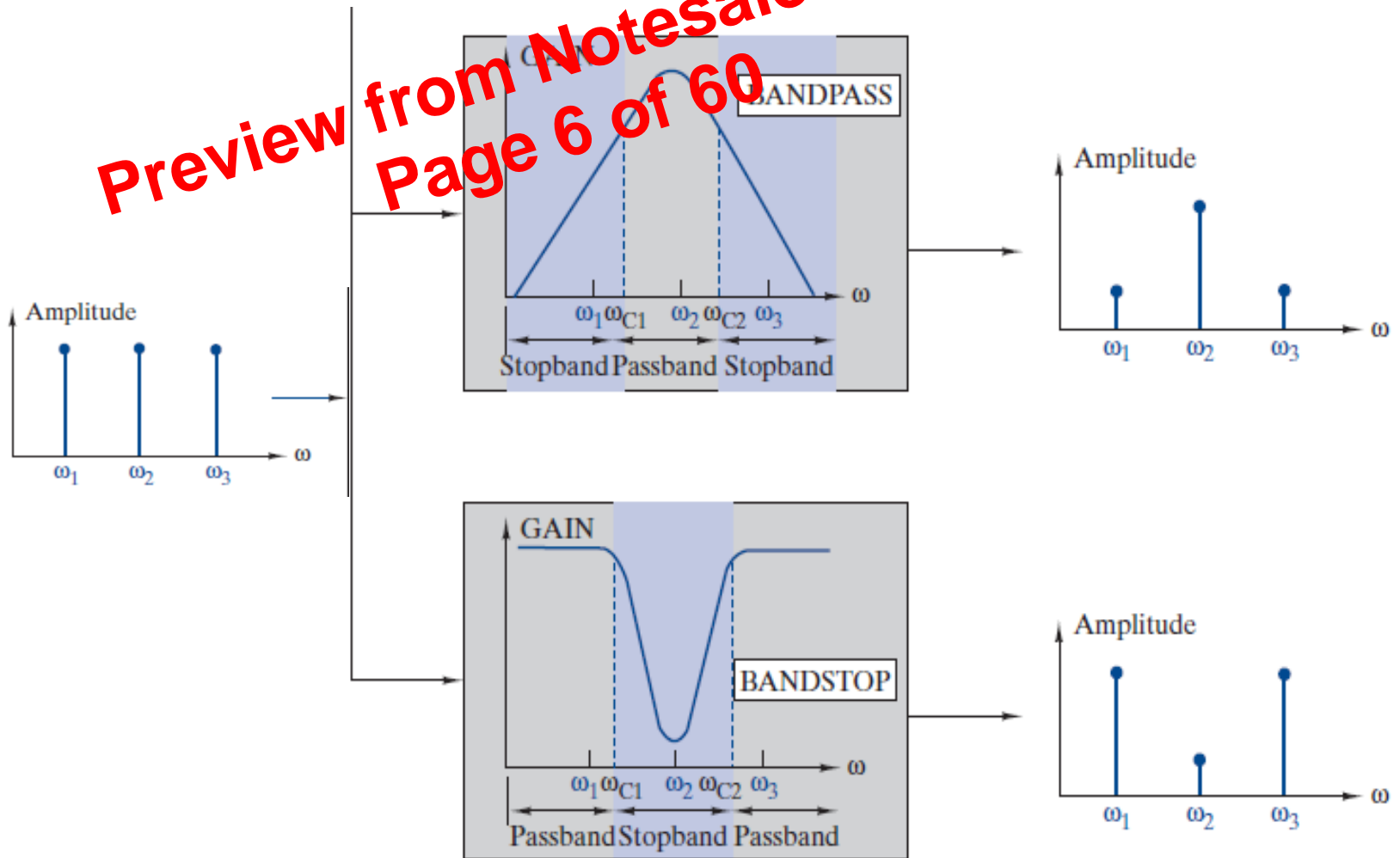
# Basic Gain Responses Cont...

Preview from Notesale.co.uk  
Page 6 of 60



# RESONANCE and the voltage response: $|V(j\omega)|$ in an RLC

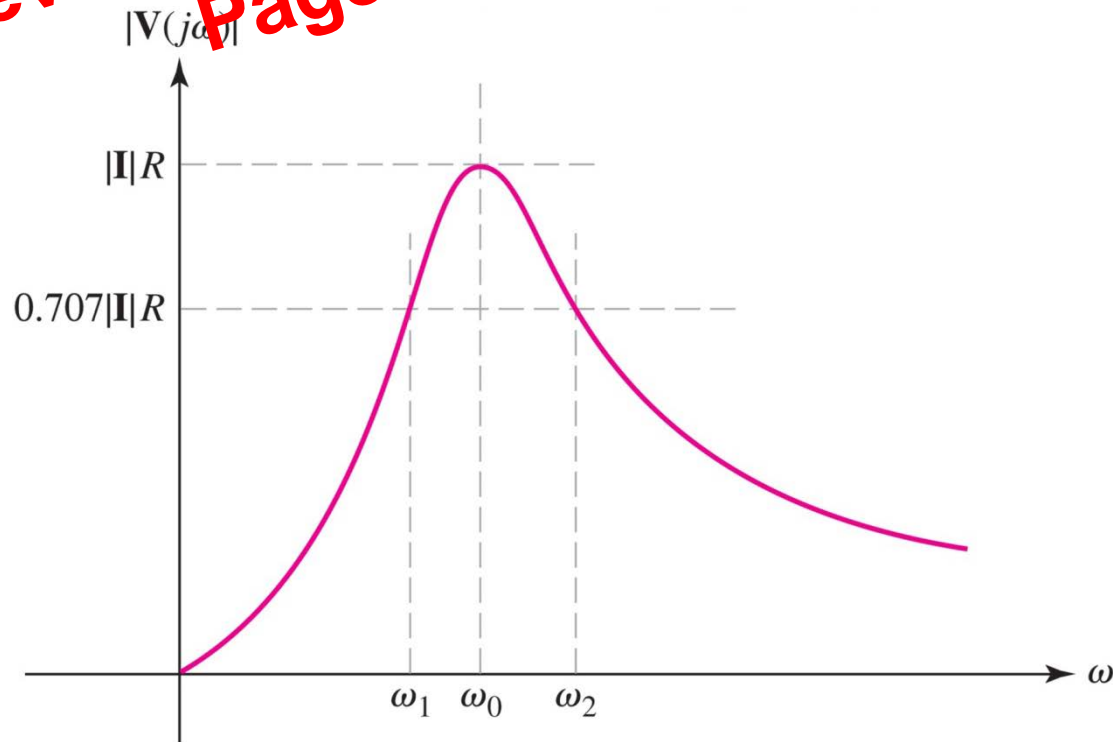Preview from [Notesale.co.uk](http://Notesale.co.uk)  
Page 22 of 60



# The Quality Factor $Q$ | EL RLC

$$Q = 2\pi \frac{[w_L(t) + w_C(t)]_{\max}}{P_R T}$$

$P_R$  total average power absorbed by all the resistor

Preview from Notesale.co.uk  
Page 26 of 60

$$i(t) = I_m \cos \omega_0 t$$

$$v(t) = Ri(t) = RI_m \cos \omega_0 t$$

$$w_C(t) = \frac{1}{2} C v^2 = \frac{I_m^2 R^2 C}{2} \cos^2 \omega_0 t$$



$$w_L(t) = \frac{1}{2} L i_L^2 = \frac{1}{2} L \left( \frac{1}{L} \int v dt \right)^2 = \frac{1}{2L} \left[ \frac{RI_m}{\omega_0} \sin \omega_0 t \right]^2$$

$$w_L(t) = \frac{I_m^2 R^2 C}{2} \sin^2 \omega_0 t$$

The total *instantaneous* stored energy is therefore constant:

$$w(t) = w_L(t) + w_C(t) = \frac{I_m^2 R^2 C}{2}$$

# RESONANCE: Series RLC

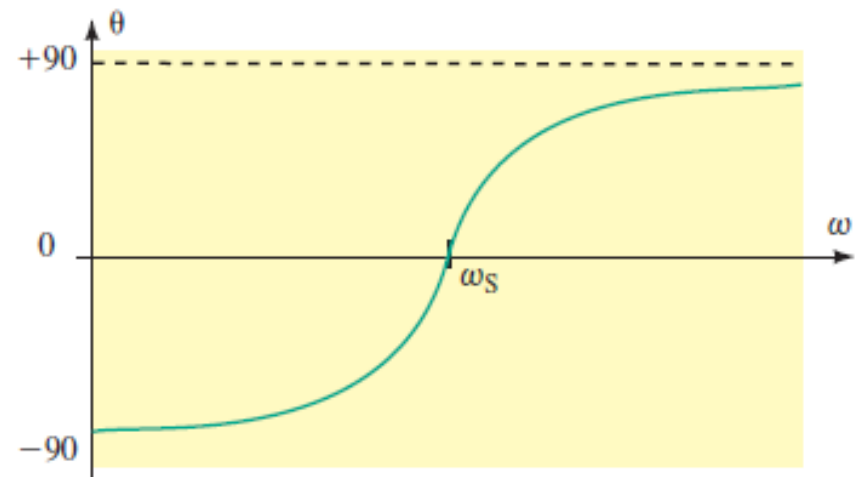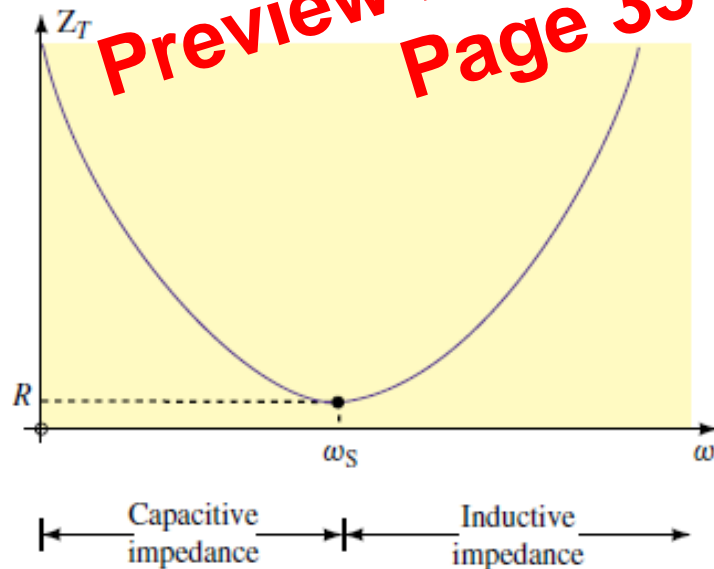

Due to the changing impedance of the circuit, we conclude that if a constant amplitude voltage is applied to the series resonant circuit, the current and power of the circuit will not be constant at all frequencies.

# RESONANCE: Series RLC

The bandwidth of the series resonant circuit is

$$BW = w_b = w_2 - w_1 = \frac{R}{L}$$

We define the Q (quality factor) of the circuit as;

$$Q = \frac{w_o L}{R} = \frac{1}{w_o RC} = \frac{1}{R} \sqrt{\left(\frac{L}{C}\right)}$$

Using Q, we can write the bandwidth as;

$$BW = \frac{w_o}{Q}$$

These are all important relationships.

# RESONANCE: Series RLC

An Observation

By using  $Q = \omega_0 L/R$  in the equations for  $\omega_1$  and  $\omega_2$  we have;


$$\omega_1 = \omega_0 \left[ \frac{-1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right]$$

and

$$\omega_2 = \omega_0 \left[ \frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right]$$
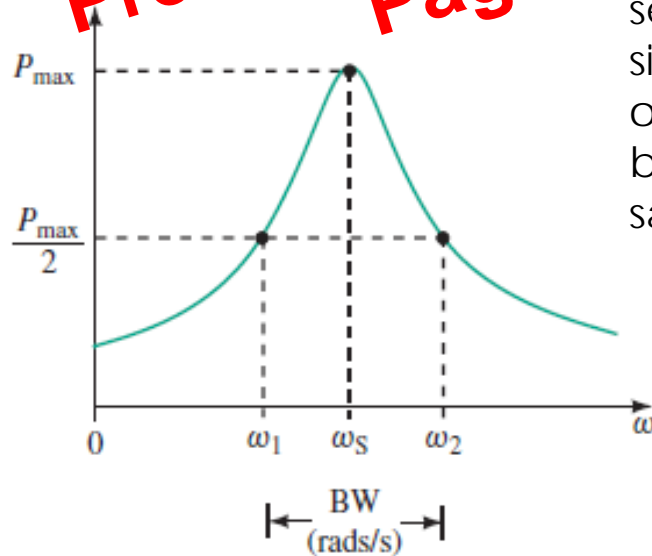
# RESONANCE: Series RLC SELECTIVITY

Preview from Notesale.co.uk  
Page 43 of 60



If the bandwidth of a circuit is kept very narrow, the circuit is said to have a high selectivity, since it is highly selective to signals occurring within a very narrow range of frequencies. On the other hand, if the bandwidth of a circuit is large, the circuit is said to have a low selectivity.

Selectivity curve.

## APPROXIMATE EXPRESSIONS

Preview from [Notesale.co.uk](http://Notesale.co.uk)  
Page 50 of 60

$$\omega_d \approx \omega_0$$

$$\omega_{1,2} \approx \omega_0 \mp \frac{1}{2}\beta$$

$$\omega_0 \approx \frac{1}{2}(\omega_1 + \omega_2)$$

## EXAMPLE 2

A series RLC resonant circuit has a resonant frequency admittance of  $2 \times 10^{-2}$  S (mhos). The Q of the circuit is 50, and the resonant frequency is 10,000 rad/sec. Calculate the values of R, L, and C. Find the half-power frequencies and the bandwidth.

First,  $R = 1/G = 1/(0.02) = 50$  ohms.

Second, from  $Q = \frac{\omega_0 L}{R}$ , we solve for L, knowing Q, R, and  $\omega_0$  to find  $L = 0.25$  H.

Third, we can use  $C = \frac{Q}{\omega_0 R} = \frac{50}{10,000 \times 50} = 100 \mu F$