

What is engineering?

Purposeful use of science

What is 6.002 about?

Gainful employment of
Maxwell's equations

Preview from Notesale.co.uk
Page 4 of 24

From electrons to digital gates
and op-amps

Lumped Circuit Abstraction

Consider



The Big Jump
from physics
to EECS

Preview from Notesale.co.uk
Page 6 of 24

Suppose we wish to answer this question:
What is the current through the bulb?

V Must also be defined.


see
A & L

So let's assume this too

V_{AB} defined when $\frac{\partial \phi_B}{\partial t} = 0$

So $V_{AB} = \int_{AB} E \cdot dl$ outside elements

What can we say about currents?

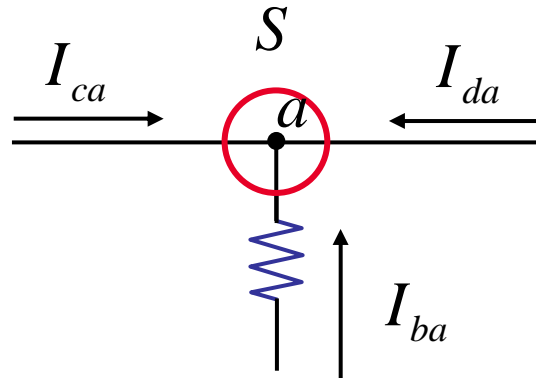

$$\oint_S \mathbf{J} \cdot d\mathbf{S} = -\frac{\partial q}{\partial t} \quad \text{under LMD}$$

$$\Rightarrow I_{ca} + I_{da} + I_{ba} = 0$$

Kirchhoff's Current Law (KCL):

The sum of the currents into a node is 0.

simply conservation of charge