

Review

Maxwell's equations simplify to algebraic KVL and KCL under LMD!

KVL:

$$\sum_{\text{loop}} v_j = 0$$

loop

Preview from Notesale.co.uk
Page 4 of 19

KCL:


$$\sum_j i_j = 0$$

node



Other Analysis Methods

Method 2— Apply element combination rules

Example

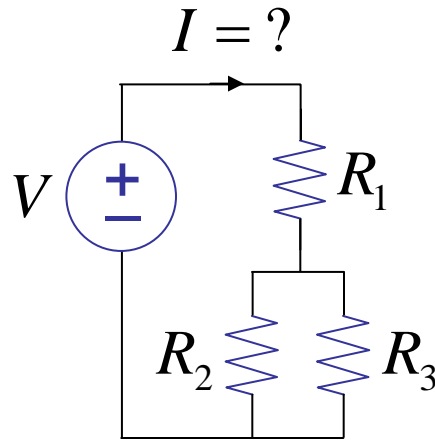

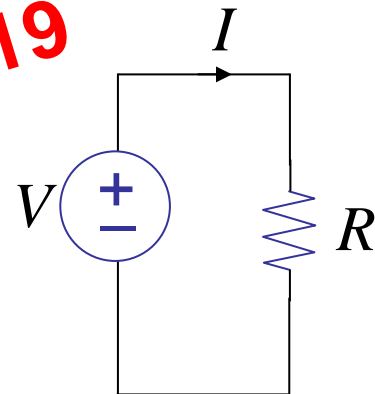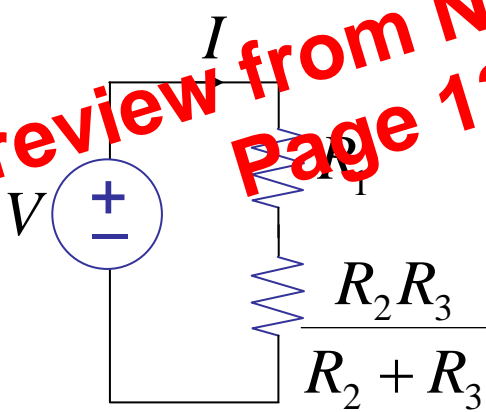Preview from Notesale.co.uk
Page 13 of 19



$$R = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

$$I = \frac{V}{R}$$

Method 3—Node analysis

Particular application of KVL, KCL method

1. Select reference node (\perp ground) from which voltages are measured.
2. Label voltages of remaining nodes with respect to ground. These are the primary unknowns.
3. Write KCL for all but the ground node, substituting device laws and KVL.
4. Solve for node voltages.
5. Back solve for branch voltages and currents (i.e., the secondary unknowns)