

(c)

$$I_B = \frac{(15 - 1)}{470K} = 29.8 \mu A$$

$$I_C = 100 \times 29.8 \mu A = 2.98 \text{ mA}$$

$$V_{CE} = 15 - 2.98 \text{ mA} \times 3.6K \Omega$$

$$= \underline{\underline{4.27 \text{ V}}}$$

## Example

Find  $V_{CE}$  from the last example

IF  $V_{BB} = 5V$

## Reading Data Sheets

2N3904

$$V_{CB} = 60V, V_{CEO} = 40V$$

$$V_{EB} = 6V, I_C = 200 \text{ mA d.c.}$$

$$P_D = 250 \text{ mW (for } T_A = 60^\circ\text{C)}$$

$$P_D = 350 \text{ mW (for } T_A = 25^\circ\text{C)}$$

$$P_D = 1 \text{ W (for } T_A = 60^\circ\text{C)?}$$

$$\alpha_{d.c.} = \frac{I_c}{I_E}$$

$$I_E = I_c + I_B$$

$$\frac{I_E}{I_c} = 1 + \frac{I_B}{I_c}$$

or

$$\frac{1}{\alpha_{d.c.}} = 1 + \frac{1}{\beta_{d.c.}}$$

Preview from Notesale.co.uk  
Page 11 of 17

$$\alpha_{d.c.} = \frac{\beta_{d.c.}}{\beta_{d.c.} + 1}$$

if  $\alpha_{d.c.} = 0.98$        $\beta_{d.c.} = 49$

$\beta_{d.c.} = 100$        $\alpha_{d.c.} = 0.99$