
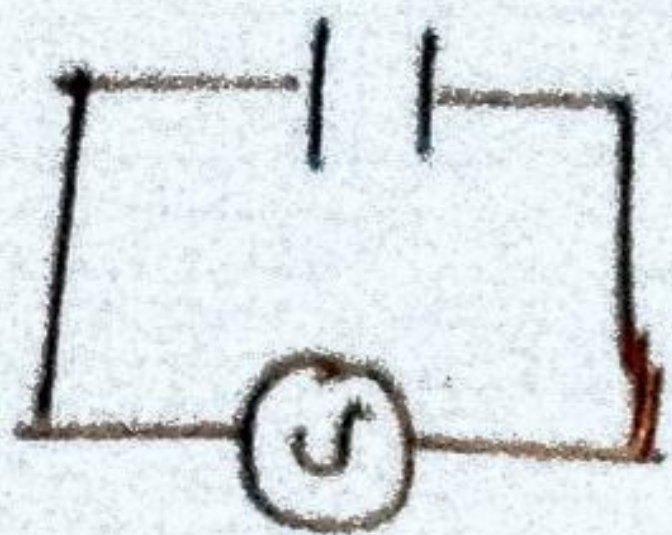


* AC Circuit with Capacitor

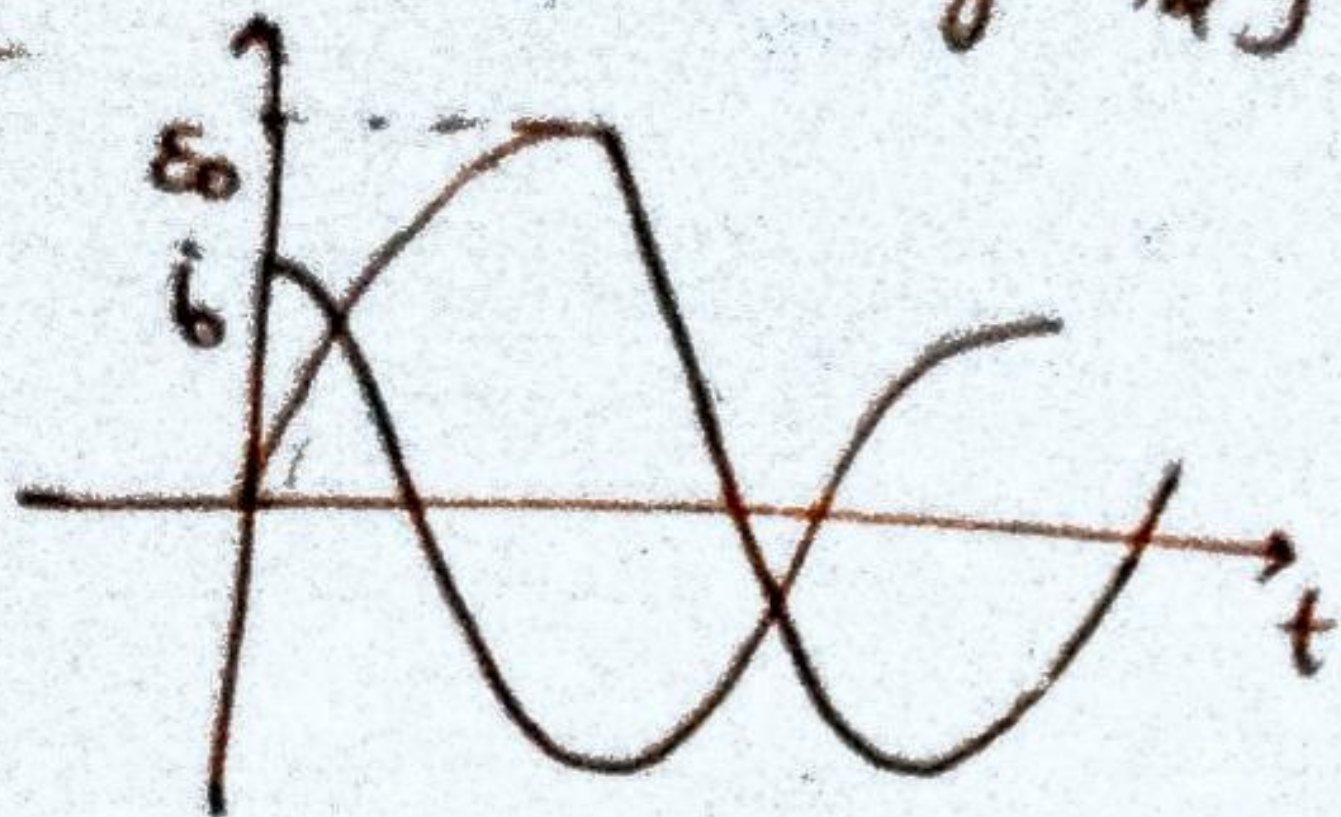

[Current Leads by $\pi/2$]



$$E = E_0 \sin(\omega t)$$

$$i = \frac{E_0}{\left(\frac{1}{\omega C}\right)} \sin(\omega t + \pi/2)$$

$$q = C E_0 \sin(\omega t)$$

$$E = E_0 \sin(\omega t)$$

$$i = \frac{E_0}{\omega L} \sin(\omega t - \pi/2)$$

NOTE:-

$X_L \rightarrow$ Inductive reactance


$$X_L = \omega L$$

$X_C \rightarrow$ Capacitive reactance

$$X_C = \frac{1}{\omega C}$$

Capacitor

Inductor

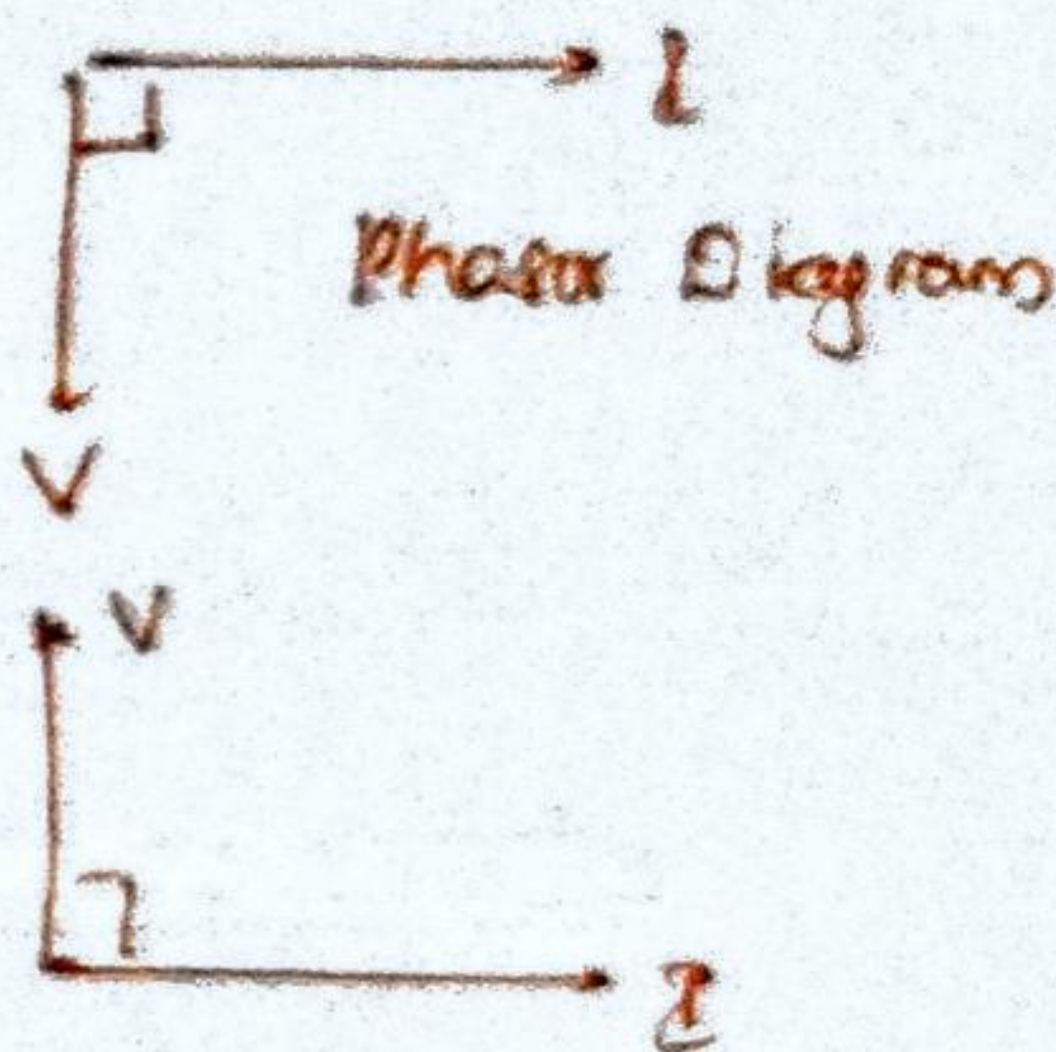

Volatge or PD across
Instrument & current

Reactance

Resistance	Capacitor	Inductor
'R'	$X_C = \frac{1}{\omega C}$	$X_L = \omega L$
	$X_C = \frac{1}{2\pi f C}$	$X_L = 2\pi f L$
	$f=0, X_C \rightarrow \infty$	$f=0, X_L = 0$

Preview from Notesale.co.uk
Page 2 of 4

* [Potential leads current
by $\pi/2$]