

Electric Current/Electricity

- The flow of electrons through a conductor
- *Direction*: always opposite the electron flow
- It is measured in *Amperes (A)*
- 1 A: 1 C/s or 1 electric charge/second

Electric Potential

- It is measured in *volts (V)*
- 1 V: 1 J/C or 1 potential energy/unit charge

Electric Resistance

- It is measured in *ohms (Ω)*

Ohm's Law

- The voltage across the total circuit or any portion of the circuit is equal to the current times the resistance
- *Formulas*: $V = IR$; $R = V/I$; $I = V/R$

Two Basic Types of Electric Circuits

- Series & Parallel Circuits

Series Circuit

- All circuit elements are connected in a line along the same conductor

Rules for Series Circuit

Preview from Notesale.co.uk
Page 5 of 15

- DC: induces no current in the secondary coil

Induction Motor

- A type of motor used with x-rays tubes
- It powers the rotating anode of an x-ray tube

Transformer Law

- The change in voltage is directly proportional to the ratio of the number of turns (*windings*) in the secondary coil (N_s) to the number of turns in the primary coil (N_p)
- Formula: $V_s/V_p = N_s/N_p$

Step-up Transformer

- Turns ratio greater than 1
- Primary Side: low voltage, high current
- Secondary Side: high voltage, low current

Step-down Transformer

- Turns ratio less than 1
- Primary Side: high voltage, low current
- Secondary Side: low voltage, high current

Transformer Law Effect on Current

- A change in current & a change in voltage are inversely related
- Formula: $I_s/I_p = N_p/N_s = V_p/V_s$

Types of Transformer

Preview from Notesale.co.uk
Page 14 of 15