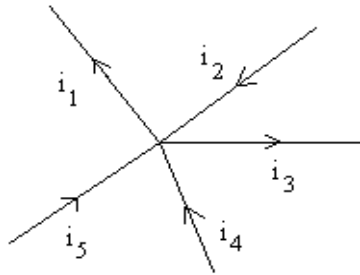


KCL is illustrated below .

Convention

Current flowing **out** of a node is considered positive (+ve)
 Current flowing **into** a node is considered negative (- ve)



$$i_1 - i_2 + i_3 - i_4 - i_5 = 0$$

or

$$i_1 + i_3 = i_2 + i_4 + i_5$$

II. Kirchhoff's voltage law [KVL] -

" In any electrical circuit, the algebraic sum of voltage drops of all branches & emf's is zero."


or

" In any electrical network, the algebraic sum of voltage drops of all branches and emf's forming a closed loop is zero."


Series , parallel , series-parallel combination circuits:-

Resistances in series :-

Series circuit

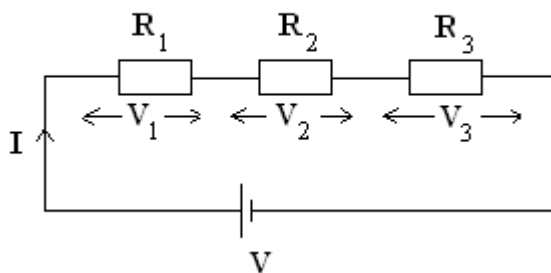









Equivalent circuit

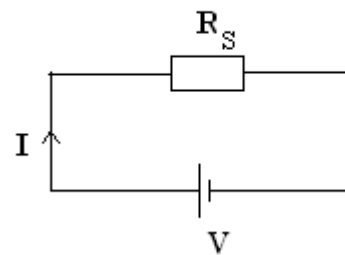

$$V = V_1 + V_2 + V_3$$

Preview from Notesale.co.uk
Page 2 of 17

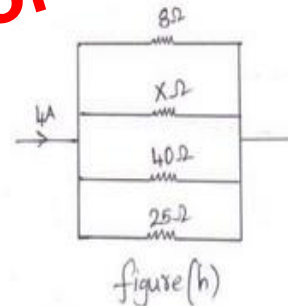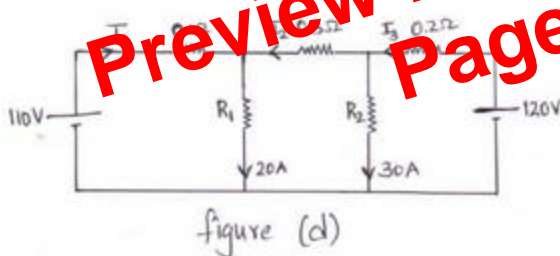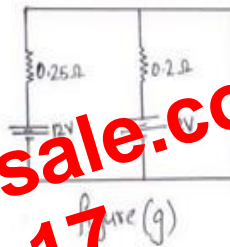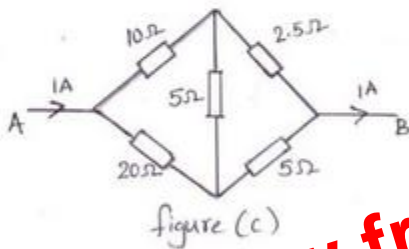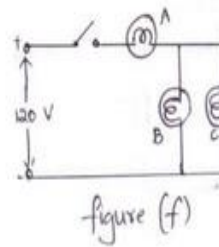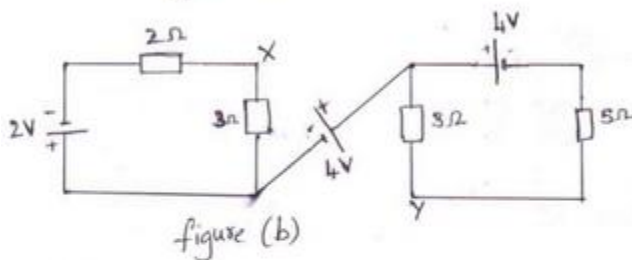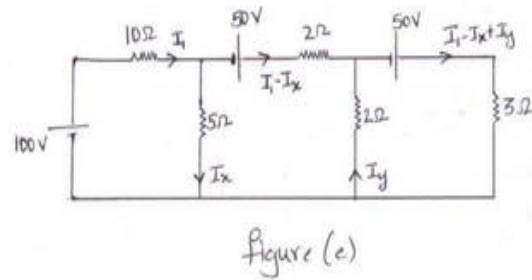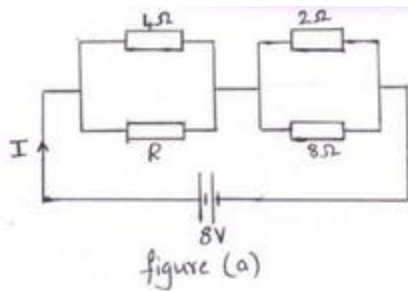14. In the parallel arrangements of resistors shown in the figure (h), the current flowing in the 8Ω resistor is $2.5A$. Find the current in other resistors, resistor X and the equivalent resistance.



Preview from Notesale.co.uk
Page 15 of 17

1(b) ELECTROMAGNETISM

1. With examples, clearly differentiate between statically induced emf & dynamically induced emf.(Jan 2013,6M)(June 2014,5M)
2. Explain Fleming's rules & their use in electromagnetism.(Jan 2015,6M)
3. Prove that the co-efficient of mutual inductance between two coils of self-inductances L_1 and L_2 is given by $M= k \sqrt{(L_1L_2)}$, where k is the co-efficient of coupling between the two coils.(Jan 2011,7M)(June 2014,8M)(June 2015,6M)