

3. A coil that has an inductance L and a resistance of $8\ \Omega$ is in parallel with a variable capacitor. At $\omega = 1.5 \times 10^6\ \text{rad/s}$, resonance is achieved when $C = 0.0037\ \mu\text{F}$. What is the inductance of the coil ? $[L = 120\ \mu\text{H}]$
4. An inductor for which $L = 40\ \text{mH}$ is to be used in parallel with a $1\ \mu\text{F}$ capacitor in a circuit that must have Q -factor at least as large as 25 when the frequency is $1\ \text{kHz}$. What is the minimum amount of resistance the coil may have ? What will the input impedance be when the minimum R is used ? $[R = 12.56\ \Omega ; Z = 3185\ \Omega]$
5. A coil has a resistance of $400\ \Omega$ and inductance of $318\ \mu\text{H}$. Find the capacitance of a capacitor which, when connected in parallel with the coil, will produce resonance with a supply frequency of $1\ \text{MHz}$. If a second capacitor of capacitance $23.5\ \text{pF}$ is connected in parallel with the first capacitor, find the frequency at which resonance will occur. $[76.5\ \text{pF} ; 870\ \text{kHz}]$

SUMMARY OF FORMULAS

1. $Y = \frac{1}{Z}$

2. $Y = \sqrt{G^2 + B^2}$

3. $G = \frac{R_1}{Z_1^2} ; \quad B = \frac{X_1}{Z_1^2}$

4. Capacitive susceptance is positive while inductive susceptance is negative.

5. The resonant frequency of a coil (R - L) in parallel with a capacitor (C) is given by ;

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

6. At parallel resonance, impedance is given by ;

$$Z_r = L/CR$$

Preview from Notesale.co.uk

Page 4 of 4