Chapter 2 Ladder Programming

2.1 Conditional Logic

The PLC scans its inputs and, depending on the program, switches on or off various combinations of outputs. The logic state of the output depends on the input conditions and so the term *conditional logic* is used.

A simple example of conditional logic could be stated as follows:

"A machine switches on if either of two *start* switches are closed and all of three *stop* switches are closed."

The conditions could be realised by a hard wire solution as shown in Fig 2.1.



Fig 2.1 Hard-Wire Conditional Logic Example

The two *start* switches are connected in parallel. Current will flow if one *or* the other *or* both are closed. The start switches are normally open. This means that the contacts are apart and no current flows when the switches are in their normal (or *unoperated* or *rest*) state.

The three *stop* switches are connected in series. Current can only flow if the first *and* the second *and* the third are closed. The *stop* switches are normally closed. This means that the contacts are connected and current can flow when the switches are in their normal state.



Machine Relay

Fig 2.13

The latch concept can be extended to any number of start and stop switches. The output Y1 in *Fig 2.13* is to be switched on by X1 or X2 and is to stay on until any of the inputs X3, X4 or X5 is switched off. The required ladder diagram is shown in *Fig 2.14* below.

	- Un
🖆 Internet TRiLOGI 5.32 (Educational Version) - Untitled	
File Edit Controller Simulate Circuit Help	Sar
Start_1 Stop_1 Stop_2	Y1 🔺
Start_2	(001)
Drev and	
Pay	

Fig 2.14

2.5 Internal relays

2.6 Timers

These have the same properties as outputs but they only exist in software. They have many uses. *Fig* 2.15 shows an internal relay being used to implement the logic function NAND. This is the inverse of the result of X1 AND X2. We will be making extensive use if internal relays later in the book.

👙 Internet TRiLOGI 5.32 (Educational Version) - Untitled	
File Edit Controller Simulate Circuit Help	
<u>Circuit # 2</u> ⊣⊢1 ⊣⊢3 ⊣⊢5 –()7 └-()8 –(Fn]9 └-(Fn]0 → / ► DE	
	Int_Relay ▲ —(RLƳ)
Int_Relay ▶ <mark>⊐_↓/</mark>	Υ1 (OUT)

Fig 2.15 Use of internal relay

Note: Most PLCs include a function called a *Set and Reset* or a *flip-flop* which latches and delatches an output or an internal relay. Throughout this food use the latch as described in section 2.4, because of the visual reset innee of the ladder rung to the equivalent hard-wire circuit, in which u chit, for is latched on by a normally-open contact connected in parallel with the start outton.

The delay-on timer introduces a delay between the start of one event and the start of another.

For example, when a start push button is pressed, the pneumatic cylinder shown in *Fig 2.16* extends, remains extended for 5 seconds and then returns. Draw the PLC wiring diagram and the appropriate ladder logic.





Fig 2.17

The *start* button and the end-of-stroke limit switch a+ are the PLC inputs and the solenoid Y1 is the output. Any other components needed for the program can be created in software.



Fig 2.18

Pressing the *start* button latches on an internal relay called *start_latch*. The *start_latch* relay switches on the output Y1 which energises the solenoid, and the cylinder extends. The cylinder rod closes the limit switch a+ which starts the timer in software. When the timer set value time has elapsed the normally-closed contact *Timer_1* in the first line of the program de-energises the *Start_latch* relay and the cylinder returns.

The timer set value in the TRiLOGI software is in units of 0.1 s. For a 5 s delay a value of 50 is entered in the drop-down menu. (More details are given in the appendix)



Fig 2.19 Setting Timer preset Value

We can do another example using the same hardware with the addition of an alarm as a second output:



Fig 2.20

Questions and Exercises



Answer:	0	a. Y1 switches on if X1 is off OR either X2 is on AND X3 is off
	0	b. Y1 switches on if X1 is on AND either X2 is off OR X3 is on
	0	c. Y1 switches on if X1 is on OR either X2 is off AND X3 is on
	0	d. Y1 switches on if X1 is off AND either X2 is on OR X3 is off

2. Pick the incorrect statement below about the ladder diagram shown



3. Which form of logic gate system is given by a ladder diagram with a rung having two normally open sets in parallel as shown?

Input_1	Output_1 (OUT)
Input_2	
Fig 2 3	1



- Answer: 👩 a. OR
 - 🕤 b. NOR
 - 🗂 c. AND
 - o d. NAND

Example 3.2.





Fig 3.16



We'll use the SFC method to implement the sequence A+B+A-B-

The SF chart is shown in *Fig 3.18* and the assignment list in *Table 3.3*.



Table 3.3

During State 2 the conveyor drive is energised (Fig 3.39) and the closing of the cam switch increments the counter. The counter is reset by the pressing of the Start button (Fig 3.40).

Questions and Exercises 3



The dcv and cylinder in Fig 3.41 are controlled by a plc with the program shown in Fig 3.43. If the 5/2 solenoid/spring dcv was replaced by a 5/2 double solenoid dcv and the second solenoid, Y2, connected to plc output Y2, then which statement below correctly describes during which

states the outputs Y1 and Y2 Answer: would be energised?

- a. Y1 in states 1 and 3, Y2 in state 2
- b. Y1 in states 1 and 3, Y2 in states 0 and 2 \sim
- c. Y1 in state 0, Y2 in state 3 $^{\circ}$
- d. Y1 in state 1, Y2 in state 2 \sim

It is necessary to automate the drilling of 2 holes in the clamp body shown in Fig. 3.52. Both holes are at an angle of 45° to the vertical.

For the drilling operation, the clamp is mounted on the rotation jig shown in Fig 3.53

Two views of the drill assembly are shown in Fig 3.54. Each double acting pneumatic cylinder is operated by a double solenoid 5/2 directional control valve. Limit switches are positioned as shown to detect the advanced and retracted cylinder positions.

When the start button is pressed the sequence is as follows

- 1. The first hole is drilled.
- 2. The jig is unclamped by cylinder I.
- 3. The jig is rotated through 90° by the rack on cylinder R.
- 4. The jig is clamped (cylinder I).
- 5. The second hole is drilled.
- 6. The jig is unclamped (cylinder I)
- 7. The jig is rotated back through 90° (cylinder R).

The drill motor runs continuously throughout the sequence **10.000 CO.UK** (a) Draw the appropriate state/transition

- (b) Draw a suitable as necessary. agram assis
- lines of lad perate the system as designed.

9.



The PLC wiring diagram is shown in Fig 4.2 and the SF chart in Fig 4.3



Example 4.2

Here is another example that uses the selective branching technique.



Fig 4.9

The cylinders above are to execute the sequence A+B+B-A- continuously until a stop button is pressed when both cylinders will stop at the end of the sequence.

If, however a self-latching switch is turned or the type becomes A+, 5s delay, A-, executed continuously as before

OVATE out an assignment list for the system

(a) Draw a plo

(c) Draw a sequential function chart for the system.

(d) Draw the ladder logic to operate the system as designed.

Solution

(a)



(d)

Initial Conditions:



Fig 4.12

Transitions:



Fig 4.13

8.

The sequence for a set of traffic lights is to be plc controlled.

The sequence is, red, red and amber, green, amber.

Select the only *incorrect* statement below regarding the program.

Answer: _____a. The transitions from one state to the next will be activated by timers.

- b. Selective branching will be necessary for the red and amber part of the sequence.
- o c. The lights will be plc outputs.
- o d. Two outputs will be on during the red and amber state.





Fig 4.36

Select the only incorrect statement below regarding the diagram Fig 4.36. (c1 is a plc counter)

Answer: a. If the plc count is less than 10, state 0 will always follow the experimental of the state of the

- b. If the plc count is less than 10, state 1 your ab ars follow state 2 Ō
- when to reset the counter. c. Provision must be made in the C
- d. The counter present value is the deciding factor between trans 2-0 and trans 2 0 0000 Page a. The courtrens and the court trans and the court trans and the court of the court

10.



Two extra waiting states S10 and S11 have been introduced because it is not possible for a the sequence to simultaneously enter a selective and a parallel branch. Once states 10 and 11 are active the choice of routes for the program depends on whether components are in place under the drill and countersink.

The PLC wiring diagram with the two additional inputs is shown in *Fig 5.18* and the modified assignment list is shown in *Table 5.3*.



Fig 5.18

■ Call the input *Start_Button* or *Start Button* and press return.

