

Series means that the devices are connected in such a way that there is the same electric current through each device

$$V = V_1 + V_2$$

$$\text{dissipation} = P = I^2 R$$

$$V = IR_1 + IR_2$$

$$V = I(R_1 + R_2)$$


$$V = IR_s$$

$$R_s = R_1 + R_2 + R_3 + \dots$$

Series resistors

Parallel wiring

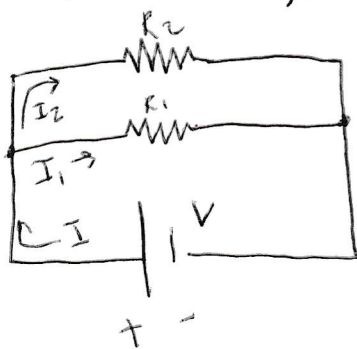means that the devices are connected in such way that the voltage is applied across each wire



$$I = I_1 + I_2$$

$$= \frac{V}{R_1} + \frac{V}{R_2}$$

$$= V \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$= V \left( \frac{1}{R_p} \right)$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

Preview from Notesale.co.uk  
Page 1 of 1