

(b) Line regulation = $\frac{\text{change in output voltage}}{\text{change in input voltage}} \cdot 100$

Line regulation = $\frac{0.194}{330} \cdot 100 = 0.058\%$

Preview from Notesale.co.uk
Page 10 of 14

References:

1. <http://www.techterms.com/definition/powersupply> (website visited on the 2nd of May, 2013)
2. <http://electronicsclub.info/powersupplies.htm> (website visited on the 24th of May, 2013)
3. <http://www.doityourself.com/stry/8-advantages-of-a-dual-dc-power-supply#b> (website visited on the 1st of June, 2013)
4. "Electron Devices & Circuits-Principles & Applications" by N. P. Deshpande
5. "Electronic Projects For Beginners" by A.K.Maini
6. www.uk.farnell.com (website visited on the 20th of June, 2013)

Preview from Notesale.co.uk
Page 14 of 14